

**VSM COLLEGE OF ENGINEERING**

**ECE DEPARTMENT**

**LECTURE NOTES**

**ON**

**POWERELECTRONICS(R19)**



**JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY: KAKINADA**  
**KAKINADA – 533 003, Andhra Pradesh, India**  
**DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING**

<b>III Year - II Semester</b>		<b>L</b>	<b>T</b>	<b>P</b>	<b>C</b>
		<b>3</b>	<b>0</b>	<b>0</b>	<b>3</b>
<b>POWER ELECTRONICS</b> <b>Open Elective (OE1)</b>					

**Course objectives:**

**The main objectives of this course are:**

- To study the characteristics of various power semiconductor devices and gate drive circuits.
- To understand the operation of single phase full-wave converters and analyze harmonics in the input current.
- To study the operation of three phase full-wave converters.
- To understand the operation of different types of DC-DC converters.
- To understand the operation of inverters and application of PWM techniques for voltage control and harmonic mitigation.

**UNIT-I:**

**Power Semiconductor Devices:** Operation of SCR, power MOSFET and power IGBT and their characteristics–Gate drive circuits for SCR, IGBT and MOSFET–protection circuits for power IGBT and power MOSFETs.

**UNIT-II:**

**AC-DC Single-Phase Converters:** 1-phase fully-controlled bridge rectifiers feeding R load, RL, RLE loads (continuous and discontinuous current conduction mode of operation)– 1-phase semi-controlled bridge rectifiers feeding R, RL and RLE loads (continuous and discontinuous current conduction mode of operation)– Harmonic Analysis.

**UNIT-III:**

**AC-DC Three-Phase Converters:** 3-phase Full converter feeding R, RL and RLE loads (continuous current conduction mode only)– 3-phase semi-converter feeding R, RL and RLE loads (continuous current conduction mode only)–Harmonic analysis -Dual converter.

**UNIT-IV:**

**DC-DC Converters:** Analysis of Buck, boost, buck-boost converters in Continuous Conduction Mode (CCM) and Discontinuous Conduction Modes (DCM) – Output voltage equations using volt-sec balance in CCM & DCM- output voltage ripple & inductor current ripple for CCM only – Principle operation of forward and fly back converters in CCM.



**JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY: KAKINADA**  
**KAKINADA – 533 003, Andhra Pradesh, India**  
**DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING**

**UNIT – V:**

**DC–AC Converters and AC-AC converters:** 1- phase half-bridge and full bridge inverters with R and RL loads – Unipolar and bipolar switching-Quasi-square wave pulse width modulation-3-phase square wave inverters –  $120^\circ$  conduction and  $180^\circ$  conduction modes of operation – Sinusoidal pulse width modulation –single-phase Current Source Inverter (CSI)-single-phase AC-AC voltage regulator with R and RLload.

**TEXT BOOKS:**

1. Power Electronics: converters, applications & design -by Nedmohan, Tore M.Undeland, Robbins by Wiley India Pvt.Ltd.
2. Power Electronics- by Daniel W.Hart, Mc Graw Hillpublications
3. Power Electronics: Circuits, Devices and Applications – by M. H. Rashid, Prentice Hallof India

**REFERENCE BOOKS:**

1. Power Electronics: Essentials & Applications by L.Umanand, Wiley, Pvt. Limited, India,2009
2. Elements of Power Electronics–Philip T.Krein. Oxfordpublishers.
3. Power Electronics – by P.S.Bhimbra, KhannaPublishers.

**Course Outcomes:**

**At the end of this course the student will be able to:**

- Explain the characteristics of various power semiconductor devicesand understand the gate drivercircuits.
- Explain the operation of single-phase full wave converters and performharmonic analysis.
- Explain the operation of three phase full–wave converters and performharmonic analysis.
- Analyze the operation of different types of DC-DCconverters.
- Explain the operation of inverters and application of PWM techniques for voltagecontrol and harmonicmitigation.

POWER SEMICONDUCTOR DEVICES

Introduction to the subject:-

Basically, the field of <sup>electrical</sup> engineering <sup>may be</sup> divided into three areas of specialisation namely, (i) electronics  
(ii) power  
(iii) control

- In that Electronics deals with the study of semiconductor devices and circuits at low power level
- Power deals with the generation, transmission and distribution of electrical energy with static and rotating power equipments.
- Control deals with the steady state and dynamic characteristics of closed loop systems.

Def:- Power electronics is defined as the use of solid state electronics for the control and conversion of electric power.  
(Control of electric power means, the output voltage can be controlled and conversion of electric power means, ac to dc, dc to ac, dc to dc and ac to ac)

HISTORY OF POWER ELECTRONICS:-






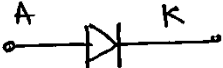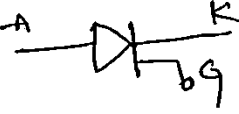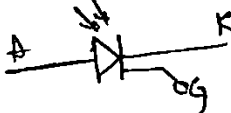
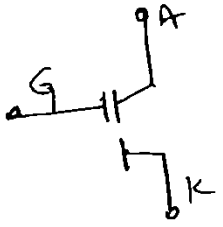

- The Power electronics history began with the development of mercury arc rectifier in the year 1900. Then the other power devices like metal tank rectifier, grid controlled vacuum tube rectifier, ignitron, phanotron, thyatron and magnetic amplifier, were developed & used gradually for power control applications until 1950.

- The first SCR (Silicon controlled Rectifier) or Thyristor was invented and developed by Bell lab's in 1956 which was the first PNPN triggering transistor.
- The second electronic revolution began in the year 1958 with the development of the commercial grade Thyristor by the General Electric company (GE)

### Applications of Power Electronics:-

- 1. control of ac and dc drives in rolling mills, paper and textile mills, traction vehicles, mine winders, cranes, ventilation fans etc.
- 2. Uninterruptible power supplies (UPS) for critical loads such as computers and space applications
- Machine tool control.
- power control in metallurgical and chemical processes using arc melting, induction heating and melting, resistance heating, arc welding etc.
- Static power compensators, transformer tap changers and static contactors for industrial power systems.
- High voltage Direct current (HVDC) system
- Illumination controls for lighting in trains, homes and theatres
- Excitation systems for alternator and synchronous condenser.
- Battery charging
- Electric Traction
- Solid state controllers for home appliances

## Maximum Ratings of Power semiconductor devices.


S.No.	Device	Circuit symbol	Voltage/ Current rating	Upper operating frequency (KHz)
1.	Diode		5000 V / 5000 A	1.0
2.	Thyristors			
a)	SCR		7000 V / 5000 A	1.0
b)	LASCR (Light activated SCR)		6000 V / 3000 A	1.0
c)	ASCR / RCT (Asymmetrical SCR, Reverse conducting thyristor)		2500 V / 400 A	2.0
d)	GTO (Gate turn off Thyristor)		5000 V / 3000 A	2.0
e)	SITH (Static Induction Thyristor)		2500 V / 500 A	100.0
f)	MCT (MOS controlled Thyristor)		1200 V / 40 A	20.0
g)	TRIAC		1200 V / 1000 A	0.156

## PRINCIPLE OF OPERATION OF SCR:-

→ SCR is a four layered, three terminal device with three junctions namely  $J_1, J_2, J_3$ .

It is a PNPN switching device.

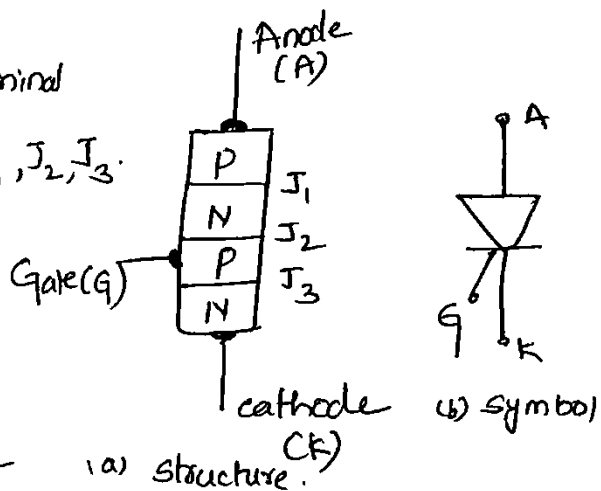
The four layers in this device are PNPN layers.



→ The three terminals of the device are Anode, cathode and gate. Here, the Anode and cathode terminals are connected to the main power circuit. The gate terminal carries a low level gate current in the direction gate to cathode. Normally, the gate terminal is provided at the layer near the cathode. This is known as cathode gate.

→ When the end P layer near the anode is made more positive when compared to N layer near the cathode, Junctions  $J_1$  and  $J_3$  gets forward biased where as the middle junction  $J_2$  gets reverse biased. Junction  $J_2$  is known as Junction capacitance as it acts as a capacitor in this mode. Due to the depletion layer formed at this junction, no current flows through the device. But due to the drift of mobile charge carriers a small amount of leakage current flows through the circuit. As the leakage current is negligibly small, the device does not conduct. This state is known as forward blocking state or OFF state of the device as it blocks the forward biased voltage.


→ During the 'OFF' state, an SCR acts as a high Impedance device.

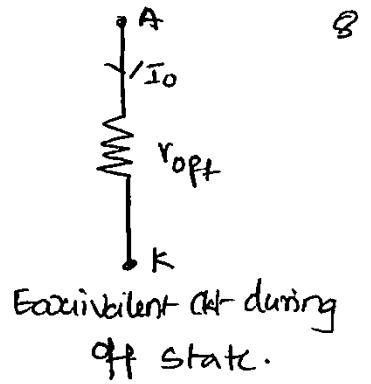

STATIC V-I CHARACTERISTICS OF AN SCR:-

→ An elementary circuit diagram for obtaining static V-I characteristics of a thyristor is shown in fig.

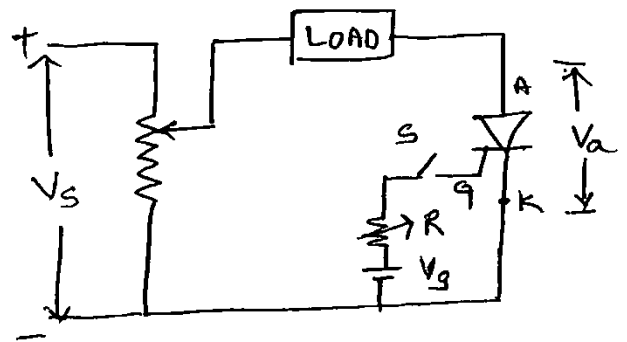
→ The anode and cathode are connected to main source through the load. The gate and cathode are fed from a source  $V_g$  which gives positive gate current from gate to cathode.



→  $V_a$  is the anode voltage across thyristor terminals A and K and  $I_a$  is the anode current. ~~Typical~~ <sup>The static</sup> V-I characteristic of a thyristor has three basic modes of operation.

- a) Reverse blocking Mode
- b) Forward blocking (off-state) Mode
- c) Forward conduction (ON-state) Mode

a)

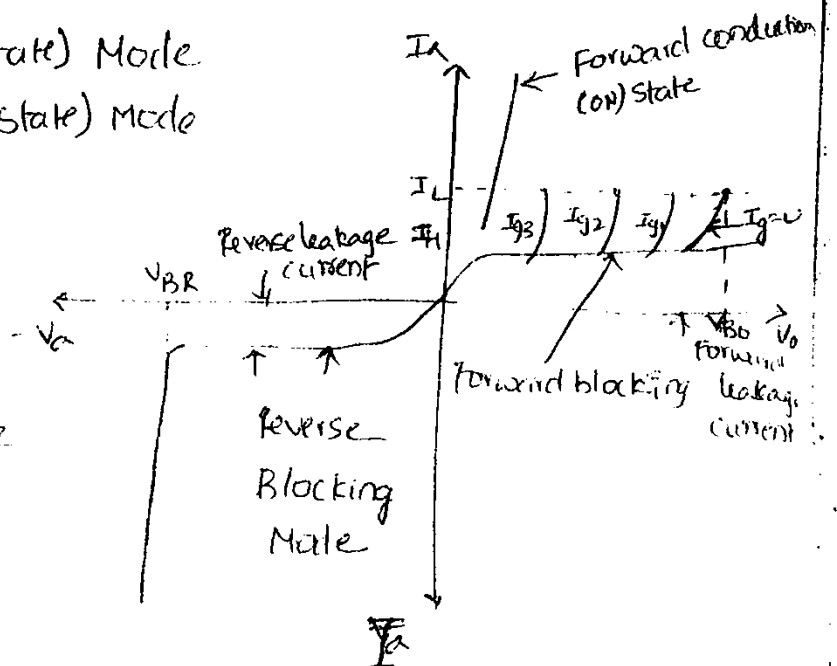


- $V_{BO}$  - Forward breakover voltage
- $V_{BR}$  - Reverse breakover voltage
- $I_g$  - gate current
- $I_L$  - Latching current
- $I_H$  - Holding current


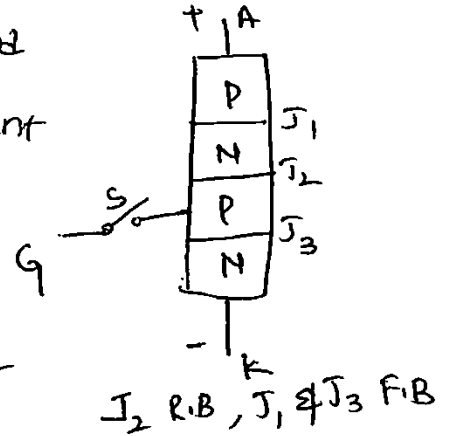
## b) Forward Blocking Region :-

In this region, the anode is made positive w.r.t cathode and therefore, junctions  $J_1$  &  $J_3$  are F.B and  $J_2$  remains R.B. Hence the anode current is a small forward leakage current.



→ In case the forward voltage is increased, then the reverse biased junction  $J_2$  will have an avalanche breakdown at a voltage called forward breakover voltage  $V_{Bo}$ .

→ When forward voltage is less than  $V_{Bo}$ , thyristor offers high Impedance.  $\therefore$  SCR can be treated as an open switch even in the forward blocking mode.

## c) FORWARD CONDUCTION MODE :-

→ In this mode, SCR conducts currents from Anode to cathode with a very small voltage drop across it. A SCR is brought from forward blocking mode to forward conduction mode by turning it ON by exceeding the forward breakover voltage (or) by applying a gate between gate and cathode.

→ In this high conduction mode, the anode current is determined essentially by the external load impedance. Therefore when the thyristor conducts forward current, it can be regarded as a closed switch.

→ Anode current  $\left\{ \begin{array}{l} \text{Latching current} \\ \text{Holding current} \end{array} \right.$

TYPES OF POWER Electronics Converters :-

→ A power electronic converter is made up of some power semiconductor devices controlled by Integrated Circuits. This converter converts the input power of one form to output power of some other form.

→ The power electronic converter (or circuits) can be classified into six types

- 1. Diode rectifiers
- 2. AC-DC converters (controlled Rectifiers)
- 3. AC-AC converters.
  - (i) AC voltage regulators
  - (ii) Cyclo converters
- 4. DC-DC converters (DC choppers)
- 5. DC-AC converters (Inverters)
- 6. Static switches.

1. Diode Rectifiers :-


A diode rectifier circuit converts ac input voltage into fixed dc output voltage. The i/p voltage to the rectifier could be either single phase or three phase.

Applications :-

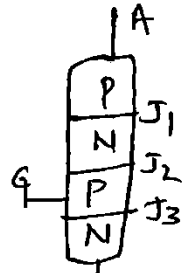- (a) Electric traction
- (b) Battery charging
- (c) uninterruptible power supply (UPS)
- (d) power supplies
- (e) electro chemical processing

Need For Snubber Circuit :-

→ when the Forward voltage is applied across the anode and cathode of the thyristor, the outer two junctions ( $J_1$  &  $J_3$ ) are Forward biased and the inner junction ( $J_2$ ) is reverse biased. In the reverse biased condition, junction  $J_2$  exhibits the characteristics of a capacitor. Holes from P layer of  $J_1$  accumulate at the junction  $J_2$  and electrons from N layer of  $J_3$  accumulates at the other side of junction  $J_2$ . There exists space charge carriers across the junction  $J_2$ .




→ If a large amount of voltage is applied with in a short interval of time, charging current  $i_c$  flows through SCR. without the application of the gate signal the SCR gets turned ON. It leads to the Malfunctioning of the device. so, the rate of rise of voltage across the anode to cathode should be limited. so, an RC network should be connected across the SCR in order to limit  $\frac{dv}{dt}$  rating.

Design Aspects of Snubber circuit :-

→ when the switch 'S' is closed, a sudden voltage appears across the circuit Capacitor  $C_s$ . The capacitor behaves as a short circuit.

→ The voltage across the capacitor and thyristor is zero at that instant because they are connected in parallel

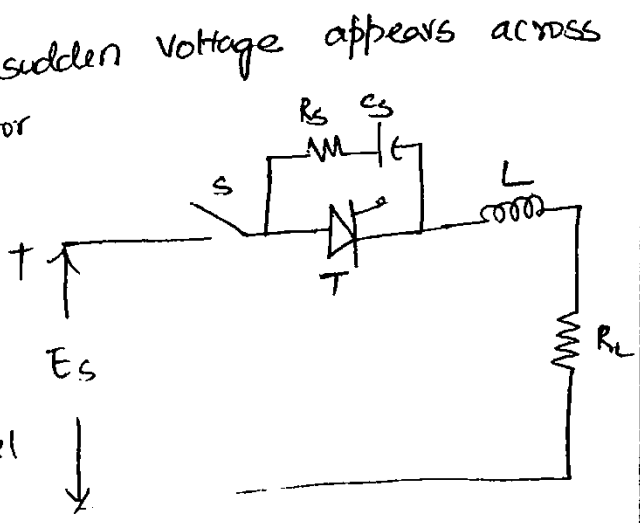→ As the time goes on, the voltage across the capacitor  $C_s$  builds up slowly with less  $\frac{dv}{dt}$  rating



CLASSIFICATION OF POWER TRANSISTORS:-

Power transistors may be classified into three types. they are

- 1. Bipolar junction Transistors (BJTs)
- 2. Metal oxide semiconductor field Effect Transistors (MOSFETs)
- 3. Insulated gate bipolar transistors (IGBTs)



Bipolar Junction Transistors:-

→ It is a three layered device having two junctions npn or pnp semiconductor device.


→ whenever the p region is sandwiched by two n regions an npn transistor is formed.

→ whenever the n region is sandwiched by two p regions a pnp transistor is formed.

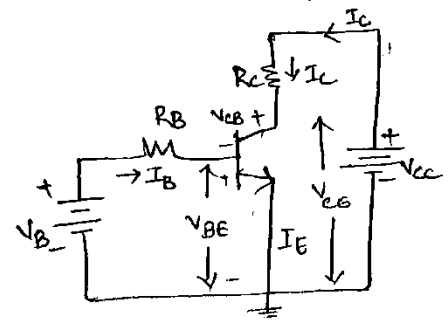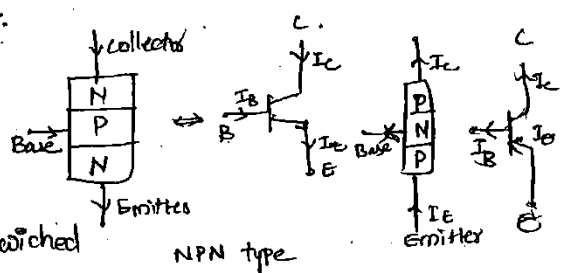⇒ BJT is a device where the current flow in the device is due to the mobility of both the charge carriers i.e electrons and holes.



NPN transistor circuit

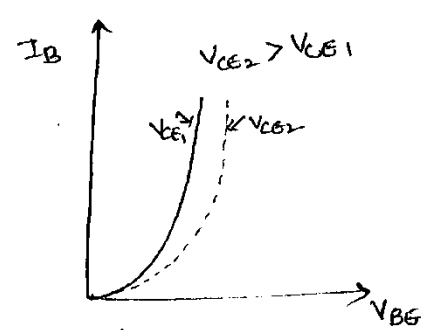


IB characteristics

→ common emitter configuration of transistor is most commonly used for switching application.

→ IB characteristics is obtained by plotting the graph b/w the base current IB and the base emitter voltage VBE.

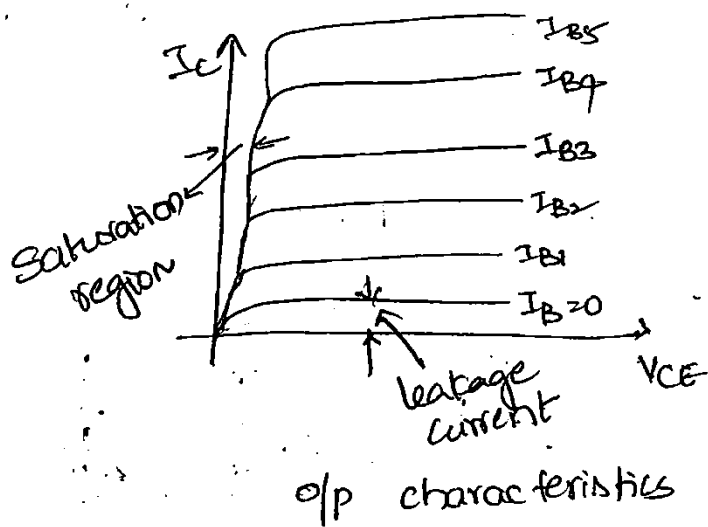→ From the i/p characteristics curve, we observe that whenever  $V_{CE}$  is increased, the base current gets decreased.




→ o/p characteristics of BJTs are obtained by plotting a graph b/w collector current  $I_C$  and collector emitter voltage  $V_{CE}$ . whenever  $I_B = 0$ , there exists a small leakage current as the voltage  $V_{CE}$  value is increased.
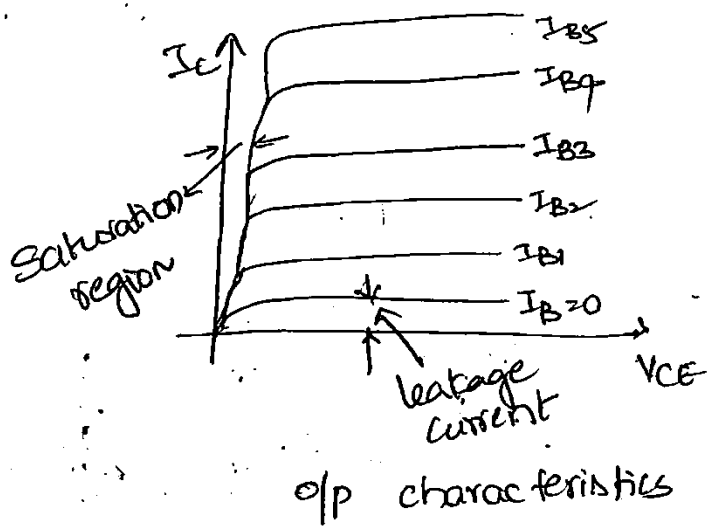
### POWER MOSFETS :-

- MOSFET stands for Metal oxide semiconductor, field effect transistor. It has 3 terminals i.e. gate, source and drain.
- It is a voltage controlled device and is available for high voltage and current ratings.
- MOSFETs are becoming popular in low to medium power applications and ~~bees~~ high frequency power electronic circuits, since the turn on time is very less.
- In the case of transistor secondary breakdown take place. But in the case of MOSFETs, it doesnot have the problem of secondary breakdown, as it operates in the safe operating area.

→ From the i/p characteristics curve, we observe that whenever  $V_{CE}$  is increased, the base current gets decreased.




→ o/p characteristics of BJTs are obtained by plotting a graph b/w collector current  $I_C$  and collector emitter voltage  $V_{CE}$ . whenever  $I_B = 0$ , there exists a small leakage current as the voltage  $V_{CE}$  value is increased

### POWER MOSFETS :-

- MOSFET stands for Metal oxide semiconductor, field effect transistor. It has 3 terminals i.e. gate, source and drain.
- It is a voltage controlled device and is available for high voltage and current ratings.
- MOSFETs are becoming popular in low to medium power applications and ~~bees~~ high frequency power electronic circuits, since the turn on time is very less.
- In the case of transistor secondary breakdown take place. But in the case of MOSFETs, it doesnot have the problem of secondary breakdown, as it operates in the safe operating area.

→ The switching times are very short, being in the range of few tens of nano secs to a few hundred nano sec. depending upon the type of device.

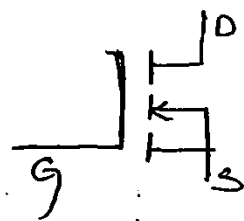→ It is used in high current applications



Symbol of Power MOSFET.

### Types of Power MOSFET:-

The two main types of Power MOSFETs are

1. Depletion MOSFET
2. Enhancement MOSFET


Each type are further classified as

- (i) n channel MOSFET
- (ii) p channel MOSFET

→ n channel enhancement MOSFET is more common because of higher mobility of electrons.

→ The bottom layer is  $n^+$  substrate. Gate and treated as a source.

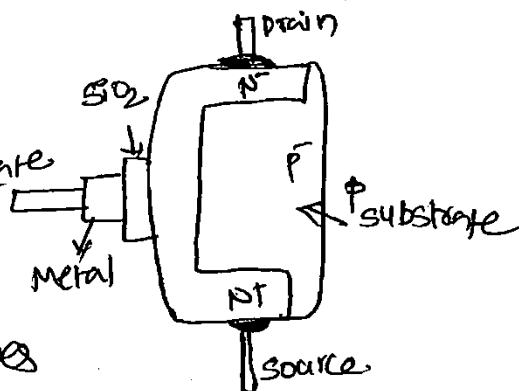The  $n^-$  layer is called the drain drift region. This <sup>drift</sup> region determines the break down voltage of the device, ~~and~~ a metal layer is deposited to form the drain terminal.



Basic structure of N channel power Mosfet

→  $p^-$  regions are diffused in the epitaxially grown  $n^-$  layer  $SiO_2$  (silicon dioxide) layer is added which is then etched so as to fit metallic source and gate terminals.


### Operation:-

When the Gate source Voltage  $V_{GS}$  is zero, and drain source Voltage  $V_{DS}$  is present, then  $n^- - p^-$  junctions are reverse biased and no current flows from drain to source. So, the device acts as a open switch.

→ when Gate terminal is made +ve w.r.t source, an electric field is created and electrons form n-channel in the  $p^-$  region.

now, the current flows from Drain to source, when gate voltage  $V_{GS}$  is increased drain current  $I_D$  also increases. controlled by gate voltage.

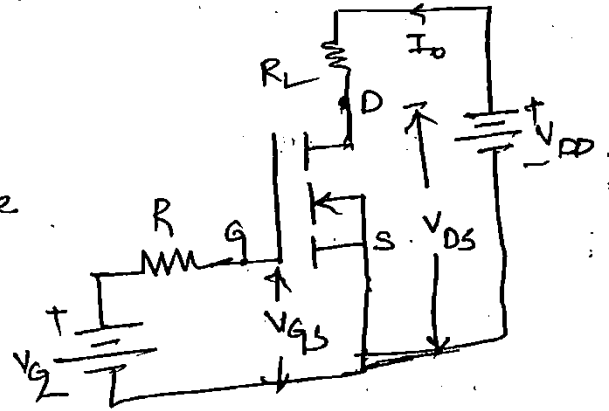so Power MOSFET is also called as Voltage controlled device. Here, the controlling parameter is gate source voltage  $V_{GS}$ .




N channel Power MOSFET  
Circuit diagram

i.e., o/p ~~power~~ current can be

### Static characteristics:-
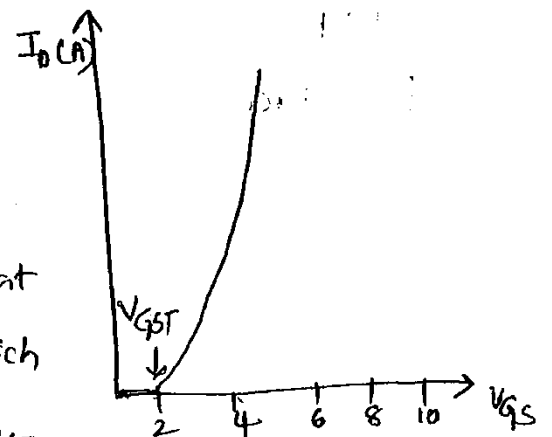
#### (a) Transfer characteristics:-

This characteristic shows the variation of drain current  $I_D$  as a function of gate source Voltage  $V_{GS}$ . It is seen that there is threshold voltage  $V_{GS(T)}$  below which the device is OFF. The magnitude of  $V_{GS(T)}$  is of the order of 2 to 3V.



Transfer characteristics  
for n-channel Power  
MOSFET




output characteristics :-

→ Power MOSFET o/p characteristics indicate the variation of drain current  $I_D$  as a function of drain-source voltage  $V_{DS}$  as a parameter.

→ For low values of  $V_{DS}$ , the graph b/w  $I_D - V_{DS}$  is almost linear.  $R_{DS} = \frac{V_{DS}}{I_D}$ .

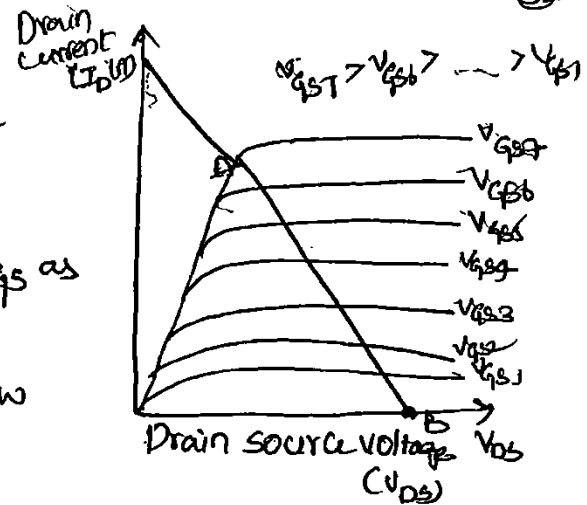→ For given  $V_{GS}$ , if  $V_{DS}$  is increased, o/p characteristics is relatively flat indicating that drain current is nearly constant.



### MOSFET


1. Power MOSFET has lower switching losses.
2. It has more conduction losses.
3. It is a voltage controlled device.
4. It is a unipolar device.
5. Power MOSFET operate at switching frequencies in the MHz range.
6. MOSFET has positive temp. coefficient.
7. Secondary breakdown does not occur in MOSFET.
8. MOSFETs are available with ratings upto 500V, 40A.

### BJT

1. BJT has higher switching losses.
2. It has low conduction losses.
3. It is a current controlled device.
4. It is a bipolar device.
5. BJT operate at switching frequencies in kHz range.
6. BJT has negative temp coefficient.
7. BJT has secondary breakdown.
8. BJTs are available with ratings upto 1200V and 800A.
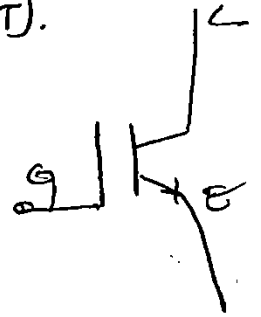
## IGBT (Insulated Gate Bipolar Transistor) :


→ IGBT has high  $i/p$  Impedance like a MOSFET and low onstate power loss as in a BJT. IGBT is also known as Metal oxide insulated Gate transistor (MOSIGT), Conductivity-Modulated Field effect transistor (COMFET) or Grain Modulated FET (GEMFET). It is also called insulated Gate transistor (IGT).


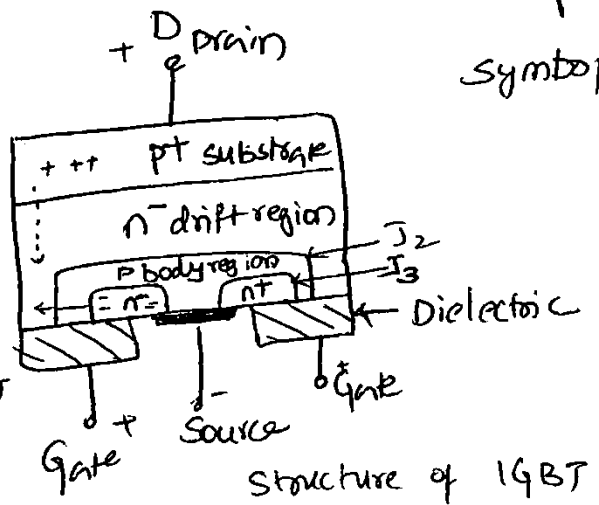
### Structure of IGBT:-

→ The IGBT structure is very close to the n-channel MOSFET.

The major difference b/w the structure of the n-channel MOSFET and IGBT is that a highly doped




Structure of IGBT

→ From the basic structure, n+ p body region, n- forms the power MOSFET. The n- drift region forms the drain. The next part will constitute the three layers p n- p, that forms a BJT b/w the drain and source terminals p n- p regions will behave as collector, base and emitter (E) of pnp transistor resp.

Drift current: The transport of the charges in a device under the influence of the electric field is known as drift current.


Diffusion current: The transport of charges in a device, under the influence of the non uniform concentration gradient is termed as diffusion current.

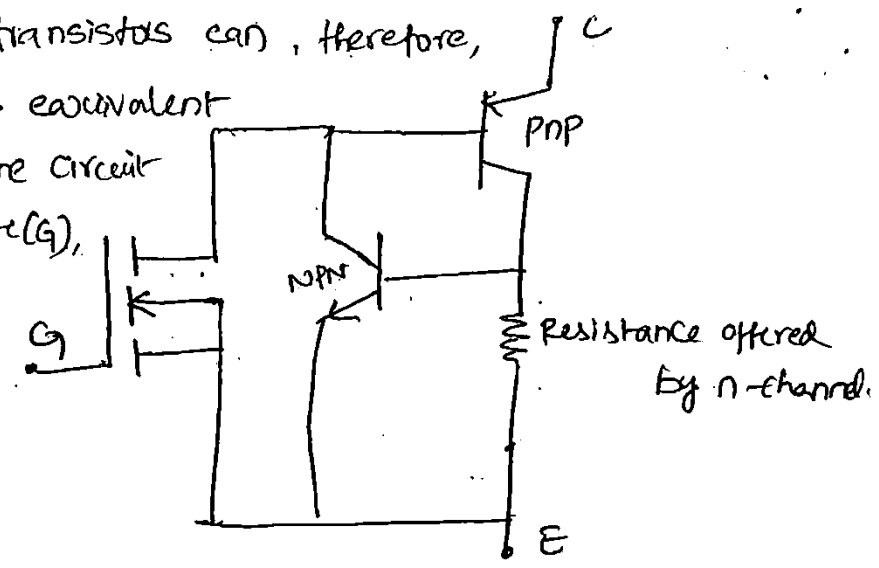→ The two PNP and NPN transistors can, therefore, be connected to give the equivalent circuit of an IGBT. The circuit symbol for IGBT with Gate (G), emitter (E) and collector (C) as its three terminals




IGBT Static characteristics:-

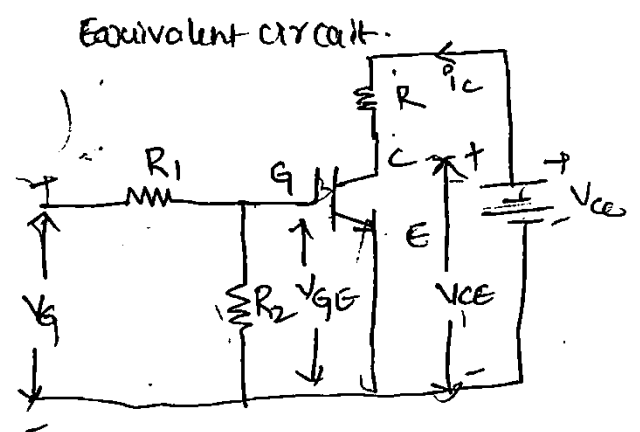→ Static V-I characteristics of an IGBT (n-channel type) shows the plot of collector current  $I_C$  vs collector-emitter voltage  $V_{CE}$  for various values of Gate emitter voltages. In the forward direction, the shape of the o/p characteristics is similar to that of BJT. But here the controlling parameter is gate emitter voltage  $V_{GE}$  because IGBT is a voltage controlled device.




IGBT circuit diagram

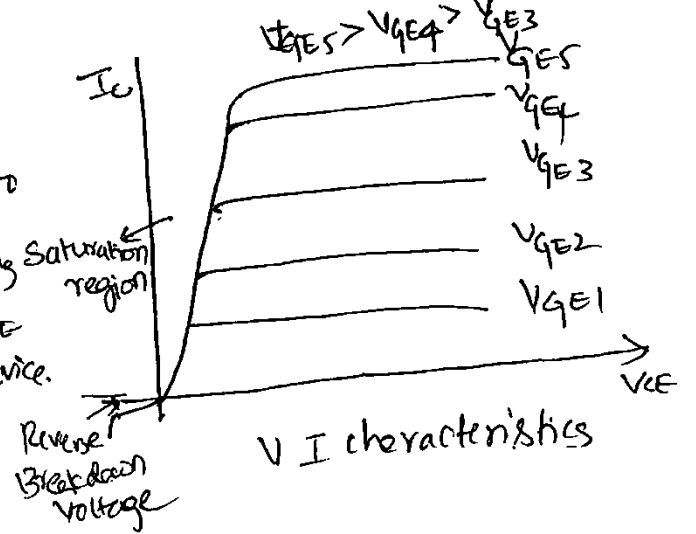

V I characteristics

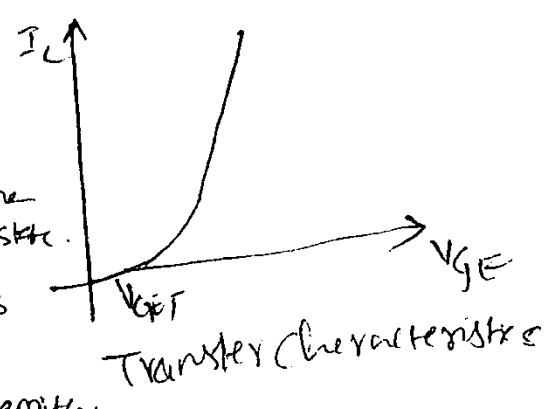→ The transfer characteristic of an IGBT is a plot of collector current  $I_C$  vs. Gate emitter voltage  $V_{GE}$ . This characteristic is same as power MOSFET. When  $V_{GE}$  is less than  $V_{GET}$ , IGBT is in the OFF state. When the device is OFF, junction  $J_2$  blocks forward voltage, and in case reverse voltage, appears across collector and emitter junction  $J_1$ , blocks it.



Transfer characteristics

## IGBT Applications:

→ IGBTs are widely used in medium power applications such as dc and ac motor drives, UPS systems, power supplies and drives for solenoids, relays and contactors.

### MOSFETS

→ In the power MOSFET, the decrease in the electron mobility with increasing temp. results in a rapid increase in the ON state resistance of the channel and hence the ON state drop.

2. The ON state voltage drop increases by a factor of 3 between room temp. and  $200^{\circ}\text{C}$
3. At highest temp., max. current rating goes down to  $\frac{1}{3}$  value
4. Current sharing in multiple paralleled MOSFETs is comparatively poor than IGBTs.
5. The turn ON transients are identical to IGBTs
6. Power MOSFET is suited for applications that require low blocking voltages and high operating frequencies

### IGBTs

→ In IGBTs, the increase in voltage drop is very small.

2. Here with the identical conditions, the increment in the ON state voltage drop is very small.
3. At high ambient temp., IGBTs extraordinarily well suited
4. Current sharing in multiple paralleled IGBTs is far better than Power MOSFET.
5. Turn ON transients are identical to MOSFETs
6. IGBT is the preferred device for applications that require high blocking voltages and lower operating frequencies

# UNIT – II

## Phase control technique – Single phase Line commutated converters

Unlike diode rectifiers, PCR or phase controlled rectifiers has an advantage of regulating the output voltage. The diode rectifiers are termed as uncontrolled rectifiers. When these diodes are switched with Thyristors, then it becomes phase control rectifier. The o/p voltage can be regulated by changing the firing angle of the Thyristors. The main application of these rectifiers is involved in speed control of DC motor.

### What is a Phase Controlled Rectifier?

The term PCR or Phase controlled rectifier is a one type of rectifier circuit in which the diodes are switched by Thyristors or SCRs (Silicon Controlled Rectifiers). Whereas the diodes offer no control over the o/p voltage, the Thyristors can be used to differ the output voltage by adjusting the firing angle or delay. A phase control Thyristor is activated by applying a short pulse to its gate terminal and it is deactivated due to line communication or natural. In case of heavy inductive load, it is deactivated by firing another Thyristor of the rectifier during the negative half cycle of i/p voltage.

### Types of Phase Controlled Rectifier

The phase controlled rectifier is classified into two types based on the type of i/p power supply. And each kind includes a semi, full and dual converter.

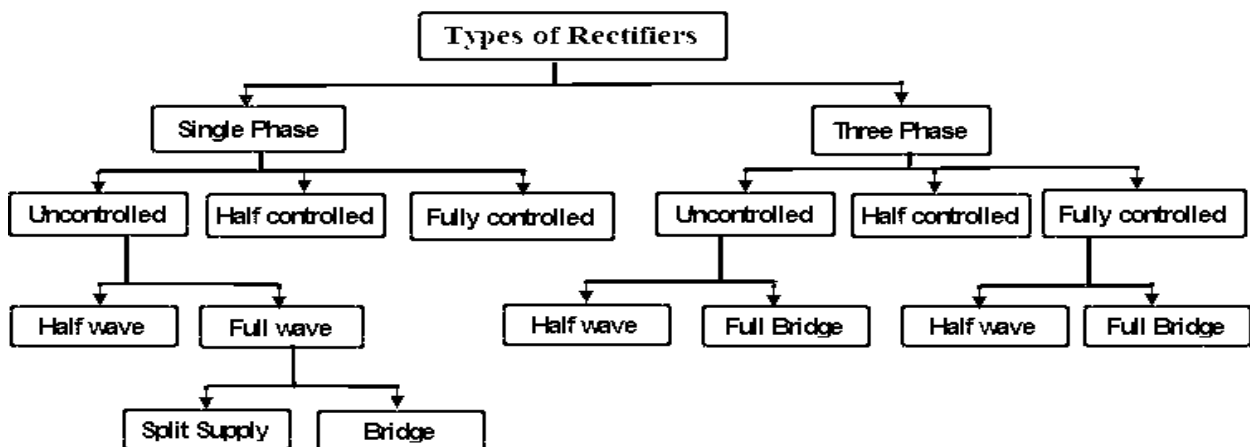


Figure: 2.1. Classification of rectifiers

### **Single-phase Controlled Rectifier**

This type of rectifier which works from single phase AC i/p power supply

Single Phase Controlled Rectifiers are classified into different types

**Half wave Controlled Rectifier:** This type of rectifier uses a single Thyristor device to provide o/p control only in one half cycle of input AC supply, and it offers low DC output.

**Full wave Controlled Rectifier:** This type of rectifier provides higher DC output

- Full wave controlled rectifier with a center tapped transformer requires two Thyristors.
- Full wave bridge controlled rectifiers do not need a center tapped transformer

### **Three-phase Controlled Rectifier**


This type of rectifier which works from three phase AC i/p power supply

- A semi converter is a one quadrant converter that has one polarity of o/p voltage and current.
- A full converter is a two quadrants converter that has polarity of o/p voltage can be either +ve or -ve but, the current can have only one polarity that is either +ve or -ve.
- Dual converter works in four quadrants – both o/p voltage and o/p current can have both the polarities.

### **Operation of Phase Controlled Rectifier**

The basic working principle of a PCR circuit is explained using a single phase half wave PCR circuit with a RL load resistive shown in the following circuit.

A single phase half wave Thyristor converter circuit is used to convert AC to DC power conversion. The i/p AC supply is attained from a transformer to offer the required AC supply voltage to the Thyristor converter based on the o/p DC voltage required. In the above circuit, the primary and secondary AC supply voltages are denoted with  $V_P$  and  $V_S$ .

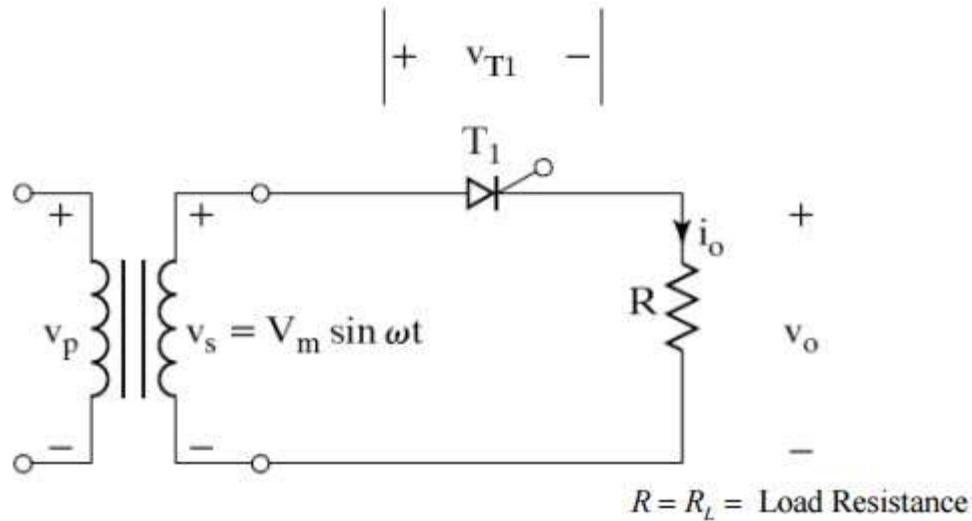

**Figure: 2.2. Single phase half wave rectifier circuit**

During the +ve half cycle of i/p supply when the upper end of the transformer secondary winding is at a +ve potential with respect to the lower end, the Thyristor is in a forward biased state.

The thyristor is activated at a delay angle of  $\omega t = \alpha$ , by applying an appropriate gate trigger pulse to the gate terminal of thyristor. When the thyristor is activated at a delay angle of  $\omega t = \alpha$ , the thyristor behaves and assuming a perfect thyristor. The thyristor acts as a closed switch and the i/p supply voltage acts across the load when it conducts from  $\omega t = \alpha$  to  $\pi$  radians. For a purely resistive load, the load current  $i_o$  that flows when the thyristor T1 is on, is given by the expression.

$$i_o = v_o / R_L, \text{ for } \alpha \leq \omega t \leq \pi$$

### Applications of Phase Controlled Rectifier

Phase controlled rectifier applications include paper mills, textile mills using DC motor drives and DC motor control in steel mills.


- AC fed traction system using a DC traction motor.
- Electro-metallurgical and Electrochemical processes.
- Reactor controls.
- Magnet power supplies.
- Portable hand instrument drives.

- Flexible speed industrial drives.
- Battery charges.
- High voltage DC transmission.
- UPS (Uninterruptible power supply systems).

**Operation of half converter with R and RL loads**

**Single Phase Half Wave Controlled Rectifier with ‘R’ load:**

As shown in figure below primary of transformer is connected to ac mains supply with which SCR becomes forward bias in positive half cycle. T1 is triggered at an angle  $\alpha$ , T1 conducts and voltage is applied across R.

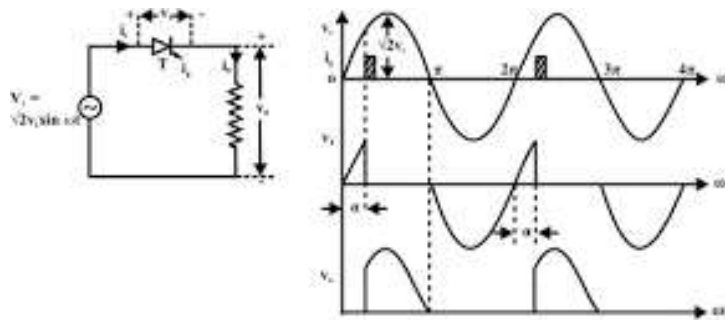

**Figure: 2.3 Single phase half wave rectifier with R load with waveforms**

The load current  $i_o$  flows through ‘R’  
the waveforms for voltage & current are as shown above.

As load is resistive,

Output current is given as,

$$I_o = \frac{V_o}{R}$$

Hence shape of output current is same as output voltage

As T1 conducts only in positive half cycle as it is reversed bias in negative cycle, the ripple frequency of output voltage is-

fripple= 50 Hz (supply frequency)

Average output voltage is given as,



$$V_o(Avg) = \frac{1}{T} \int_0^T V_o(\omega t) d\omega t$$

i.e Area under one cycle.

Therefore  $T=2\pi$  &  $V_o(\omega t) = V_m \sin \omega t$  from  $\alpha$  to  $\pi$  & for rest of the period  $V_o(\omega t)=0$

$$\begin{aligned} \therefore V_o(Avg) &= \frac{1}{2\pi} \int_0^{2\pi} V_m \sin(\omega t) d\omega t \\ &= \frac{V_m}{2\pi} [-\cos \omega t]_{\alpha}^{\pi} \\ &= \frac{V_m}{2\pi} (1 + \cos \alpha) \end{aligned}$$

Power transferred to load,

$$P_o(Avg) = \frac{V_o^2(Avg)}{R}$$

Thus, power & voltage can be controlled by firing angle.

### Single Phase Half Wave Controlled Rectifier with 'RL' load:

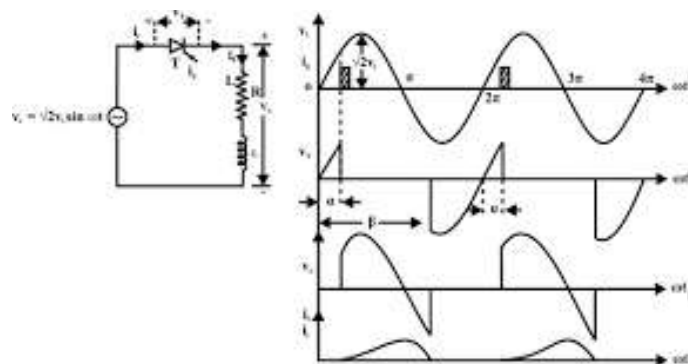


Figure: 2.4 Single phase half wave rectifier with RL load with waveforms

Figure above shows the single phase half wave rectifier with RL Load.

- Normally motors are inductive loads

L= armature of field coil inductance

R= Resistance of coil.

- In positive half cycle, SCR starts conduction at firing angle “ $\alpha$ ”.
- Drop across SCR is small & neglected so output voltage is equal to supply voltage.
- Due to ‘ $R_L$ ’ load, current through SCR increases slowly.
- At ‘ $\pi$ ’, supply voltage is at zero where load current is at its max value.
- In positive half cycle, inductor stores energy & that generates the voltage.
- In negative half cycle, the voltage developed across inductor, forward biases SCR & maintains its conduction.
- Basically with the property of inductance it opposes change in current.
- Output current & supply current flows in same loop, so all the time  $i_o=i_s$ .
- After  $\pi$  the energy of inductor is given to mains & there is flow of ‘ $i_o$ ’. The energy reduces as it gets consumed by circuit so current also reduces.
- At ‘ $\beta$ ’ energy stored in inductance is finished, hence ‘ $i_o$ ’ becomes zero & ‘T1’ turns off.
- ‘ $i_o$ ’ becomes zero from ‘ $\beta$ ’ to ‘ $2\pi+\alpha$ ’ hence it is discontinuous conduction.

The average output voltage  $V_0 = \frac{1}{2\pi} \int_{\alpha}^{\beta} V_m \sin wt \, d(wt) = \frac{V_m}{2\pi} (\cos\alpha - \cos\beta)$

$$I_0 = \frac{V_m}{2\pi R} (\cos\alpha - \cos\beta)$$

RMS load voltage  $V_{0r} = \left\{ \frac{1}{2\pi} \int_{\alpha}^{\beta} V_m^2 \sin^2 wt \, d(wt) \right\}^{1/2}$

$$= \frac{V_m}{2\sqrt{\pi}} \left[ (\beta - \alpha) - \frac{1}{2} \{ \sin 2\beta - \sin 2\alpha \} \right]^{1/2}$$

### Single phase half controlled converter with RLE load

The diode D2 and D4 conducts for the positive and negative half cycle of the input voltage waveform respectively. On the other hand T1 starts conduction when it is fired in the positive half cycle of the input voltage waveform and continuous conduction till T3 is fired in the negative half cycle. Fig. shows the circuit diagram and the waveforms of a single phase half controlled converter supplying an R – L – E load.

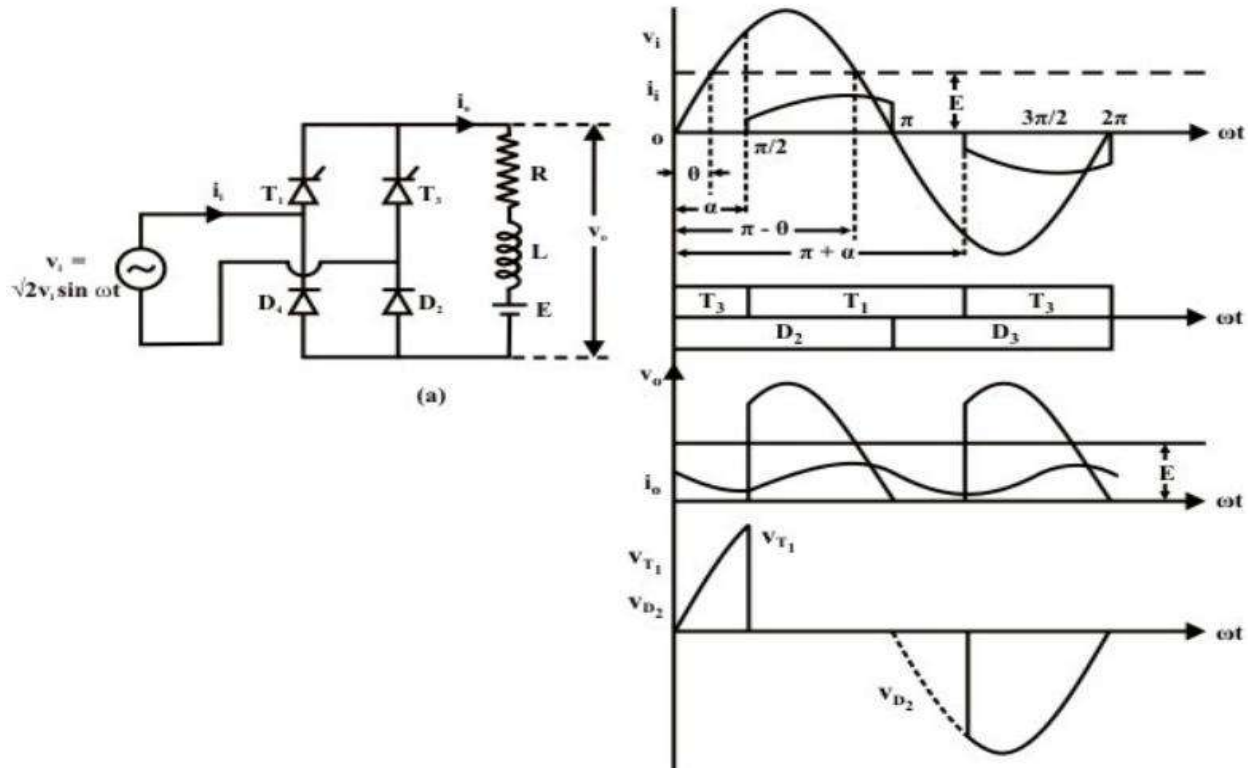


Figure: 2.5 single phase half controlled converter with RLE load

Referring to Fig T1 D2 starts conduction at  $\omega t = \alpha$ . Output voltage during this period becomes equal to  $v_i$ . At  $\omega t = \pi$  as  $v_i$  tends to go negative D4 is forward biased and the load current commutates from D2 to D4 and freewheels through D4 and T1. The output voltage remains clamped to zero till T3 is fired at  $\omega t = \pi + \alpha$ . The T3 D4 conduction mode continues upto  $\omega t = 2\pi$ . Where upon load current again free wheels through T3 and D2 while the load voltage is clamped to zero. From the discussion in the previous paragraph it can be concluded that the output voltage (hence the output current) is periodic over half the input cycle. Hence

$$V_{oav} = \frac{1}{\pi} \int_0^{\pi} v_o d\omega t = \frac{1}{\pi} \int_{\alpha}^{\pi} \sqrt{2}V_i \sin \omega t d\omega t = \frac{\sqrt{2}V_i}{\pi} (1 + \cos\alpha)$$

$$I_{ov} = \frac{V_{oav} - E}{R} = \frac{\sqrt{2}V_i}{\pi R} (1 + \cos\alpha - \pi \sin\theta)$$

**Single phase half controlled converter with RLE load and freewheeling diode**

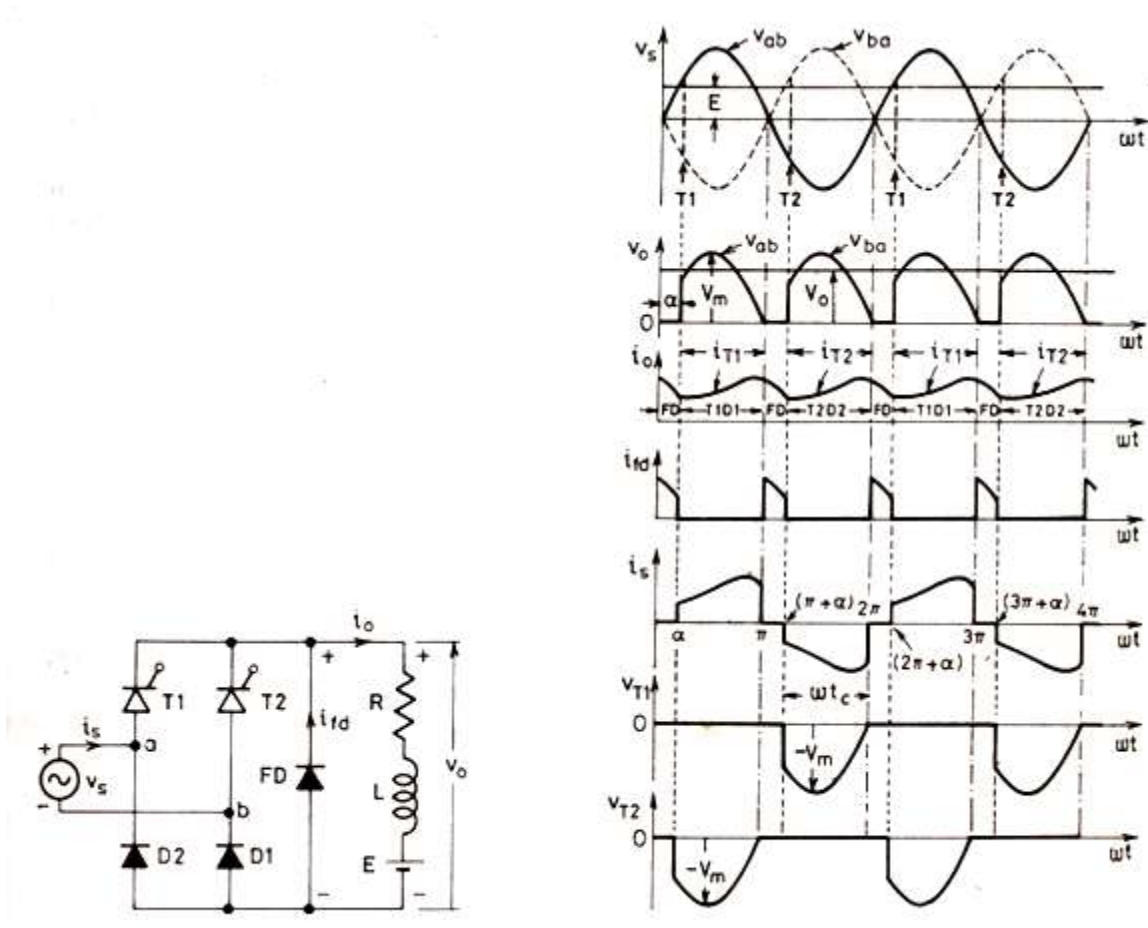


Figure: 2.6 single phase half controlled converter with RLE load and freewheeling diode

**Numerical problems**

1. A single phase 230V, 1 Kwheater is connected across 1 phase 230V, 50Hz supply through an SCR. For firing angle delay of  $45^0$  and  $90^0$ , calculate the power absorbed in the heater element.

Solution: Heater resistance  $R = 230^2/1000 \Omega$

The rms value of voltage is  $V_{or} = \frac{Vm}{2\sqrt{\pi}} \left[ (\pi - \alpha) + \frac{1}{2} \sin 2\alpha \right]^{1/2}$

$$= \frac{\sqrt{2} \times 230}{2\sqrt{\pi}} \left[ \left( \pi - \frac{\pi}{4} \right) + \frac{1}{2} \sin 90 \right]^{1/2} = 155.071V$$

Power absorbed by the heater element for  $\alpha = 45^\circ$  is

$$\frac{V_{or}^2}{R} = \left[ \frac{155.071}{230} \right]^2 \times 1000 = 454.57W$$

for  $\alpha = 90^\circ$  the rms voltage is

$$V_{or} = \frac{\sqrt{2} \times 230}{2\sqrt{\pi}} \left[ \left( \pi - \frac{\pi}{2} \right) + \frac{1}{2} \sin 180 \right]^{1/2} = 115V$$

Power absorbed by the heater element for  $\alpha = 90^\circ$  is

$$\frac{V_{or}^2}{R} = \left[ \frac{115}{230} \right]^2 \times 1000 = 250W$$

2. A resistive load of  $10\Omega$  is connected through a half-wave controlled rectifier circuit to 220V, 50 Hz, single phase source. Calculate the power delivered to the load for a firing angle of  $60^\circ$ . Find also the value of input power factor
3. A single phase semi converter delivers to RLE load with  $R=5\Omega$ ,  $L = 10mH$  and  $E = 80V$ . The source voltage is 230V, 50Hz. For continuous conduction, Find the average value of output current for firing angle =  $50^\circ$ .

### Single phase full wave controlled rectifier

Single Phase Full Wave Controlled Rectifier with 'R' load:

Figure below shows the Single phase Full Wave Controlled Rectifiers with R load


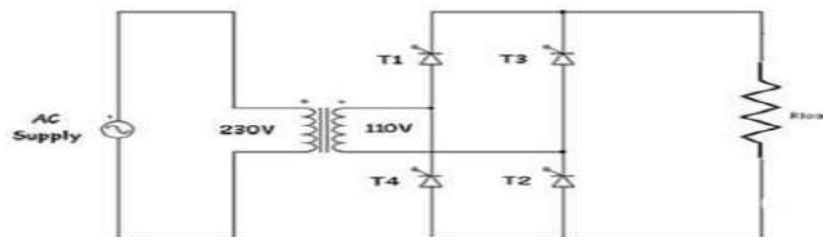


Figure: 2.7 single phase full converter circuit with R load

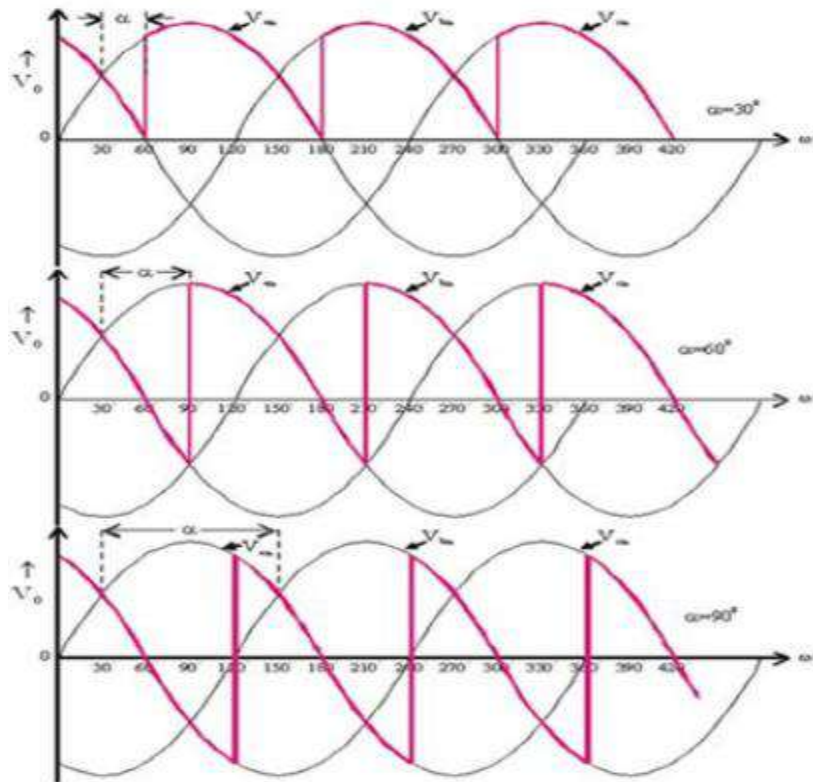

**Figure: 2.8 single phase full converter circuit with R load input and output waveforms**

- The single phase fully controlled rectifier allows conversion of single phase AC into DC. Normally this is used in various applications such as battery charging, speed control of DC motors and front end of UPS (Uninterruptible Power Supply) and SMPS (Switched Mode Power Supply).

- All four devices used are Thyristors. The turn-on instants of these devices are dependent on the firing signals that are given. Turn-off happens when the current through the device reaches zero and it is reverse biased at least for duration equal to the turn-off time of the device specified in the data sheet.

- In positive half cycle Thyristors T1 & T2 are fired at an angle  $\alpha$ .

- When T1 & T2 conducts

$$V_o = V_s$$

$$I_o = i_s = V_o / R = V_s / R$$

- In negative half cycle of input voltage, SCR's T3 & T4 are triggered at an angle of  $(\pi + \alpha)$

- Here output current & supply current are in opposite direction


$$\therefore i_s = -i_o$$

T3 & T4 becomes off at  $2\pi$ .


$$V_0 = \frac{1}{\pi} \int_{\alpha}^{\pi+\alpha} V_m \sin \omega t \, d(\omega t) = \frac{2V_m}{\pi} \cos \alpha$$

**Single Phase Full Wave Controlled Rectifier with 'RL' load:**

Figure below shows Single phase Full Wave Controlled Rectifiers with RL load.

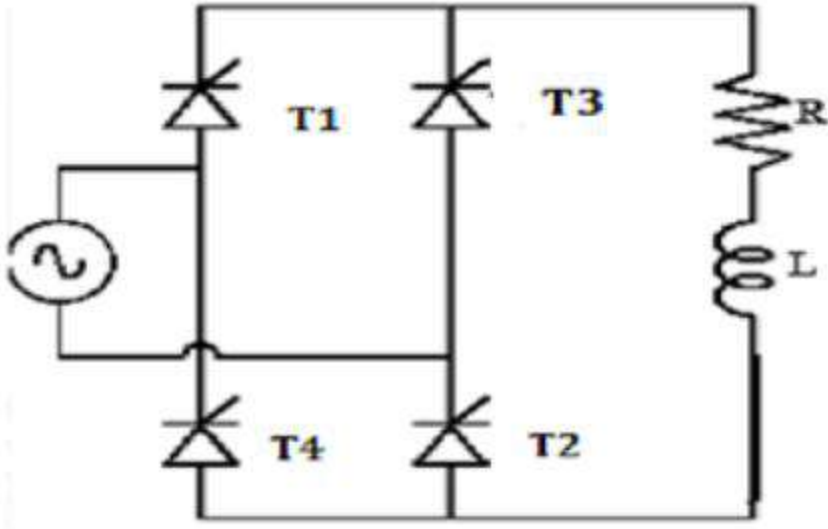

**Figure: 2.9 single phase full converter circuit with RL load**

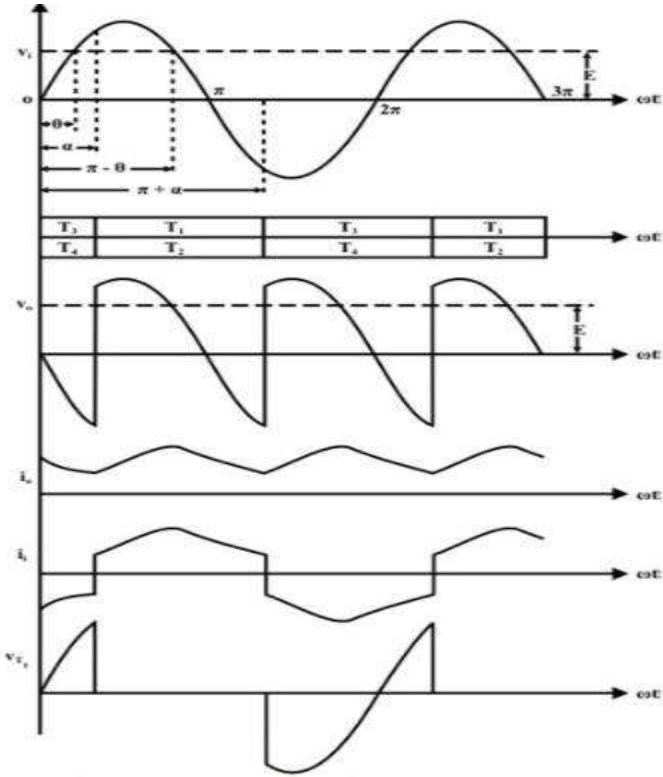

**Figure: 2.10 single phase full converter circuit with RL load input and output waveforms**

## Operation of this mode can be divided between four modes

### Mode 1 ( $\alpha$ to $\pi$ )

- In positive half cycle of applied ac signal, SCR's T1 & T2 are forward bias & can be turned on at an angle  $\alpha$ .
- Load voltage is equal to positive instantaneous ac supply voltage. The load current is positive, ripple free, constant and equal to  $I_o$ .
- Due to positive polarity of load voltage & load current, load inductance will store energy.

### Mode 2 ( $\pi$ to $\pi+\alpha$ )

- At  $\omega t = \pi$ , input supply is equal to zero & after  $\pi$  it becomes negative. But inductance opposes any change through it.
- In order to maintain a constant load current & also in same direction. A self induced emf appears across 'L' as shown.
- Due to this induced voltage, SCR's T1 & T2 are forward bias in spite the negative supply voltage.
- The load voltage is negative & equal to instantaneous ac supply voltage whereas load current is positive.
- Thus, load acts as source & stored energy in inductance is returned back to the ac supply.

### Mode 3 ( $\pi+\alpha$ to $2\pi$ )

- At  $\omega t = \pi + \alpha$  SCR's T3 & T4 are turned on & T1, T2 are reversed bias.
- Thus, process of conduction is transferred from T1, T2 to T3, T4.
- Load voltage again becomes positive & energy is stored in inductor
- T3, T4 conduct in negative half cycle from  $(\pi + \alpha)$  to  $2\pi$
- With positive load voltage & load current energy gets stored

### Mode 4 ( $2\pi$ to $2\pi+\alpha$ )

- At  $\omega t = 2\pi$ , input voltage passes through zero.
- Inductive load will try to oppose any change in current if in order to maintain load current constant & in the same direction.
- Induced emf is positive & maintains conducting SCR's T3 & T4 with reverse polarity also.



- Thus VL is negative & equal to instantaneous ac supply voltage. Whereas load current continues to be positive.
- Thus load acts as source & stored energy in inductance is returned back to ac supply
- At  $\omega t = \alpha$  or  $2\pi + \alpha$ , T3 & T4 are commutated and T1, T2 are turned on.

$$V_0 = \frac{1}{\pi} \int_{\alpha}^{\pi+\alpha} V_m \sin \omega t d(\omega t) = \frac{2V_m}{\pi} \cos \alpha$$

### Single phase fully controlled converters with RLE load

The circuit diagram of a full wave bridge rectifier using thyristors is shown in figure below. It consists of four SCRs which are connected between single phase AC supply and a load.

This rectifier produces controllable DC by varying conduction of all SCRs.

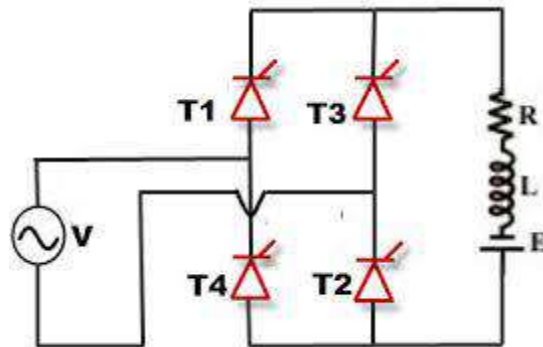


Figure: 2.11 single phase full converter circuit with RLE load

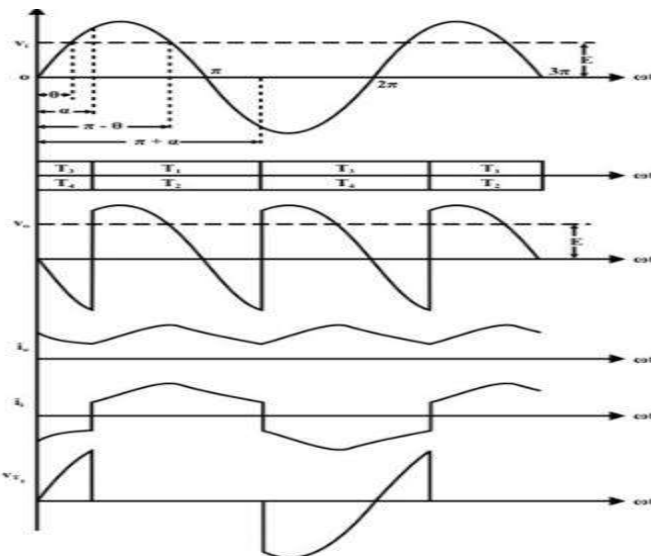


Figure: 2.12 single phase full converter circuit with RLE load input and output waveforms

In positive half-cycle of the input, Thyristors T1 and T2 are forward biased while T3 and T4 are reverse biased. Thyristors T1 and T2 are triggered simultaneously at some firing angle in the positive half cycle, and T3 and T4 are triggered in the negative half cycle.

The load current starts flowing through them when they are in conduction state. The load for this converter can be RL or RLE depending on the application.

By varying the conduction of each thyristor in the bridge, the average output of this converter gets controlled. The average value of the output voltage is twice that of half-wave rectifier.

The average output voltage is

$$V_0 = \frac{1}{\pi} \int_{\alpha}^{\pi+\alpha} V_m \sin wt \, d(wt) = \frac{2V_m}{\pi} \cos \alpha$$

### Line commutated converters

#### For single phase half wave converter

1. Average DC load voltage: ( $V_{\text{avg}}$ )

$$V_{\text{avg}} = V_0 = \frac{1}{T} \int_0^T V_m \sin wt \, d(wt) \quad \text{where T is time period}$$

$$V_{\text{avg}} = \frac{1}{2\pi} \left[ \int_{\alpha}^{\pi} V_m \sin wt \, d(wt) + \int_{\pi}^{2\pi+\alpha} 0 \, d(wt) \right]$$

$$= \frac{1}{2\pi} \left[ \int_{\alpha}^{\pi} V_m \sin wt \, d(wt) \right]$$

$$= \frac{V_m}{2\pi} [-\cos wt]_{\alpha}^{\pi}$$

$$= \frac{V_m}{2\pi} - [\cos \pi - \cos \alpha]$$

$$= \frac{V_m}{2\pi} [1 + \cos \alpha]$$

$$\text{If } \alpha = 0 \quad V_{\text{avg max}} = \frac{V_m}{\pi}$$

$$\text{If } \alpha = 180 \quad V_{\text{avg}} = 0$$

2. Average DC load current is given as

$$I_{\text{avg}} = \frac{V_{\text{avg}}}{R}$$

$$I_{\text{avg}} = \frac{Vm}{2\pi R} [1 + \cos\alpha]$$

### 3. RMS load voltage

$$V_{\text{rms}} = \left\{ \frac{1}{T} \int_0^T Vm^2 \sin^2 wt \, d(wt) \right\}^{1/2}$$

$$V_{\text{rms}} = \left\{ \frac{1}{2\pi} \int_{\alpha}^{\pi} Vm^2 \sin^2 wt \, d(wt) \right\}^{1/2}$$

$$V_{\text{rms}} = \frac{Vm}{2\sqrt{\pi}} \left[ (\pi - \alpha) + \frac{1}{2} \sin 2\alpha \right]^{1/2}$$

If  $\alpha = 0$   $V_{\text{rms}} = \frac{Vm}{2}$

If  $\alpha = 180$   $V_{\text{rms}} = 0$

The RMS voltage may be varied from 0 to  $\frac{Vm}{2}$  by varying  $\alpha$  from 180 to 0

### 4. Power delivered to the resistive load is given

$$\begin{aligned} P_L &= (\text{RMS load voltage})(\text{RMS load current}) \\ &= V_{\text{rms}} \times I_{\text{rms}} \\ &= \frac{V_{\text{rms}}^2}{R} = I_{\text{rms}}^2 X R \end{aligned}$$

### 5. Input volt amperes = (RMS source voltage)(RMS line current)

$$\begin{aligned} &= V_s I_{\text{rms}} \\ &= V_s \frac{\sqrt{2} V_s}{R 2 \sqrt{\pi}} \left[ (\pi - \alpha) + \frac{1}{2} \sin 2\alpha \right]^{1/2} \\ &= \frac{V_s^2}{\sqrt{2\pi} X R} \left[ (\pi - \alpha) + \frac{1}{2} \sin 2\alpha \right]^{1/2} \end{aligned}$$

### 6. Input power factor: It is defined as the ratio of total mean input power to the total rms input volt amperes

$$\begin{aligned} \text{Input power factor} &= \frac{\frac{\sqrt{2}V_s}{2\sqrt{\pi}}[(\pi-\alpha) + \frac{1}{2}\sin 2\alpha]^{1/2}}{V_s} \\ &= \frac{1}{\sqrt{2\pi}}[(\pi-\alpha) + \frac{1}{2}\sin 2\alpha]^{1/2} \end{aligned}$$

7. Form factor: Form factor is defined as the ratio of RMS voltage to the average DC voltage

$$\text{Form Factor} = \frac{V_{rms}}{V_{avg}}$$

8. Effective value of the AC component of the output voltage

$$V_{ac} = [V_{rms}^2 - V_{avg}^2]^{1/2}$$

9. Ripple factor ( $R_f$ )

It is defined as the ratio of AC component to the DC. Where ripple is the amount of AC component present in DC component

$$R_f = \frac{V_{ac}}{V_{avg}} = \frac{[V_{rms}^2 - V_{avg}^2]^{1/2}}{V_{avg}} = \left[ \left( \frac{V_{rms}}{V_{avg}} \right)^2 - 1 \right]^{1/2} = \sqrt{FF^2 - 1}$$

10. Transformer Utilization Factor (TUF):

It is defined as the ratio of output DC power to the volt ampere rating of the transformer

$$\text{TUF} = \frac{P_{dc}}{\text{VA rating of secondary winding of the transformer}}$$

11. Rectifier efficiency:

It is defined as the ratio of output DC power to the input ac power

$$\eta = \frac{V_{avg}I_{avg}}{V_{rms}I_{rms}}$$

12. Peak inverse voltage (PIV):

It is defined as the maximum voltage that an SCR can be subjected to in the reverse biased condition


In the case of Half wave rectifier it is  $V_m$

### Operation of three phase fully controlled rectifier with R and RL loads

**Three phase full converter** is a fully controlled bridge controlled rectifier using six thyristors connected in the form of a full wave bridge configuration. All the six thyristors are controlled switches which are turned on at a appropriate times by applying suitable gate trigger signals.

The **three phase full converter** is extensively used in industrial power applications upto about 120kW output power level, where two quadrant operations is required. The figure shows a **three phase full converter** with highly inductive load. This circuit is also known as three phase full wave bridge or as a six pulse converter.

The thyristors are triggered at an interval of  $(\pi/3)$  radians (i.e. at an interval of  $30^\circ$ ). The frequency of output ripple voltage is  $6f_s$  and the filtering requirement is less than that of **three phase semi and half wave converters**.

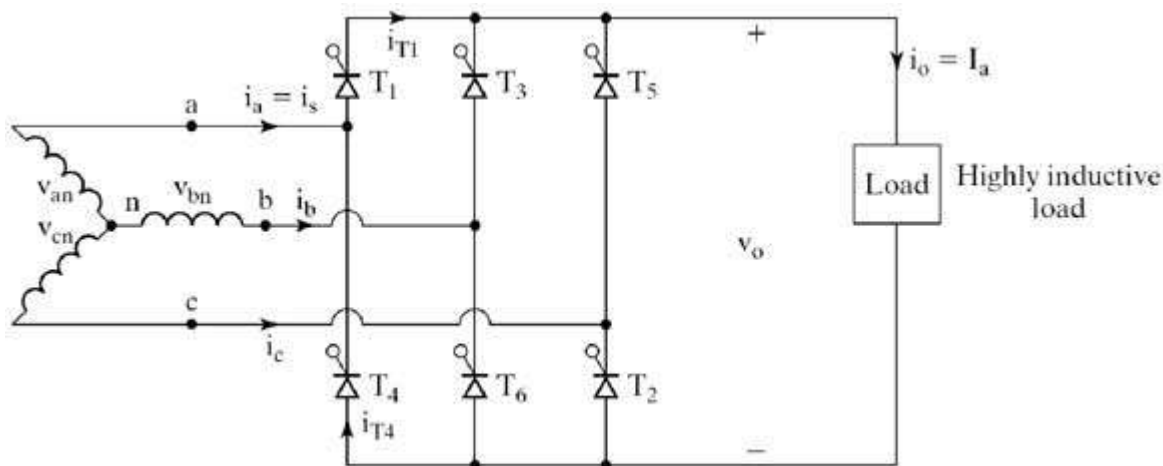

**Figure: 2.20 circuit diagram three phase fully controlled rectifier with R and RL load**

At  $\omega t = (\pi/6 + \alpha)$ , thyristor is already conducting when the thyristor is turned on by applying the gating signal to the gate of . During the time period  $\omega t = (\pi/6 + \alpha)$  to  $(\pi/2 + \alpha)$ , thyristors and conduct together and the line to line supply voltage appears across the load.

At  $\omega t = (\pi/2 + \alpha)$ , the thyristor  $T_2$  is triggered and  $T_6$  is reverse biased immediately and  $T_6$  turns off due to natural commutation. During the time period  $\omega t = (\pi/ + \alpha)$  to  $(5\pi/6 + \alpha)$ , thyristor  $T_1$  and  $T_2$  conduct together and the line to line supply voltage appears across the load.

The thyristors are numbered in the circuit diagram corresponding to the order in which they are triggered. The trigger sequence (firing sequence) of the thyristors is 12, 23, 34, 45, 56, 61, 12, 23, and so on. The figure shows the waveforms of three phase input supply voltages, output voltage, the thyristor current through  $T_1$  and  $T_4$ , the supply current through the line 'a'.

We define three line neutral voltages (3 phase voltages) as follows

$$V_{RN} = V_{an} = V_m \sin \omega t \text{ where } V_m \text{ is the maximum voltage}$$

$$V_{YN} = V_{bn} = V_m \sin \left( \omega t - \frac{2\pi}{3} \right)$$

$$V_{BN} = V_{cn} = V_m \sin \left( \omega t - \frac{4\pi}{3} \right)$$

The corresponding line to line voltages are

$$V_{RY} = V_{ab} = V_{an} - V_{bn} = \sqrt{3} V_m \sin \left( \omega t + \frac{\pi}{6} \right)$$

$$V_{YB} = V_{bc} = V_{bn} - V_{cn} = \sqrt{3} V_m \sin \left( \omega t - \frac{\pi}{2} \right)$$

$$V_{BR} = V_{ca} = V_{cn} - V_{an} = \sqrt{3} V_m \sin \left( \omega t + \frac{\pi}{2} \right)$$

To derive an expression for the average output voltage of **three phase full converter** with highly inductive load assuming continuous and constant load current

The output load voltage consists of 6 voltage pulses over a period of  $2\pi$  radians, hence the average output voltage is calculated as

$$V_{avg} = \frac{6}{2\pi} \int_{\frac{\pi}{6} + \alpha}^{\frac{\pi}{2} + \alpha} V_{od}(\omega t) d(\omega t)$$

$$V_o = V_{ab} = \sqrt{3} V_m \sin \left( \omega t + \frac{\pi}{6} \right)$$

$$V_{avg} = \frac{3}{\pi} \int_{\frac{\pi}{6} + \alpha}^{\frac{\pi}{2} + \alpha} \sqrt{3} V_m \sin \left( \omega t + \frac{\pi}{6} \right) d(\omega t)$$

$$= \frac{3\sqrt{3}V_m}{\pi} \cos \alpha$$

$$= \frac{3V_m}{\pi} \cos \alpha$$

The RMS value of the output voltage is found from

$$\begin{aligned}
 V_{\text{orms}} &= \left[ \frac{6}{2\pi} \int_{\frac{\pi}{6}+\alpha}^{\frac{\pi}{2}+\alpha} V_0^2 d(\omega t) \right]^{1/2} \\
 &= \left[ \frac{6}{2\pi} \int_{\frac{\pi}{6}+\alpha}^{\frac{\pi}{2}+\alpha} V_{ab}^2 d(\omega t) \right]^{1/2} \\
 &= \left[ \frac{3}{\pi} \int_{\frac{\pi}{6}+\alpha}^{\frac{\pi}{2}+\alpha} 3 V_m^2 \sin^2 \left( \omega t + \frac{\pi}{6} \right) d(\omega t) \right]^{1/2} \\
 &= \sqrt{3} V_m \left( \frac{1}{2} + \frac{3\sqrt{3}}{4\pi} \cos 2\alpha \right)^{1/2}
 \end{aligned}$$


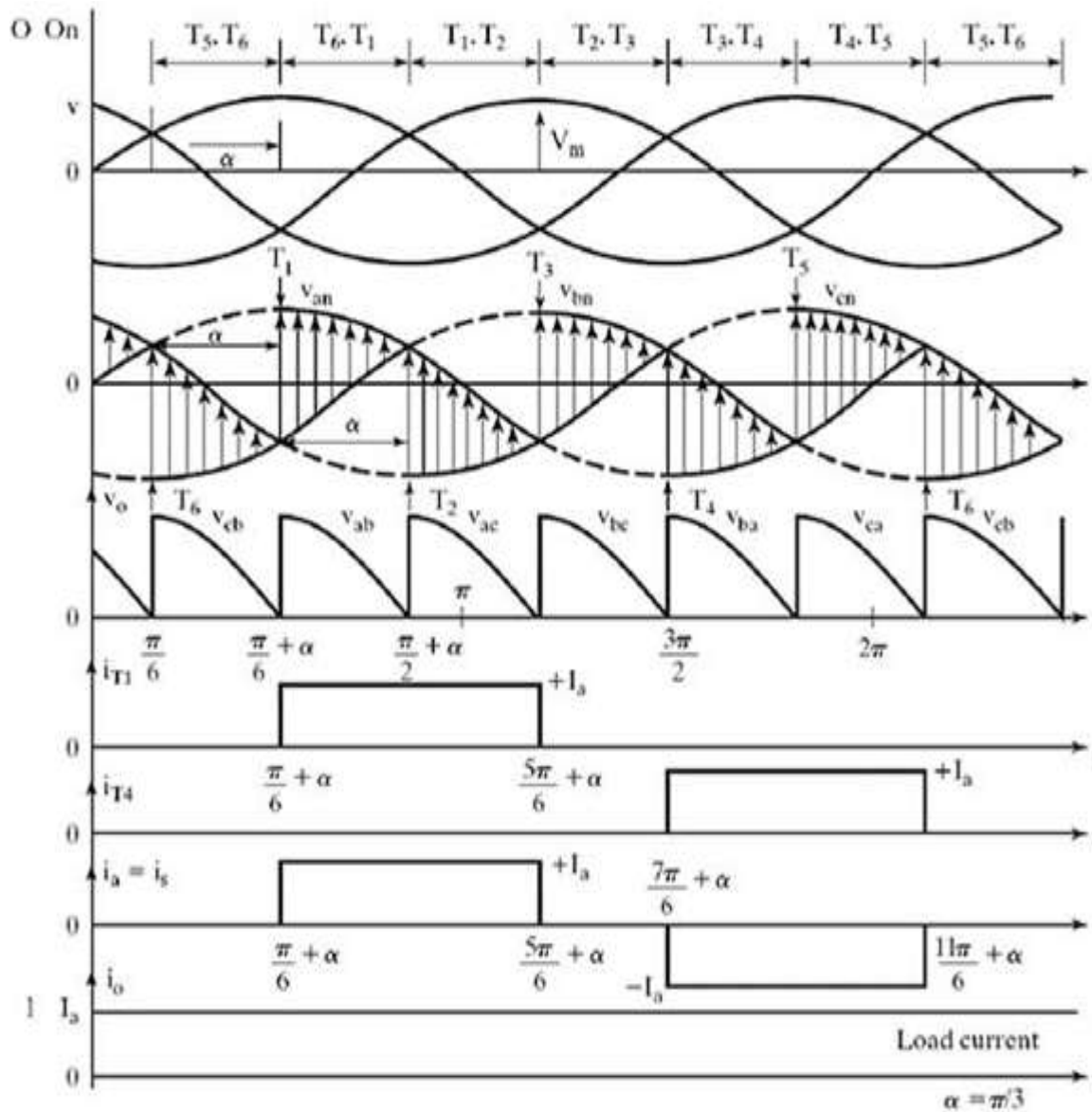


Figure: 2.21 Input and output waveforms of three phase fully controlled rectifier

### Operation of three phase half wave rectifier with RLE loads

A three phase fully controlled converter is obtained by replacing all the six diodes of an uncontrolled converter by six thyristors as shown in Figure

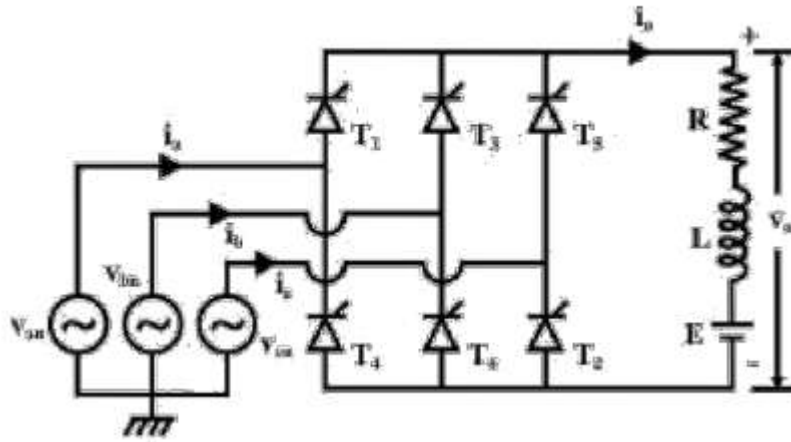

**Figure: 2.22 circuit diagram of three phase fully controlled rectifier with RLE load**

For any current to flow in the load at least one device from the top group ( $T_1, T_3, T_5$ ) and one from the bottom group ( $T_2, T_4, T_6$ ) must conduct. It can be argued as in the case of an uncontrolled converter only one device from these two groups will conduct.

Then from symmetry consideration it can be argued that each thyristor conducts for  $120^\circ$  of the input cycle. Now the thyristors are fired in the sequence  $T_1 \rightarrow T_2 \rightarrow T_3 \rightarrow T_4 \rightarrow T_5 \rightarrow T_6 \rightarrow T_1$  with  $60^\circ$  interval between each firing. Therefore thyristors on the same phase leg are fired at an interval of  $180^\circ$  and hence can not conduct simultaneously. This leaves only six possible conduction mode for the converter in the continuous conduction mode of operation. These are  $T_1T_2, T_2T_3, T_3T_4, T_4T_5, T_5T_6, T_6T_1$ . Each conduction mode is of  $60^\circ$  duration and appears in the sequence mentioned. Each of these line voltages can be associated with the firing of a thyristor with the help of the conduction table-1. For example the thyristor  $T_1$  is fired at the end

of  $T_5 T_6$  conduction interval. During this period the voltage across  $T_1$  was  $v_{ac}$ . Therefore  $T_1$  is fired  $\alpha$  angle after the positive going zero crossing of  $v_{ac}$ . similar observation can be made about other thyristors.

Fig. 2.23 shows the waveforms of different variables. To arrive at the waveforms it is necessary to draw the conduction diagram which shows the interval of conduction for each thyristor and can be drawn with the help of the phasor diagram of fig. 2.22. If the converter firing angle is  $\alpha$  each thyristor is fired " $\alpha$ "



for  $\mu \leq 60^\circ$ . It can be shown that for this condition to be satisfied

$$I_0 \leq \frac{V_L}{\sqrt{2}\omega L} \cos\left(\alpha - \frac{\pi}{3}\right)$$

To calculate the dc voltage

For  $\alpha \leq \omega t \leq \alpha + \mu$

$$v_0 = v_a - v_b + L \frac{di_b}{dt} = \frac{3}{2} v_a$$

for  $\alpha + \mu \leq \omega t \leq \alpha + \frac{\pi}{3}$   $v_0 = v_{ac}$

$$\therefore V_0 = \frac{3}{\pi} \left[ \int_{\alpha}^{\alpha+\mu} \frac{3}{2} v_a d\omega t + \int_{\alpha+\mu}^{\alpha+\frac{\pi}{3}} v_{ac} d\omega t \right]$$

$$= \frac{3}{\pi} \left[ \int_{\alpha}^{\alpha+\mu} \left( v_{ac} + \frac{3}{2} v_a - v_{ac} \right) + \int_{\alpha+\mu}^{\alpha+\frac{\pi}{3}} v_{ac} d\omega t \right]$$

$$= \frac{3}{\pi} \left[ \int_{\alpha}^{\alpha+\frac{\pi}{3}} v_{ac} d\omega t + \int_{\alpha}^{\alpha+\mu} \left( \frac{v_a}{2} + v_0 \right) d\omega t \right]$$

$$= \frac{3\sqrt{2}}{\pi} V_L \cos\alpha - \frac{3}{2\pi} \int_{\alpha}^{\alpha+\mu} v_{bc} d\omega t$$


or 
$$V_0 = \frac{3\sqrt{2}}{\pi} V_L \cos\alpha - \frac{3\sqrt{2}V_L}{2\pi} \int_{\alpha}^{\alpha+\mu} \sin\omega t d\omega t$$

$$= \frac{3\sqrt{2}}{\pi} V_L \cos\alpha - \frac{3\sqrt{2}V_L}{2\pi} [\cos\alpha - \cos(\alpha + \mu)]$$

$$V_0 = \frac{3\sqrt{2}}{\pi} V_L \cos\alpha - \frac{3}{\pi} \omega L I_0$$

### Introduction to dual converters

*Dual converter*, the name itself says two converters. It is really an electronic converter or circuit which comprises of two converters. One will perform as rectifier and the other will perform as inverter. Therefore, we can say that double processes will occur at a moment. Here, two full converters are arranged in anti-parallel pattern and linked to the same dc load. These converters can provide four quadrant operations. The basic block diagram is shown below

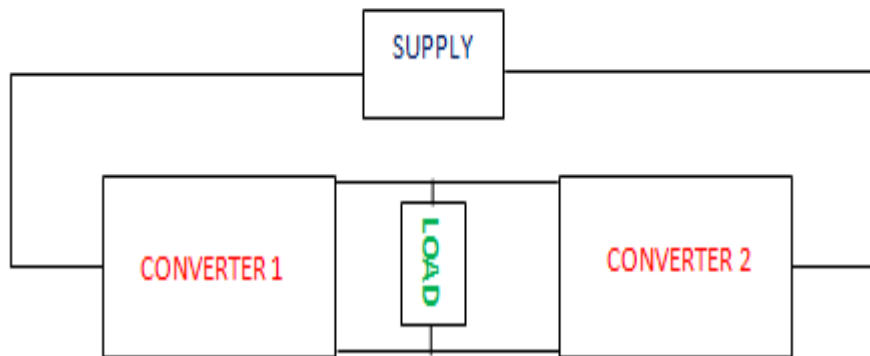

**Figure: 2.28 Block diagram of dual converter**

### **Modes of Operation of Dual Converter**

There are two functional modes: Non-circulating current mode and circulating mode.

#### **Non Circulating Current Mode**

- One converter will perform at a time. So there is no circulating current between the converters.
- During the converter 1 operation, firing angle ( $\alpha_1$ ) will be  $0 < \alpha_1 < 90^\circ$ ;  $V_{dc}$  and  $I_{dc}$  are positive.
- During the converter 2 operation, firing angle ( $\alpha_2$ ) will be  $0 < \alpha_2 < 90^\circ$ ;  $V_{dc}$  and  $I_{dc}$  are negative.

#### **Circulating Current Mode**

- Two converters will be in the ON condition at the same time. So circulating current is present.
- The firing angles are adjusted such that firing angle of converter 1 ( $\alpha_1$ ) + firing angle of converter 2 ( $\alpha_2$ ) =  $180^\circ$ .
- Converter 1 performs as a controlled rectifier when firing angle be  $0 < \alpha_1 < 90^\circ$  and Converter 2 performs as an inverter when the firing angle be  $90^\circ < \alpha_2 < 180^\circ$ . In this condition,  $V_{dc}$  and  $I_{dc}$  are positive.
  - Converter 1 performs as an inverter when firing angle be  $90^\circ < \alpha_1 < 180^\circ$  and Converter 2 performs as a controlled rectifier when the firing angle be  $0 < \alpha_2 < 90^\circ$  In this condition,  $V_{dc}$  and  $I_{dc}$  are negative.
- The four quadrant operation is shown below

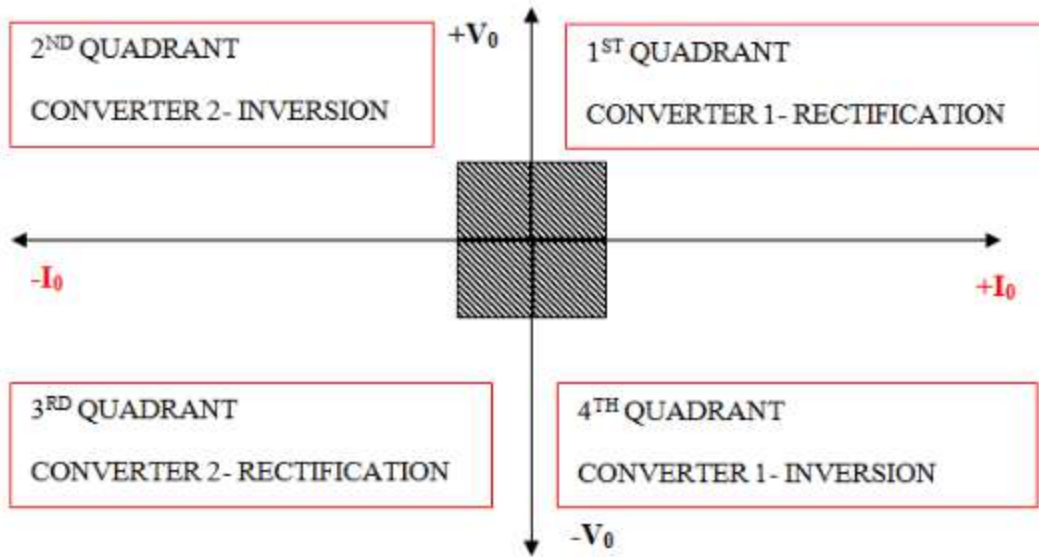


Figure: 2.29 Four quadrant operations of dual converter

### Ideal Dual Converter

The term ‘ideal’ refers to the ripple free output voltage. For the purpose of unidirectional flow of DC current, two diodes ( $D_1$  and  $D_2$ ) are incorporated between the converters. However, the direction of current can be in any way. The average output voltage of the converter 1 is  $V_{o1}$  and converter 2 is  $V_{o2}$ . To make the output voltage of the two converters in same polarity and magnitude, the firing angles of the Thyristors have to be controlled.

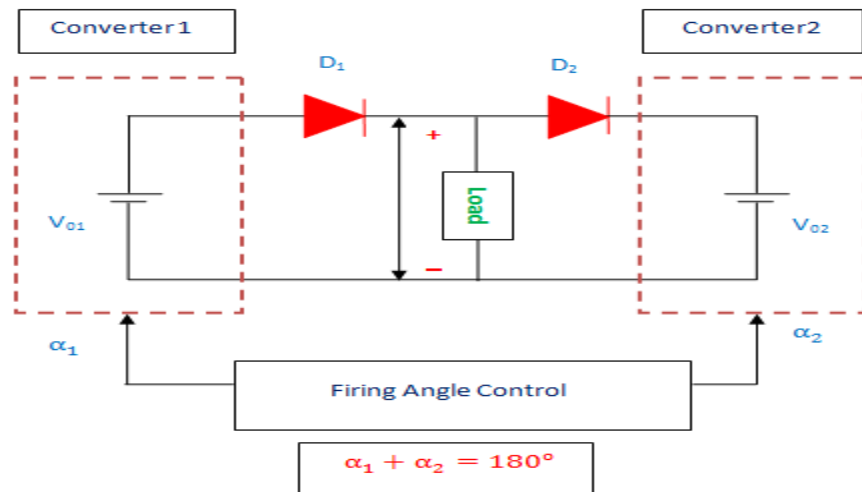


Figure: 2.30 Ideal dual converter

## Single Phase Dual Converter

The source of this type of converter will be single-phase supply. Consider, the converter is in non-circulating mode of operation. The input is given to the converter 1 which converts the AC to DC by the method of rectification. It is then given to the load after filtering. Then, this DC is provided to the converter 2 as input. This converter performs as inverter and converts this DC to AC. Thus, we get AC as output. The circuit diagram is shown below.

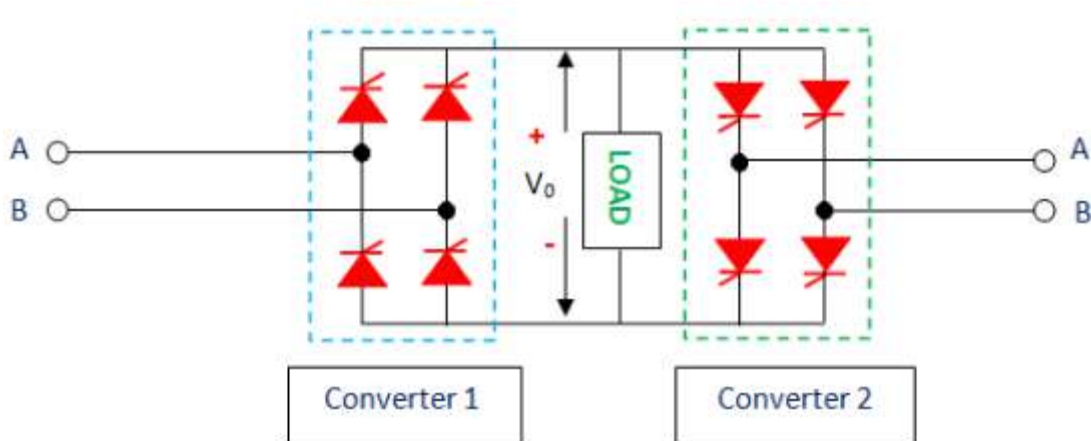


Figure: 2.31 Single phase Dual converter

$$\text{Average output voltage of Single-phase converter} = \frac{2V_m \cos \alpha}{\pi}$$

$$\text{Average output voltage of Three-phase converter} = \frac{3V_{m1} \cos \alpha}{\pi}$$

$$\text{For converter 1, the average output voltage, } V_{01} = V_{max} \cos \alpha_1$$

$$\text{For converter 2, the average output voltage, } V_{02} = V_{max} \cos \alpha_2$$

$$V_0 = V_{01} = -V_{02}$$

$$V_{max} \cos \alpha_1 = -V_{max} \cos \alpha_2$$

$$\cos \alpha_1 = \cos(180^\circ - \alpha_2) \text{ or } \cos \alpha_2 = \cos(180^\circ + \alpha_2)$$

$$\text{Output voltage, } \alpha_1 + \alpha_2 = 180^\circ \text{ And } \alpha_1 - \alpha_2 = 180^\circ$$

The firing angle can never be greater than  $180^\circ$ . So,  $\alpha_1 + \alpha_2 = 180^\circ$

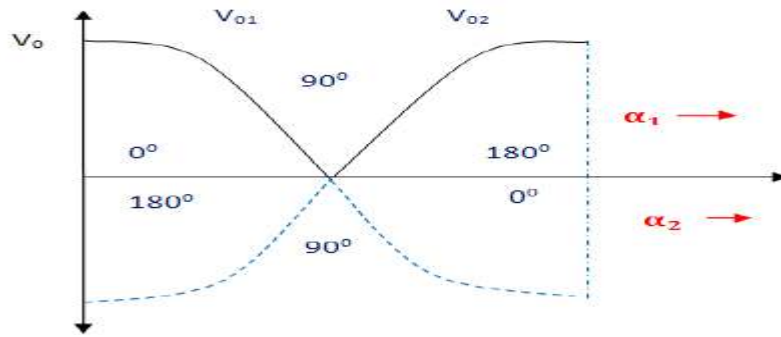


Figure: 2.32 output voltage variation with firing angle

### Three Phase Dual Converter

Here, three-phase rectifier and three-phase inverter are used. The processes are similar to single-phase dual converter. The three-phase rectifier will do the conversion of the three-phase AC supply to the DC. This DC is filtered and given to the input of the second converter. It will do the DC to AC conversion and the output that we get is the three-phase AC. Applications where the output is up to 2 megawatts. The circuit is shown below.


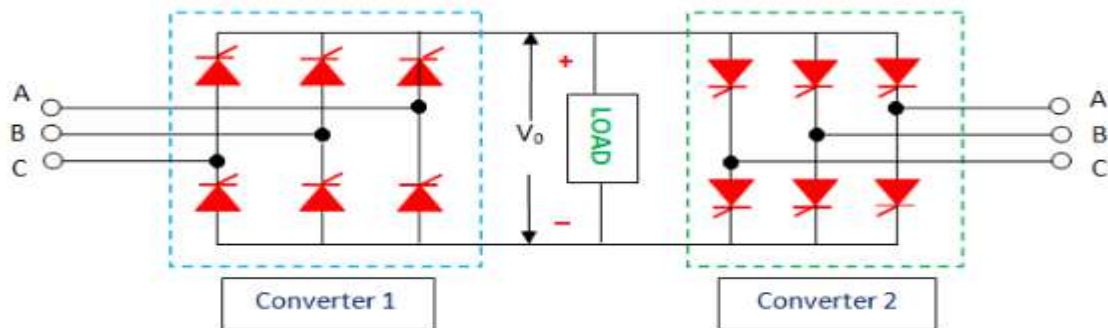


Figure: 2.33 Three phase dual converter

### Application of Dual Converter

- Direction and Speed control of DC motors.
- Applicable wherever the reversible DC is required.
- Industrial variable speed DC drives.
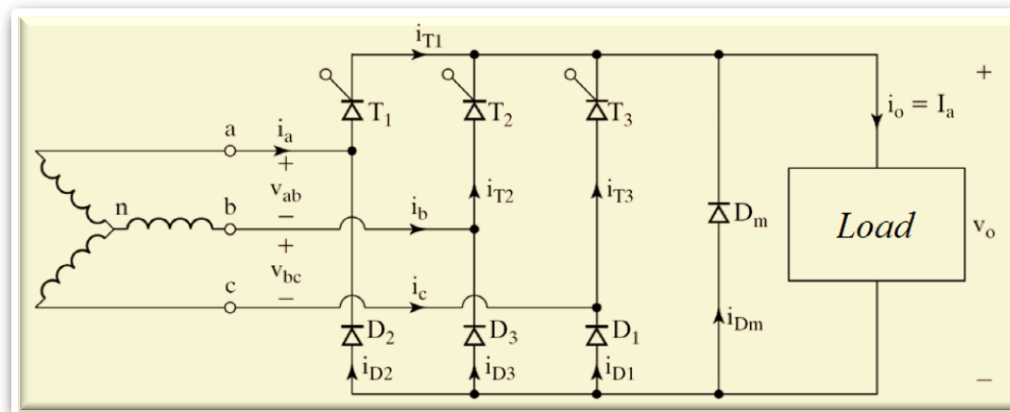
# Three Phase Full Wave Half Controlled Rectifiers



- **3-phase semi-converters are three phase half controlled bridge controlled rectifiers which employ three thyristors and three diodes connected in the form of a bridge configuration. Three thyristors are controlled switches which are turned on at appropriate times by applying appropriate gating signals. The three diodes conduct when they are forward biased by the corresponding phase supply voltages.**
- **The power factor of 3-phase semi-converter decreases as the trigger angle  $\alpha$  increases. The power factor of a 3-phase semi-converter is better than three phase half wave converter.**

# Three Phase Full Wave Half Controlled Rectifiers

- Thyristor  $T_1$  is forward biased when the phase supply voltage  $v_{an}$  is positive and greater than the other phase voltages  $v_{bn}$  and  $v_{cn}$ . The diode  $D_1$  is forward biased when the phase supply voltage  $v_{cn}$  is more negative than the other phase supply voltages.
- Thyristor  $T_2$  is forward biased when the phase supply voltage  $v_{bn}$  is positive and greater than the other phase voltages. Diode  $D_2$  is forward biased when the phase supply voltage  $v_{an}$  is more negative than the other phase supply voltages.
- Thyristor  $T_3$  is forward biased when the phase supply voltage  $v_{cn}$  is positive and greater than the other phase voltages. Diode  $D_3$  is forward biased when the phase supply voltage  $v_{bn}$  is more negative than the other phase supply voltages.
- The frequency of the output supply waveform is  $3f_s$ , where  $f_s$  is the input ac supply frequency. The trigger angle  $\alpha$  can be varied from  $0$  to  $180^\circ$ .

# Three Phase Full Wave Half Controlled Rectifiers


For  $\alpha > 60^\circ$

- During the time period  $\pi/6 \leq \omega t \leq 7\pi/6$  (i.e.  $30^\circ \leq \omega t \leq 210^\circ$ ) thyristor  $T_1$  is forward biased. If  $T_1$  is triggered at  $\omega t = \pi/6 + \alpha$ ,  $T_1$  and  $D_1$  conduct together and the line to line supply voltage  $v_{ac}$  appears across the load. At  $\omega t = 7\pi/6$ ,  $v_{ac}$  starts to become negative and the free wheeling diode  $D_m$  turns on and conducts. The load current continues to flow through the free wheeling diode  $D_m$  and thyristor  $T_1$  and diode  $D_1$  are turned off.
- If the free wheeling diode  $D_m$  is not connected across the load, then  $T_1$  would continue to conduct until the thyristor  $T_2$  is triggered at  $\omega t = 5\pi/6 + \alpha$  and the free wheeling action is accomplished through  $T_1$  and  $D_2$ , when  $D_2$  turns on as soon as  $v_{an}$  becomes more negative at  $\omega t = 7\pi/6$ .



# Three Phase Full Wave Half Controlled Rectifiers

Waveforms for  $\alpha=90^\circ$

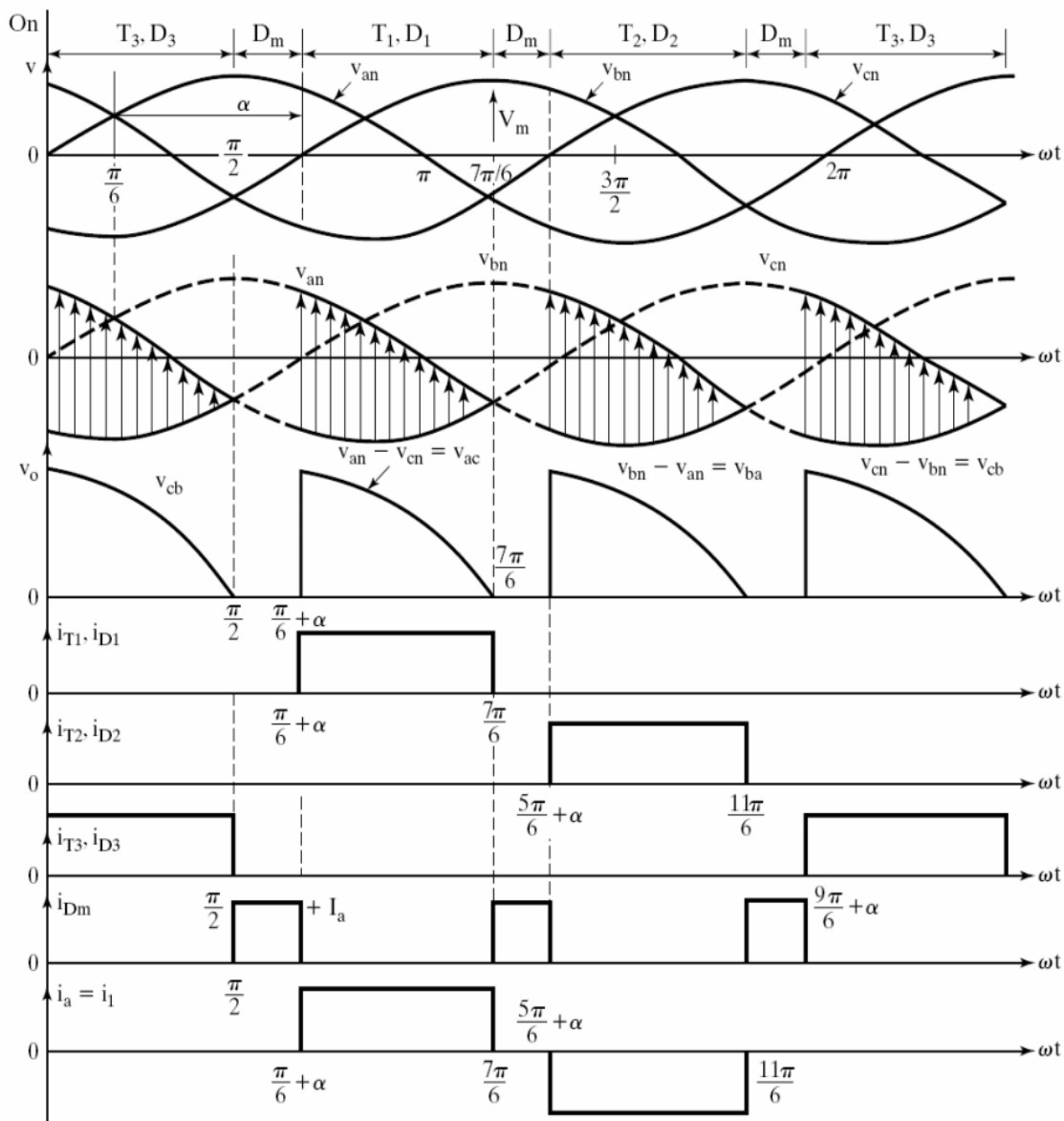


Dr. Firas

# Three Phase Full Wave Half Controlled Rectifiers

For  $\alpha < 60^\circ$

If the trigger angle  $\alpha \leq \pi/3$  each thyristor conducts for  $2\pi/3$  and the free wheeling diode  $D_m$  does not conduct.

Waveforms for  $\alpha = 30^\circ$

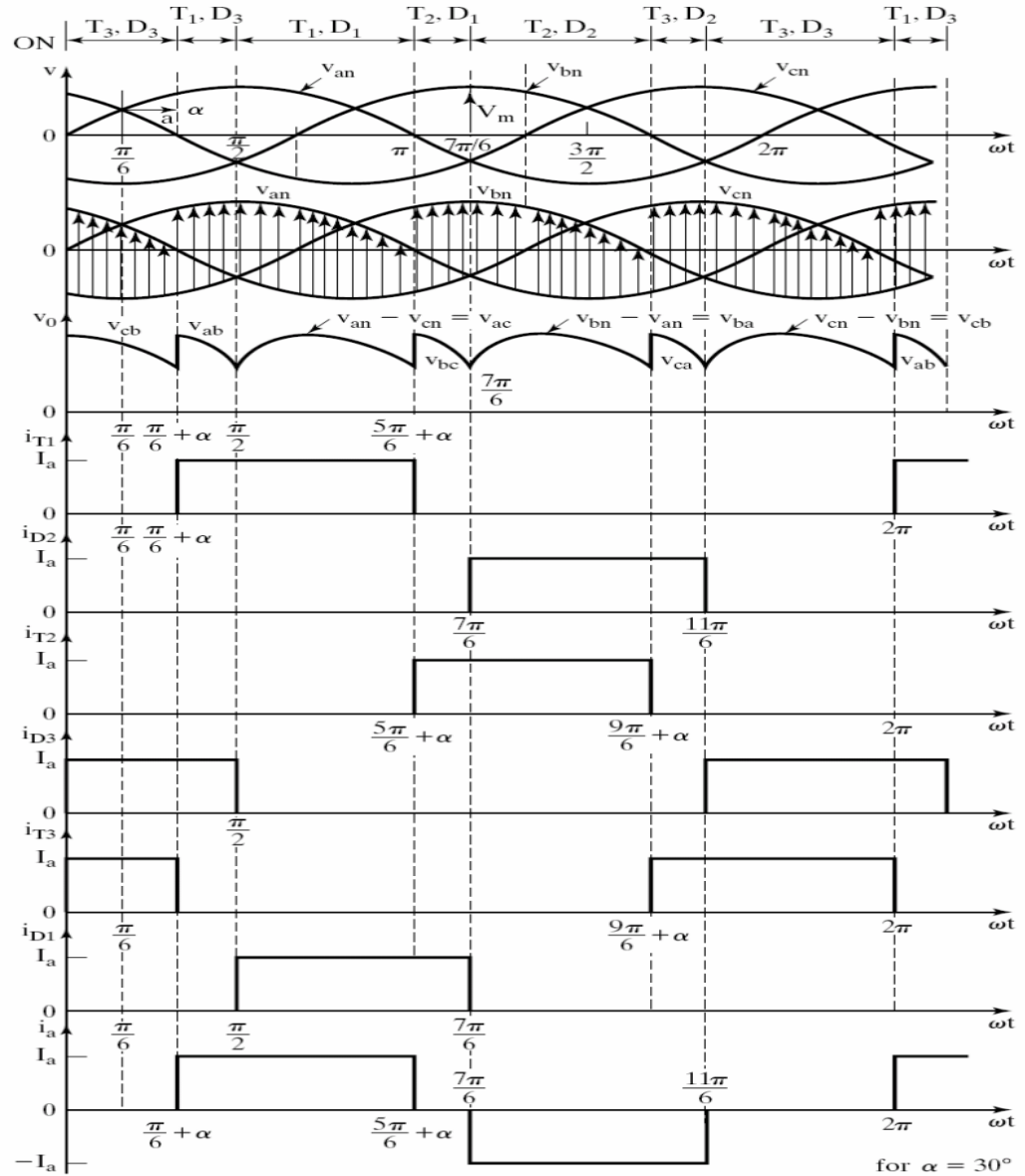


# Three Phase Full Wave Half Controlled Rectifiers

For  $\alpha < 60^\circ$

If the trigger angle  $\alpha \leq \pi/3$  each thyristor conducts for  $2\pi/3$  and the free wheeling diode  $D_m$  does not conduct.

Waveforms for  $\alpha = 30^\circ$

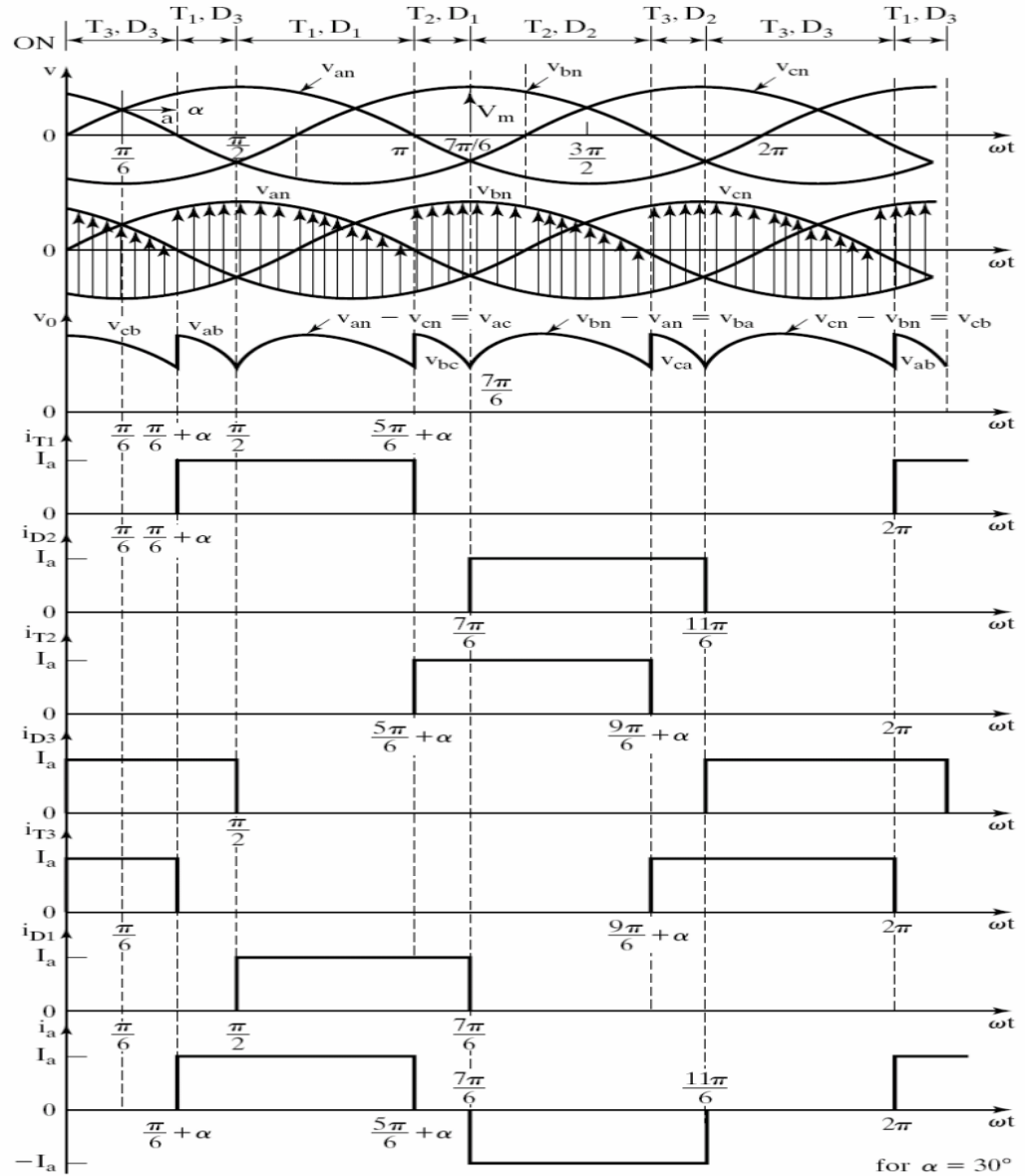

# Three Phase Full Wave Half Controlled Rectifiers

Let  $V_{an} = V_m \sin \omega t$        $V_{bn} = V_m \sin(\omega t - 2\pi/3)$        $V_{cn} = V_m \sin(\omega t - 4\pi/3)$

**For  $\alpha > 60^\circ$  and Discontinuous Output Voltage**

$$V_o = V_{ac} = \sqrt{3}V_m \sin\left(\omega t - \frac{\pi}{6}\right)$$

The dc component of the output voltage and current can be found as

$$V_{dc} = \frac{3}{2\pi} \int_{\frac{\pi}{6}+\alpha}^{\frac{7\pi}{6}} \sqrt{3}V_m \sin\left(\omega t - \frac{\pi}{6}\right) d\omega t = \frac{3\sqrt{3}V_m}{2\pi} (1 + \cos \alpha)$$

$$I_{dc} = \frac{V_{dc}}{R} = \frac{3\sqrt{3}V_m}{2\pi R} (1 + \cos \alpha)$$

The *rms* component of the output voltage and current waveforms are determined from

$$V_{rms} = \sqrt{\frac{3}{2\pi} \int_{\frac{\pi}{6}+\alpha}^{\frac{7\pi}{6}} \left(\sqrt{3}V_m \sin\left(\omega t - \frac{\pi}{6}\right)\right)^2 d\omega t} = \frac{3V_m}{2} \sqrt{1 - \frac{\alpha}{\pi} + \frac{\sin 2\alpha}{2\pi}}$$

$$I_{rms} = \frac{V_{rms}}{\sqrt{R^2 + (\omega L)^2}} = \frac{3V_m}{2\sqrt{R^2 + (\omega L)^2}} \sqrt{1 - \frac{\alpha}{\pi} + \frac{\sin 2\alpha}{2\pi}}$$

# Three Phase Full Wave Half Controlled Rectifiers

For  $\alpha \leq 60^\circ$  and Continuous Output Voltage

$$V_o = V_{ab} = \sqrt{3}V_m \sin\left(\omega t + \frac{\pi}{6}\right)$$

The dc component of the output voltage and current can be found as

$$V_{dc} = \frac{3}{2\pi} \int_{\frac{\pi}{6} + \alpha}^{\frac{\pi}{2}} \sqrt{3}V_m \sin\left(\omega t + \frac{\pi}{6}\right) d\omega t = \frac{3\sqrt{3}V_m}{2\pi} (1 + \cos \alpha)$$

$$I_{dc} = \frac{V_{dc}}{R} = \frac{3\sqrt{3}V_m}{2\pi R} (1 + \cos \alpha)$$


The *rms* component of the output voltage and current waveforms are determined from

$$V_{rms} = \sqrt{\frac{3}{2\pi} \left[ \int_{\frac{\pi}{6} + \alpha}^{\frac{\pi}{2}} (V_{ab})^2 d\omega t + \int_{\frac{\pi}{6}}^{\frac{5\pi}{6}} (V_{ac})^2 d\omega t \right]} = \frac{3V_m}{2} \sqrt{\frac{2}{3} + \frac{\sqrt{3}(\cos \alpha)^2}{\pi}}$$

$$I_{rms} = \frac{V_{rms}}{\sqrt{R^2 + (\omega L)^2}} = \frac{3V_m}{2\sqrt{R^2 + (\omega L)^2}} \sqrt{\frac{2}{3} + \frac{\sqrt{3}(\cos \alpha)^2}{\pi}}$$

switched mode regulators & DC-DC converters  
classified into 2 types.

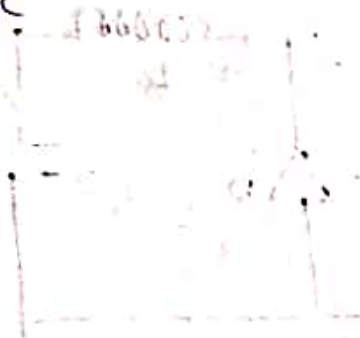1. NON isolated
2. Isolated  $\rightarrow$ 
  - 1) Half bridge
  - 2) full-bridge
  - 3) fly Back
  - 4) Push pull
  - 5) forward.




NON-isolated:

1. Buck converter. ( $V_o < V_s$ ) | step down
2. Boost converter ( $V_o > V_s$ ) | step down up
3. Buck-Boost converter step up & down.
4. CUK
5. SEPIC

Assumptions:

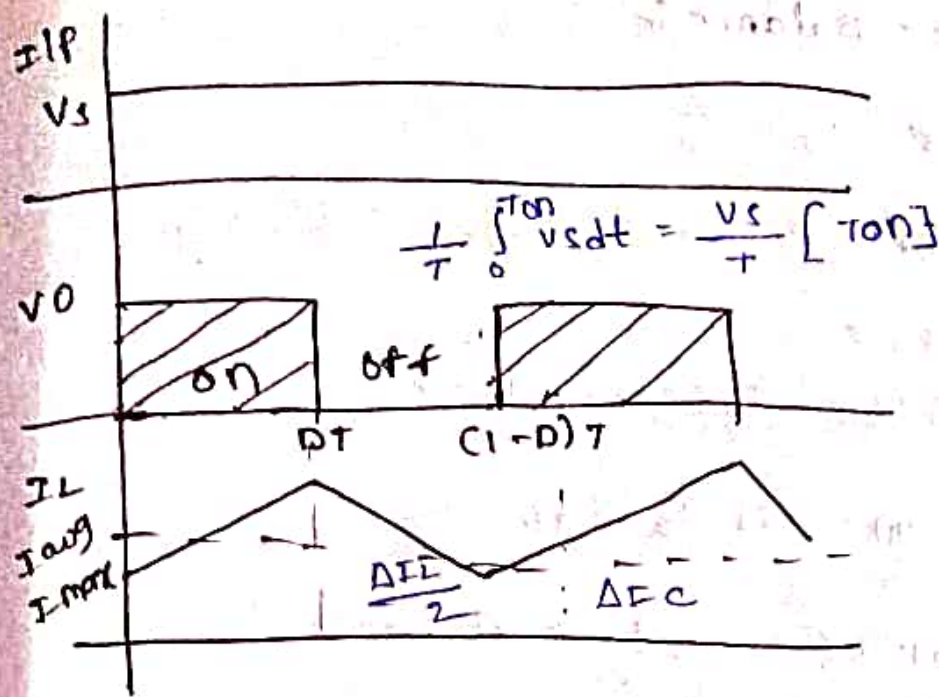1. Inductor current is continuous.
2. The inductance is large enough to minimize current ripple.
3. The capacitor is very large so that the voltage is held constant.



switch off condition

$L^{(-)}$  - load - Diode -  $L^{(+)}$

$$T_{off} = T - T_{on}$$

$$V_L(off) = -V_o$$

$$I_C(off) = I_L - I_o$$

\*\*

Volt sec Balance

$$V_L(on) T_{on} + V_L(off) T_{off} = 0$$

$$(V_s - V_o) DT + (-V_o) (1-D) T = 0$$

$$V_s DT - V_o DT - V_o T + V_o DT = 0$$

$$V_s DT - V_o T = 0$$

$$V_s D T = V_o T$$

$$V_s D = V_o$$

$$\Delta I_L = \frac{D(1-D)V_S}{fL}$$

Max value of inductor current :

$$= I_L + \frac{\Delta I_L}{2}$$

$$= I_0 + \frac{\Delta I_L}{2}$$

$$I_{L \max} = I_0 + \frac{D(1-D)V_S}{2fL}$$

$$I_{L \min} = I_L - \frac{\Delta I_L}{2}$$

$$= I_0 - \frac{D(1-D)V_S}{2fL}$$


Source current :

$$P_{in} = P_{out}$$

$$V_S I_S = V_0 I_0$$

$$I_S = \frac{V_0 I_0}{V_S}$$

Switch current :

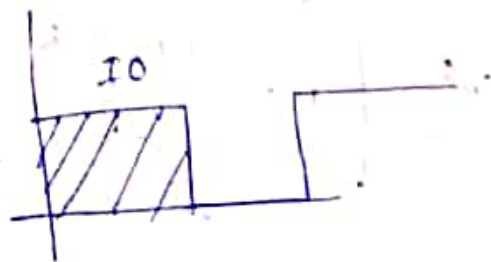


$$I_{sw}(\text{avg}) = I_0 \frac{DT}{T} = I_0 D$$

$$I_{sw}(\text{rms}) = I_0 \sqrt{\frac{DT}{T}}$$

$$= I_0 \sqrt{D}$$



Diode current

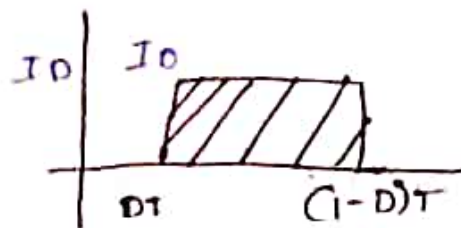

$$I_D = I_0 \frac{(1-D)T}{T}$$

$$I_D = I_0 (1-D)$$

(Avg)

$$I_{D \text{ rms}} = I_0 \sqrt{\frac{(1-D)T}{T}}$$

$$* I_{D \text{ rms}} = I_0 \sqrt{(1-D)}$$

Critical value of inductance

$$I_L(\text{min}) = 0$$

$$I_L - \frac{\Delta I_L}{2} = 0$$

$$I_0 - \frac{\Delta I_L}{2} = 0$$

$$I_0 = \frac{\Delta I_L}{2}$$

$$\frac{V_0}{R} = \frac{\Delta I_L}{2}$$

$$\frac{\phi V_s}{R} = \frac{\phi (1-D) V_s}{2 f L}$$

$$\frac{1}{R} = \frac{(1-D)}{2 f L C}$$

$$R = \frac{2 f L C}{(1-D)}$$

$$L C = \frac{(1-D) R}{2 f}$$

$\Delta V_C$  or  $\Delta V_O$

$Q = CV$

$\Delta Q = C \Delta V$

$\Delta V = \frac{\Delta Q}{C}$

$\Delta V = \frac{\Delta I L}{8 f C}$

$\Delta V = \frac{DC(1-D)V_S}{8 f C L}$

critical value of capacitance

$V_C \min = 0$

$V_C - \frac{\Delta V_C}{2} = 0$

$V_C = \frac{1}{2} [\Delta V_C]$


$V_C = \frac{1}{2} \left[ \frac{\Delta I L}{8 f C} \right]$

$= \frac{1}{2} \left[ \frac{DC(1-D)V_S}{8 f^2 L C} \right]$

$D V_S = \frac{1}{2} \left[ \frac{DC(1-D)V_S}{8 f^2 L C} \right]$

$C = \frac{(1-D)}{16 f^2 L}$

Discontinuous Current mode

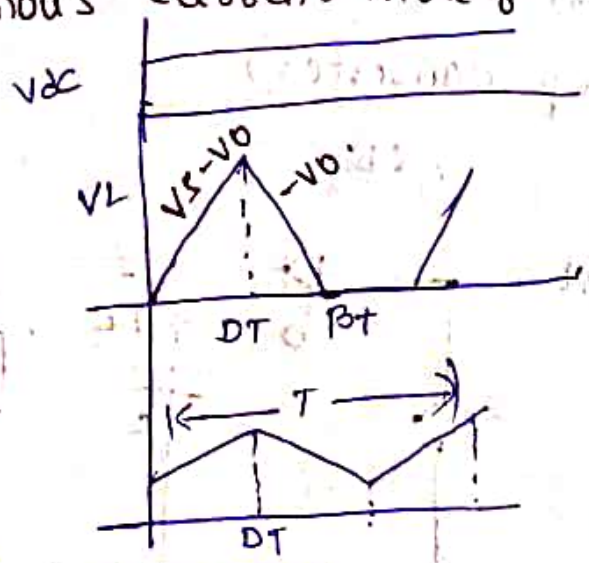

$\angle < \angle_{crit} \rightarrow$  Dis. C.M.

$V_O (avg)_{DCM} > V_O (avg)_{CCM}$

Switch on

$V_{L(on)} = V_S - V_O$ ,  $T_{on} = DT$

Switch off

$V_{L(off)} = -V_O$

VOL - sec balance =

$$T_{off} + T_{on} = T$$

$$T_{off} = (1-D)T$$



$$(V_s - V_o)DT + (-V_o)(1-D)T = 0$$

$$V_s D T - V_o (1-D) T = 0$$

$$V_s D = V_o (1-D)$$

$$V_o = \frac{V_s D}{1-D}$$


Boost converter  
(step up converter)

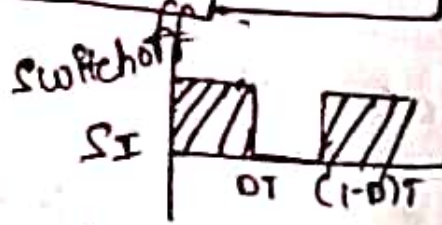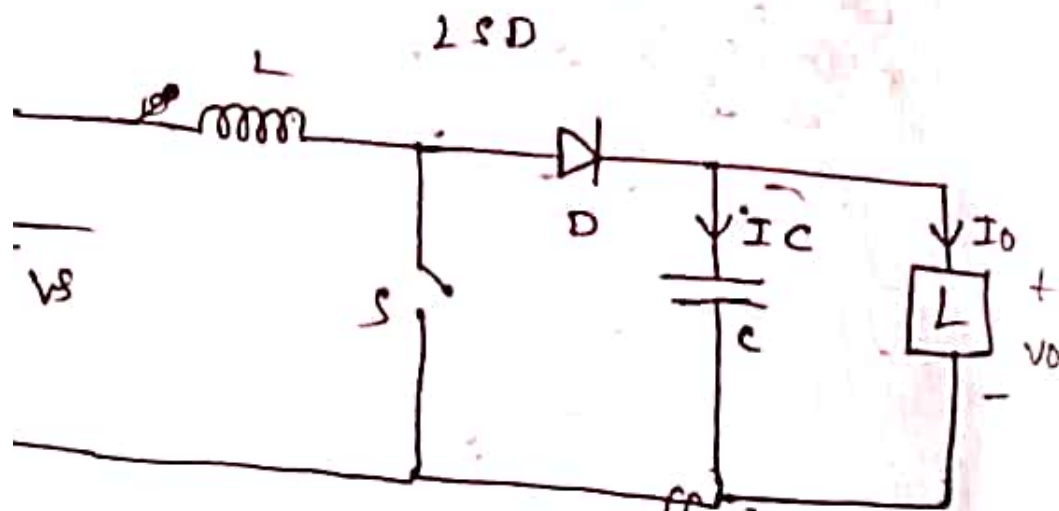


operation:

Continuous current mode:

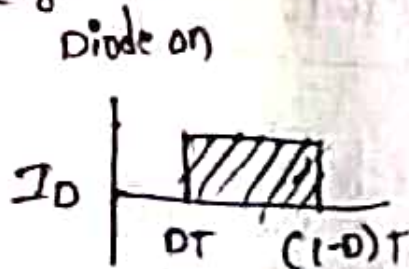switch  $\left\{ \begin{array}{l} \text{on} \\ \text{off} \end{array} \right.$  switch.



switch on:

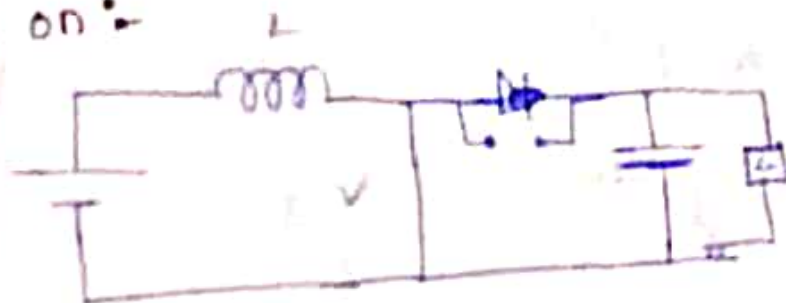

switch on, diode is off.

$$V_S^+ - L - \text{sw} - v_c^-$$

$$V_L(\text{on}) = V_S$$


$$T_{\text{on}} = DT$$

$$I_c = -I_0$$

$$I_0 = I_c + I_D$$

$$0 = I_c + I_D$$


$$I_c = -I_0$$

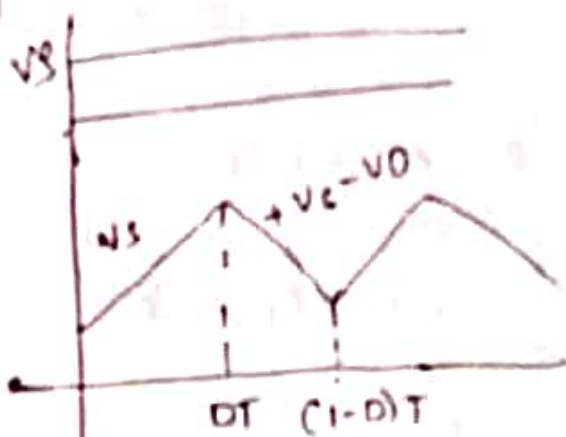

Voltage across capacitor



switch off

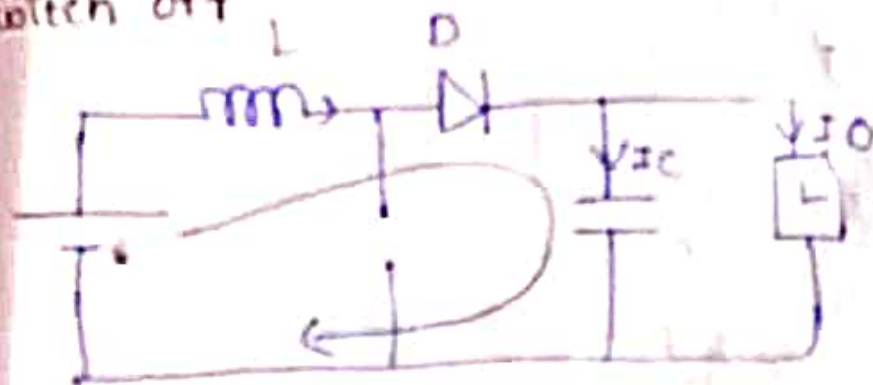

$$-V_S + V_L(\text{off}) + v_0 = 0$$

$$V_L(\text{off}) = V_S - v_0$$

$$-I_0 DT + I_L (1-D)T - I_0 (1-D)T = 0$$

$$-I_0 DT + I_L T - I_L DT - I_0 T + I_0 DT = 0$$

$$I_L T - I_L DT - I_0 T = 0$$

$$I_L T [1-D] - I_0 T = 0$$

$$I_0 T = I_L T [1-D]$$

$$I_0 = I_L (1-D)$$

$$I_L = \frac{I_0}{(1-D)}$$

\*\*

Current ripple ( $\Delta I_L$ )

$$V_L(\text{con}) = V_S$$

$$L \frac{di(\text{con})}{dt} = V_S$$

$$L \frac{\Delta I_L}{DT} = V_S$$

$$\Delta I_L = \frac{V_S D}{fL}$$

Buck

$$V_L = L \frac{di}{dt}$$

$$V_L(\text{con}) = V_S - V_0$$

$$L \frac{di}{dt} = V_S - V_0$$

$$t_{\text{on}} = DT$$

$$L \frac{\Delta I_L}{DT} = V_S - V_0$$

$$\Delta I_L = \frac{(V_S - V_0) D}{fL}$$

$$\Delta I_L = \frac{D(1-D)V_S}{fL}$$

Switch current

$$I_{\text{sw}}(\text{avg}) = I_L \frac{DT}{T}$$

$$= I_0 D$$

Switch RMS:

$$I_{\text{RMS}} = I_L \sqrt{\frac{DT}{T}}$$
$$\Rightarrow I_L \sqrt{D}$$
$$\Rightarrow \frac{I_0}{(1-D)} \sqrt{D}$$

Diode current:

$$I_{D(\text{avg})} = I_L \frac{(1-D)T}{T}$$
$$= \frac{I_0}{(1-D)} (1-D)$$
$$= I_0$$

$$I_{D(\text{RMS})} = I_L \sqrt{\frac{(1-D)T}{T}}$$
$$= I_L \sqrt{(1-D)}$$
$$= \frac{I_0}{(1-D)} (\sqrt{1-D})$$

Capacitor current in output voltage:

$$\Delta V_C = \Delta V_D$$

$$I_C = -I_0$$

$$C \frac{dv}{dt} = -I_0$$

Buck current

$$I_D = I_0 \frac{(1-D)T}{T}$$
$$= I_0 (1-D)$$

$I_D$

$$I_{D(\text{RMS})} = I_0 \sqrt{\frac{(1-D)T}{T}}$$
$$= I_0 \sqrt{(1-D)}$$

$$V_C = \frac{1}{2} \left[ \frac{I_0 D}{fC} \right]$$

$$V_C = \frac{1}{2} \left[ \frac{V_0 D}{R f C} \right]$$

$$V_C = \frac{1}{2} \left[ \frac{V_S D}{R f C} \right]$$

$V_C = V_0$

$$V_0 = \frac{1}{2} \left[ \frac{V_0 D}{R f C} \right]$$

$$C = \frac{D}{2 f R}$$

Discontinuous current mode  
Boost converter.

$$V_{on} = V_S$$

$$T_{on} = D T$$

$$V_{off} = V_S - V_0$$

$$T_{off} = (1-D) T$$

1st sec Balance

$$V_{on} \cdot T_{on} + V_{off} \cdot T_{off} = 0$$

$$V_S D T + (V_S - V_0) (1-D) T = 0$$

$$V_S D T + V_S (1-D) T - V_0 (1-D) T = 0$$

$$V_s \beta T - V_o \beta T + V_o D T = 0$$

$$V_s \beta T - V_o T (\beta - D) = 0$$

$$V_s \beta T = V_o T (\beta - D)$$

$$V_o = \frac{V_s \beta}{\beta - D}$$

Problems :-

A Buck regulator has a supply voltage of 24 volts and a duty ratio of 0.375, the chopping frequency is 25 kHz. The filter consist of an inductance of 100  $\mu$ H and a capacitance of 200  $\mu$ F the average load current is 2 Ampe. Determine the peak to peak ripple current, upper and lower limits currents and peak to peak ripple voltage.

Sol<sup>o</sup>

Given data

$$V_s = 24 \text{ volts}$$

$$\text{duty ratio } (D) = 0.375$$

$$\text{frequency} = 25 \text{ kHz}$$



## Assignment-4.

1.  $V_s = 220V$

$$f = 1\text{kHz}$$

$$I_o = 50A$$

$$R = 3\Omega$$

$$L = ?$$

$$\Delta I_L = ?$$

$$\Delta I_L = \frac{V_o(1-D)}{fL}$$

$$L = \frac{R(1-D)}{2f} \Rightarrow 3(1-D)$$

1. Design a boost converter  
(or)

Dc boost regulator with an output voltage of 15V from a 6V source. The load is pure resistance of 25ohms. The peak to peak ripple is to be  $< 0.6\%$ . The inductor current is to be continuous. also find maximum and minimum value of the inductor current.

Sol<sup>n</sup>

$$V_s = 6V$$

$$V_o = 15V$$

$$R = 25\Omega$$

$$I_L + \frac{\Delta I_L}{2}$$

peak to peak capacitance.

$$C = \frac{I_0 D}{(\Delta V_0 F)} \Rightarrow \frac{0.6 \times 0.6}{150 \times \frac{0.6}{100} \times 30 \times 10^{-3}}$$


$$\Rightarrow \frac{0.36}{9000 \times 180 \times 15}$$

$$\Rightarrow 4 \times 10^{-5} \Rightarrow 1.33 \times 10^{-4}$$

$$\Rightarrow 133.3$$

Buck-Boost Converter

stepdown and stepup / Indirect Regulator

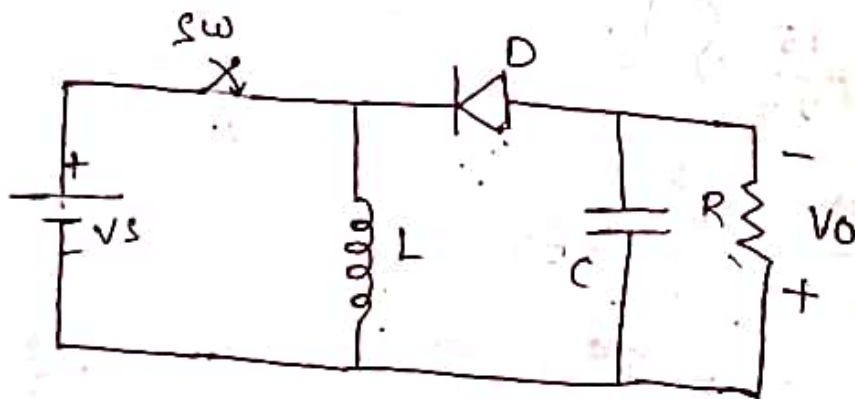

It operates 2 modes.

1. switch on. ( $0 < D < DT$ )

2. switch off ( $DT < D < T$ )

1. switch on

voltage  $V_L$

$$V_L = V_S$$

$\Delta I_L$  (current ripple):

$$V_{L(on)} = V_S$$

$$L \frac{di_{(on)}}{dt} = V_S$$

$$L \frac{\Delta I_L}{DT} = V_S$$

$$\Delta I_L = \frac{V_S D}{fL}$$

$$I_{L(max)} = I_L + \frac{\Delta I_L}{2}$$

$$I_{L(min)} = I_L - \frac{\Delta I_L}{2}$$

switch current:

$$I_{sw(avg)} = I_L$$

$$V_C = V_D$$

$$\frac{OD}{FC} = 0$$

$$\frac{D}{C} = 0$$

$$\frac{D}{D}$$

critical value of inductance

$$I_L \min = 0$$

$$I_L - \frac{\Delta I_L}{2} = 0$$

$$-\left(\frac{I_0}{C(1-D)}\right) - \frac{VSD}{2fL} = 0$$

$$-\left(\frac{\frac{V_0}{R}}{C(1-D)}\right) - \frac{VSD}{2fL} = 0$$

$$-\left(\frac{V_0}{RC(1-D)}\right) - \frac{VSD}{2fL} = 0$$

$$-\left(\frac{-VSD}{2C(1-D)^2}\right) = \frac{1}{2fL}$$

$$2fL = RC(1-D)^2$$

$$L_c = \frac{RC(1-D)^2}{2f}$$

critical value of inductan capacitance

$$V_C \min = 0$$

$$V_C = V_0$$

$$V_C - \frac{\Delta V_C}{2} = 0$$

$$\frac{I_0}{C} - \frac{V_0 D}{2fC} = 0$$

$$V_0 - \frac{V_0 D}{2RfC} = 0$$

$$V_0 = \frac{V_0 D}{2RfC}$$

220  $\mu$ F and the load resistance is 10-ohms.

determining avg o/p voltage, average max and

min value of inductor current & peak to peak voltage ripple?

Sol<sup>n</sup> Given that

$$V_s = 24, D = 0.4, f = 40 \text{ kHz},$$

$$L = 100 \mu\text{H}, C = 220 \mu\text{F}, R = 10 \Omega$$

$$\textcircled{1} V_{0 \text{ avg}} = \frac{-V_s D}{C(1-D)} \quad 0 < D < 0.5 \text{ Buck.}$$
$$= \frac{-24(0.4)}{1-0.4} \Rightarrow \frac{9.6}{0.6} \Rightarrow 16 \text{ volts.}$$

$\textcircled{2}$  average max and min.

$$V_{\text{max}} \Rightarrow \Delta V_C + \frac{V_C}{2}$$

$$I_{L \text{ max}} = I_L + \frac{\Delta I_L}{2}$$

$$I_L = -\left(\frac{I_O}{1-D}\right) \Rightarrow -\left(\frac{V_O}{R(1-D)}\right) \Rightarrow -\left(\frac{-V_s D}{R(1-D)}\right)$$

$$\Rightarrow \left(\frac{24 \times 0.4}{10(0.6)}\right) \Rightarrow 2.66$$

$$\Delta I_L \Rightarrow \frac{V_s D}{fL} \Rightarrow \frac{24 \times 0.4}{40 \times 10^3 \times 100 \times 10^{-6}} \Rightarrow \frac{9.6}{4}$$
$$\Rightarrow 2.4 \text{ A}$$

$$I_{L \text{ max}} = 2.66 + \frac{2.4}{2} \Rightarrow 3.86$$

to peak ripple voltage?

Given that

$$V_s = 24V, f = 30, D = 0.25,$$

$$L = 300\mu H, C = 150\mu F, I_o = 1.5A$$

average output voltage

$$V_o = \frac{V_{SD}}{C(1-D)} \Rightarrow - \left( \frac{24 \times 0.25}{1 - 0.25} \right) \Rightarrow -8$$

inductor current

$$\Delta I_L \Rightarrow \frac{D V_s}{f L} \Rightarrow \frac{0.25 \times 24}{30 \times 10^{-3} \times 300 \times 10^{-6}}$$

$$\Rightarrow 0.66 \text{ Amps.}$$

peak to peak ripple ~~current~~ voltage.

$$\Delta V_C = \frac{I_{OP}}{f C} \Rightarrow \frac{(1.5)(0.25)}{30 \times 10^{-3} \times 150 \times 10^{-6}}$$

$$\Rightarrow \frac{0.375}{\phantom{30 \times 10^{-3} \times 150 \times 10^{-6}}} \Rightarrow 0.083 V.$$

$$I_c = \frac{R(1-D)^2}{2f} \Rightarrow \frac{V_o(1-D)^2}{2f I_o}$$

$$\Rightarrow \frac{-8(1-0.25)^2}{2 \times 30 \times 10^3 \times 1.5} \Rightarrow 5 \times 10^{-5}$$

$$C = \frac{D}{I_c} \Rightarrow \frac{0.25}{\phantom{5 \times 10^{-5}}} \Rightarrow \frac{0.25}{5 \times 10^{-5}} = 5000 \mu F$$

$$I_{L \min} = I_L - \frac{I_D}{2}$$

$$\Rightarrow 2.664 - 1.2$$

$$\Rightarrow 1.46 \text{ amp.}$$

③

$$\text{Peak to peak ripple } \Delta V_C \Rightarrow \frac{I_D D}{FC}$$

$$\Delta V_C \Rightarrow \frac{(0.4)(-1.6)}{40 \times 10^3 \times 220 \times 10^{-6}}$$

$$\Rightarrow \frac{-0.64}{8.8}$$

$$\Rightarrow 0.072$$

Percentage of voltage ripple.

$$\Rightarrow \frac{\Delta V_O}{V_O} \times 100.$$

$$\Rightarrow \frac{0.072}{0.96} \times 100 \Rightarrow 7.5$$

Assignment:

Buck Boost converter has input 24V and operates at 30 kHz, when the duty cycle is 0.25,  $L = 300 \mu\text{H}$ ,  $C = 150 \mu\text{F}$ , avg load current 1.5A. Determine the average peak to peak

$$C = \frac{D}{2FR}$$

continuous current

$$V_{L on} = V_s$$

$$V_{L off} = V_o$$

$$T_{on} = DT$$

$$T_{off} = (\beta - D)T$$

volt sec balance

$$T_{on} \cdot V_{L on} + V_{L off} \cdot T_{off} = 0$$


$$V_s DT + (\beta - D)T V_o = 0$$

$$V_s D + V_o \beta - V_o D = 0$$

$$V_s D + V_o T (\beta - D) = 0$$

$$V_s D = -V_o (\beta - D)$$

$$V_o = -\frac{V_s D}{(\beta - D)}$$

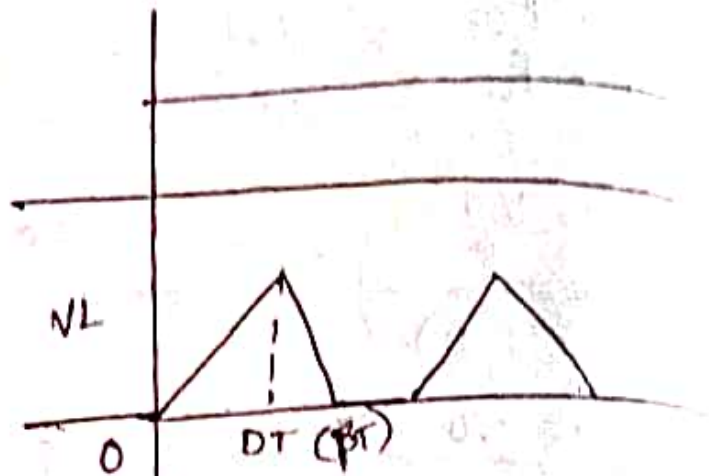

+  $V_s$  → switch -  $V_L$

$$V_L = (V_s - V_o) - V_L$$

- Design a Buck Boost regulator with an input voltage of 25 volts and duty ratio of 0.4. the switching frequency is 40kHz. The inductance value is 100 μH and capacitance value is



Ripple in voltage ( $\Delta V_C$ ) :-

$\Delta V_C$  :-

during on  $D \rightarrow$  off

$$I_C = -I_O$$

$$C \frac{dV_C}{dt} = -I_O$$

$$\int dV_C = \int \frac{-I_O}{C} dt$$

$$\int_{\text{Max}}^{\text{min}} dV_C = \int_0^{DT} -\frac{I_O}{C} dt$$

$$V_{\text{min}} - V_{\text{max}} = -\frac{I_O}{C} (DT)$$

$$\Delta V_C = \frac{I_O}{C} (DT)$$

$$\Delta V_C = \frac{I_O}{C} (DT)$$

$$\Delta V_C = \frac{I_O D}{fC}$$

$$-I_L T (1-D) = -I_O$$

$$-I_L (1-D) = I$$

$$-I_L (1-D) =$$

$$I_O = -I_L (1-D)$$

$$I_L = -\frac{I_O}{1-D}$$



$$V_S D T + V_O (1-D) T = 0$$

$$V_S D T + V_O T - V_O D T = 0$$

$$V_S D T + V_O T (1-D) = 0$$

$$V_S D T = -V_O T (1-D)$$

$$V_S D = -V_O (1-D)$$

$$V_O = \frac{-V_S D}{(1-D)}$$

ampere sec balance theory

$$I_C(\text{on}) D T + I_C(\text{off}) (1-D) T = 0$$

$$-I_O D T + -(I_L + I_O) (1-D) T = 0$$

$$-I_O D T - (I_L T - I_L D T + I_O T - I_O D T) = 0$$

$$-I_O D T - I_L T + I_L D T - I_O T + I_O D T = 0$$

$$-I_L T + I_L D T - I_O T = 0$$

$$-I_L T (1-D) - I_O T = 0$$

$$-I_L T (1-D) = I_O T$$

$$-I_L (1-D) = I_O$$

$$I_O = -I_L (1-D)$$

$$I_L = -\left(\frac{I_O}{1-D}\right)$$


→ opposite to boost converter.

$$I_D = I_C + I_O$$

$$0 = I_C + I_O$$

$$I_C = -I_O$$


switch off:

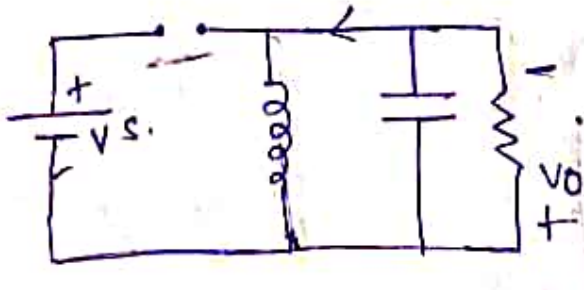

$$V_{L,off} - V_o = 0$$

$$V_L(off) = V_o$$

$$I_{C,off} = -(I_L + I_O)$$

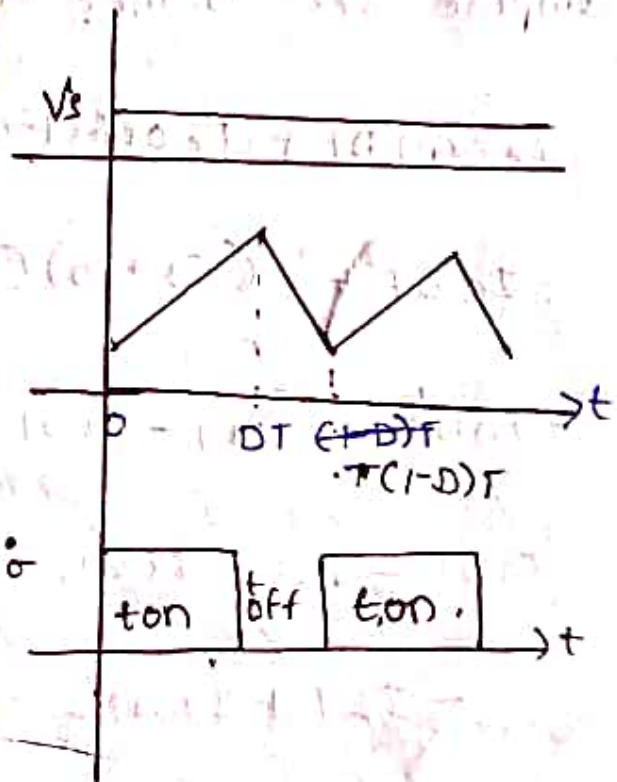

Volt sec balance theory:

$$V_{on} T_{on} + V_{off} T_{off} = 0$$

$$V_s D T + V_o (1-D) T = 0$$

$$V_s D T + V_o T - V_o D T = 0$$

$$V_s D T + V_o T (1-D) = 0$$

$$V_s D = -V_o (1-D)$$

$$V_s D = -V_o$$

$$V_o = -V_s D$$

$$I_{max} = I_L + \frac{\Delta I_L}{2}$$

$$I_{min} = I_L - \frac{\Delta I_L}{2}$$

$$\Delta I_L = \frac{V_{SD}}{fL} \Rightarrow$$

$$D \Rightarrow V_0$$

$$L = \frac{D(1-D)^2 R}{2F}$$

$$V_0 = \frac{V_S}{1-D} \Rightarrow$$

chopping frequency  $F = 30 \text{ kHz}$

$$(1-D) = \frac{V_S}{V_0}$$

$$L = \frac{0.6^2 (1-0.6)^2 R}{2(30)}$$

$$(1-D) = \frac{6}{15} \Rightarrow 0.4 \Rightarrow 0.6$$

$$D = 1 - 0.4$$

$$\Rightarrow 40 \text{ mH}$$

$$D = 0.6$$

$$I_0 = \frac{V_0}{R} \Rightarrow \frac{15}{25} \Rightarrow 0.6$$

$$\Delta I_L = \frac{V_{SD}}{fL} \Rightarrow \frac{0.6 \times 0.6}{30 \times 60}$$

$$I_L = \frac{I_0}{(1-D)}$$

$$\Rightarrow \left( \frac{0.6}{1-0.6} \right)$$

$$\Rightarrow \cancel{3 \times 10^{-6}} 2 \text{ A}$$

$$\Rightarrow \frac{0.6}{0.4} \Rightarrow 1.5$$

$I_{max} =$

select an inductance of  $l = 60.91 \text{ mH}$

$$I_{max} = 1.5 + \frac{2}{2}$$

$$\Rightarrow 1.5 + 1 \Rightarrow 2.5$$

$$I_{min} = 1.5 - \frac{2}{2} \Rightarrow 0.5$$

$$= 2 + \frac{2.25}{2}$$

$$= 3.125$$

$$I_L \text{ min} \Rightarrow I_L = \frac{\Delta I_L}{2}$$

$$\Rightarrow 2 = \frac{2.25}{2}$$

$$= 0.875$$

determine the min value of inductance for which the current is continuous.

$$L_{\text{min (or)}} L_C = \frac{R(1-D)}{2fL}$$

$$\Rightarrow \frac{0(1-0) \text{ Vs}}{2fL}$$

$$\Rightarrow \frac{5.625}{2 \times 25 \times 10^3 \times 100 \times 10^{-6}}$$

$$\Rightarrow$$

Note :-

The relation b/w  $\Delta I_L$  and  $I_C$  in buck

$$\text{Converter } L_C = \frac{\Delta I_L}{2}$$

$$\text{Inductance} = 100 \mu\text{H}$$

$$\text{Capacitance} = 200 \mu\text{f}$$

$$\Delta I_L = \frac{D(1-D) V_S}{fL}$$

$$\Rightarrow \frac{0.375(1-0.375) 24}{10^3 \times 25 \times 100}$$

$$\Rightarrow 2.25 \text{ Ampere}$$

$$\Delta V_C = \frac{D(1-D) V_S}{8f^2 LC}$$

$$= \frac{0.375(1-0.375) 24}{8 \times (25)^2 \cdot (100)(200)}$$

$$\Rightarrow \frac{5.625}{8 \times (25 \times 10^3)^2 (100)(200)}$$

$$= \frac{5.625}{1000}$$

$$= 0.05625 \text{ Volts}$$

$$I_L \text{ max} = I_L + \frac{\Delta I_L}{2}$$

$$\Rightarrow I_0 + \frac{\Delta I_L}{2}$$

$$\int_{\text{max}}^{\text{min}} dv = \int_0^T -\frac{I_0}{C} dt$$

$$V_{\text{min}} - V_{\text{max}} = -\frac{I_0}{C} [DT - 0]$$

$$\Delta V_C = \frac{I_0}{C} [DT]$$

$$\therefore V_{\text{max}} - V_{\text{min}} = \Delta V_C$$

$$\Delta V_C = \frac{I_0 D}{fC}$$

Buck's

$\Delta V_C$ 's

$$\Delta V_C = \frac{\Delta I_L}{8fC}$$

critical value of inductance's

$$I_L \text{ min} = 0 \Rightarrow \frac{I_0}{(1-D)} - \frac{V_0}{2fL} = 0$$

$$I_L - \frac{\Delta I_L}{2} = 0$$

$$\Rightarrow \frac{V_0}{R} - \frac{VSD}{2fL} = 0$$

$$\frac{I_0}{(1-D)} - \frac{VSD}{2fL} = 0$$

$$\Rightarrow \frac{\frac{VS}{R(1-D)}}{(1-D)} - \frac{VSD}{2fL} = 0$$

$$L_c = \frac{D(1-D^2)R}{2f}$$

$$\frac{VS}{R(1-D)^2} - \frac{VSD}{2fL} = 0$$

$$\frac{VS}{R(1-D)^2} = \frac{VSD}{2fL}$$

critical value of capacitance's

$$T_{off} = (1-D)T$$

$$I_D = I_C + I_O$$

$$I_C = I_D - I_O$$

$$I_D = I_L$$

$$I_{C_{off}} = I_L - I_O$$

volt sec balance ⚡

$$T_{on} + T_{off} = T$$

$$V_S D T + (1-D)T(V_S - V_O) = 0$$

$$V_S D T + V_S T - V_O T - V_S D T + V_O D T = 0$$

$$V_S T - V_O T + V_O D T = 0$$

$$V_S T - V_O T(1-D) = 0$$

$$V_S T = V_O(1-D)T$$

$$V_S = \frac{V_O(1-D)}{D}$$

$$V_O = \frac{V_S D}{(1-D)}$$

amp sec balance ⚡

$$I_{C(on)} D T + I_{C(off)} (1-D) T = 0$$

$$-I_O D T + (I_L - I_O)(1-D) T = 0$$



\* ampere sec Balance

$$I_c(\text{on}) = I_L - I_0$$

$$I_c(\text{off}) = I_L - I_0$$

$$(I_L - I_0)T_{\text{on}} +$$

$$I_c(\text{on})T_{\text{on}} + I_c(\text{off})T_{\text{off}} = 0$$

$$(I_L - I_0)T_{\text{on}} + (I_L - I_0)T_{\text{off}} = 0$$

$$(I_L - I_0)DT + (I_L - I_0)(1-D)T = 0$$

$$I_L DT - I_0 DT + I_L T - I_0 DT - I_0 T + I_0 DT = 0$$

$$I_L T - I_0 T = 0$$

$$I_L T = I_0 T$$

$$\boxed{I_L = I_0}$$

\*

ripple current  $\Delta I_L$

$$V_L = L \frac{di}{dt}$$

$$V_L(\text{on}) = V_S - V_0$$

$$L \frac{di_{\text{on}}}{dt_{\text{on}}} = V_S - V_0$$

$$t_{\text{on}} = DT$$

$$L \frac{\Delta I_L}{DT} = V_S - V_0$$

$$\Delta I_L = \frac{(V_S - V_0)D}{fL}$$


$$= \frac{(V_S - V_S D)D}{fL}$$

4. The circuit is operating at steady state.

$$\text{Duty cycle } D = \frac{T_{on}}{T} = \frac{T_{on}}{T_{on} + T_{off}}$$

5.  $T_{on} = D T$ , and switch  $T_{off} = (1 - D) T$

Analysis of Buck Converter  
SDL

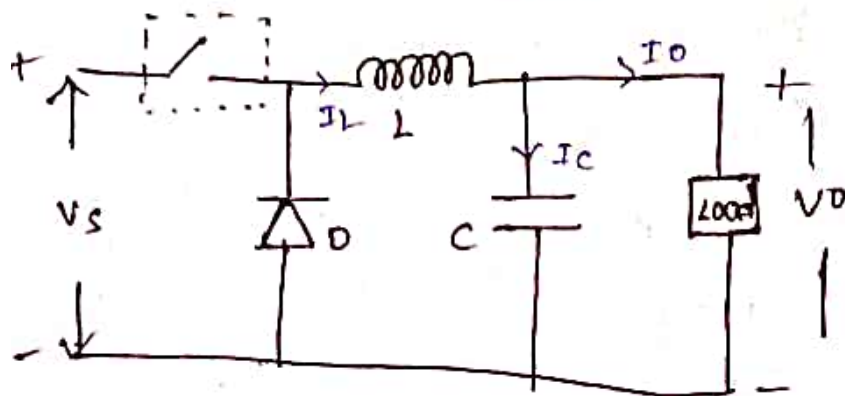

continuous current mode

it operates in 2 modes.

1. switch on 2. switch off condition.

using  
switch on conditions

$$V_s^+ - L - \text{load} - V_s^-$$

$$T_{on} = D T$$

$$D = \frac{\text{chopping time period}}{\text{switching period}}$$

$f =$  chopping frequency.



$$V_L(\text{con}) = V_s - V_O$$

$$I_C(\text{con}) = I_L - I_O$$

# Unit - 5
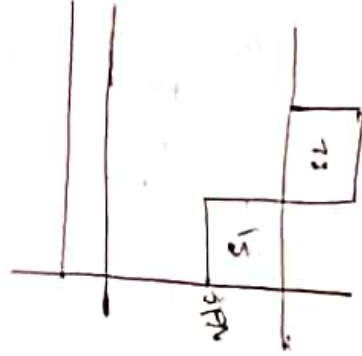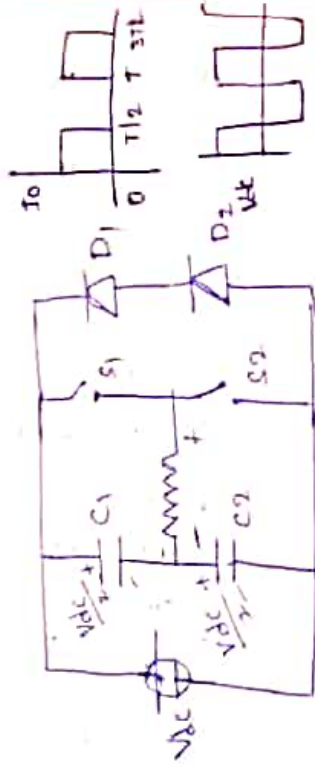
## DC - AC Converters

Classification:  $1-\phi \rightarrow$  H.B, F.B  $\rightarrow$  R, RL  
Home Appliances, Electrical vehicles  
 $3-\phi \rightarrow 120^\circ, 150^\circ$  - variable frequency  
displays, AC drive, induction heaters, supply  
 applications: UPS, HVDC, FACTS, induction heaters with R-load  
 Single Phase Half bridge inverter with R-load



Rms o/p voltage:-

$$V_o = \sqrt{\frac{1}{T_1} \int_0^{T_1} \left(\frac{V_{dc}}{2}\right)^2 dt}$$

$$V_{or} = \sqrt{\frac{1}{T_1} [T_1] \left(\frac{V_{dc}}{2}\right)^2}$$

$$V_o = \frac{V_{dc}}{2}$$

$V_o$  can be expressed in fourier series as

$$V_o = \frac{a_0}{2} + \sum_{n=1}^{\infty} a_n \cos n\omega t + b_n \sin n\omega t$$

Due to quarter wave symmetry along time

$n=1,3,5$ , the value of  $a_n$  and  $a_n$  is zero. The

value of  $b_n$  is

$$b_n = \frac{1}{\pi} \int_{-\pi/2}^{\pi/2} \frac{-V_m \sin(\omega t)}{2} d(\omega t) = \frac{2V_m}{n\pi} \Rightarrow \frac{2V_{dc}}{n\pi}$$

$$V_0 = \sum_{n=1,3,5} \frac{2V_{dc}}{n\pi} \sin(n\omega t)$$


similarly current through the reactor.

$$i_L = \sum_{n=1,3,5} \frac{1}{R} \frac{2V_{dc}}{n\pi} \sin(n\omega t)$$

Single phase half bridge with R-L load's



It operates in 4 modes (4 intervals)

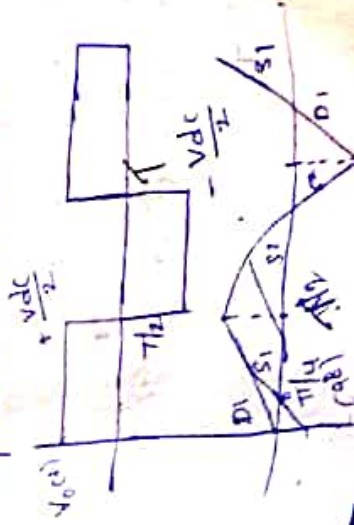

voltage control of inverter is (PWR)  
Two types of " width of the longest pulse:

$$\left(1 - \frac{V_s}{V_c}\right) \pi / N$$

1. External control.
2. Internal control.

Sinusoidal pulse width modulation.

- ① No of pulses  $N_p = \frac{f_c}{2f_r}$  for half cycle.  $\rightarrow$  call
- ②  $N_p - 1 \Rightarrow \frac{f_c}{2f_r - 1}$  when the peak voltages are the reference wave [Both]
- ③ The Harmonic number of the highest

amplitude is equal to

$$\frac{f_c}{f_r} \pm 1 = 2rP$$

Problem:

A 50 Hz, PWM inverter uses sinusoidal pulse width modulation based on sine triangle comparison

If the triangular frequency is 15 kHz, what will be no. of pulses for half period in the off coast and 80% modulation index. what will be the width of the longest pulse.

Sol:  $HI = 80\% \Rightarrow 0.8 \left(\frac{V_k}{V_c}\right)$

$$f_c = 15 \text{ kHz}$$

$$f_R = 50 \text{ Hz}$$

① No of pulses per half cycle

$$\Rightarrow \frac{F_c}{2 F_R} = \frac{15 \times 10^3}{2 \times 50} = 150$$

$$\Rightarrow \left(1 - \frac{V_x}{V_c}\right) \frac{\pi}{N}$$

$$\Rightarrow (1 - 0.8) \frac{\pi}{150} \Rightarrow 4.18 \text{ H.s}$$


Note :-

o/p voltage of 1- $\phi$  PWM inverter

$$V_d(t) = \sum_{n=1,3,5}^{\infty} \frac{V_s}{n\pi} \sin n\omega t$$

1. Explain the working of a 3- $\phi$  inverter with 120° mode of conduction with 3- $\phi$  delta connected resistive load.

resistive load?

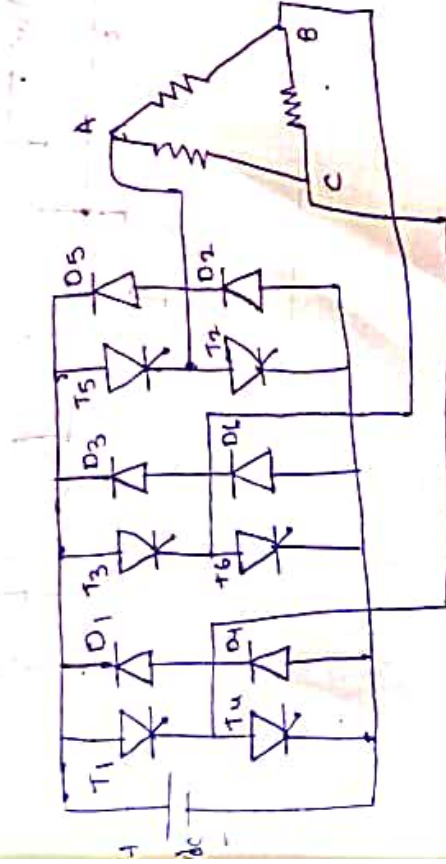

$A_{13}$  connected +ve,  $B_{11}$ -ve.

Mode -2.

$$T_2 \text{ & } T_1$$

firing pulses are given to  $T_3$  &  $T_4$

$B_{11}$  +ve,  $A_{11}$ -ve

Mode -3

$$T_2 \text{ & } T_2 \text{ } 3T/2$$

$T_3$  &  $T_4$  are on.

Mode -4


$$\frac{3T}{2} \text{ & } T \text{ & } T$$

( $0 \text{ & } T \text{ & } T$ )

$T_3$  &  $T_4$  off

2. current source inverter ?


a)

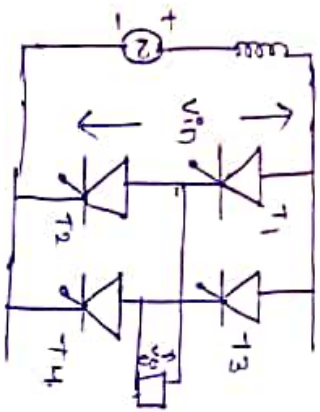



To maintain constant current

Inductance will be used load commutation

depends upon the free load.

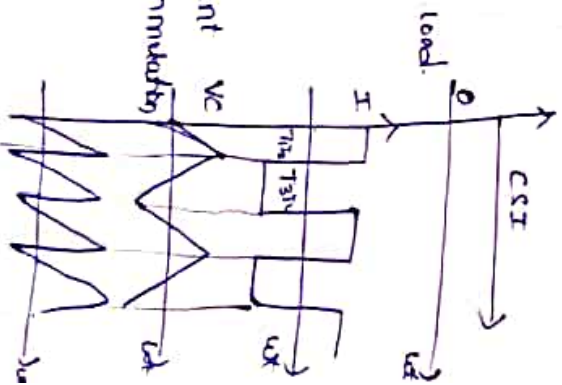

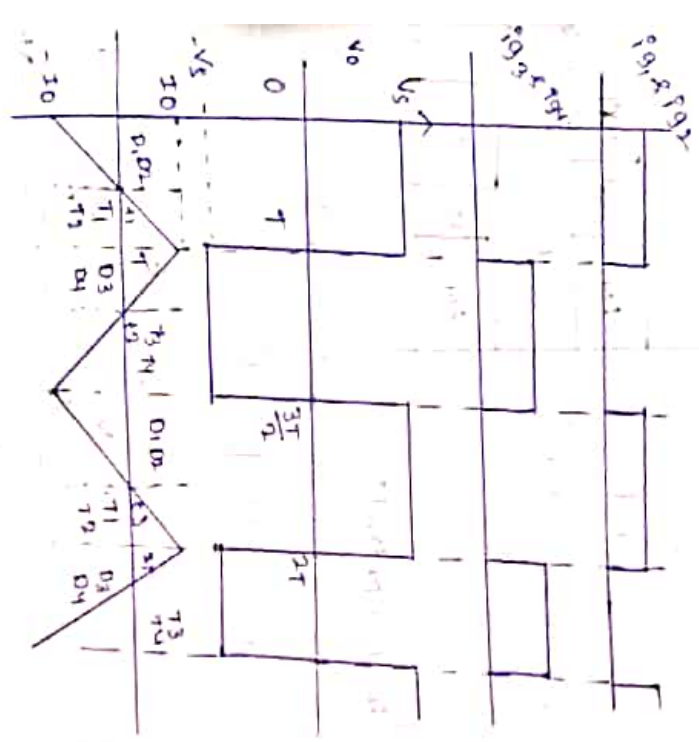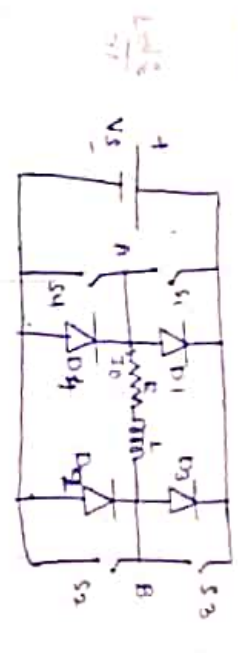1. Draw a neat CRT diagram for 1- $\phi$  full bridge inverter feeding inductive load. what is the function of feedback diodes?




4- Modes.

Model 16  
t1, t2, t3, t4

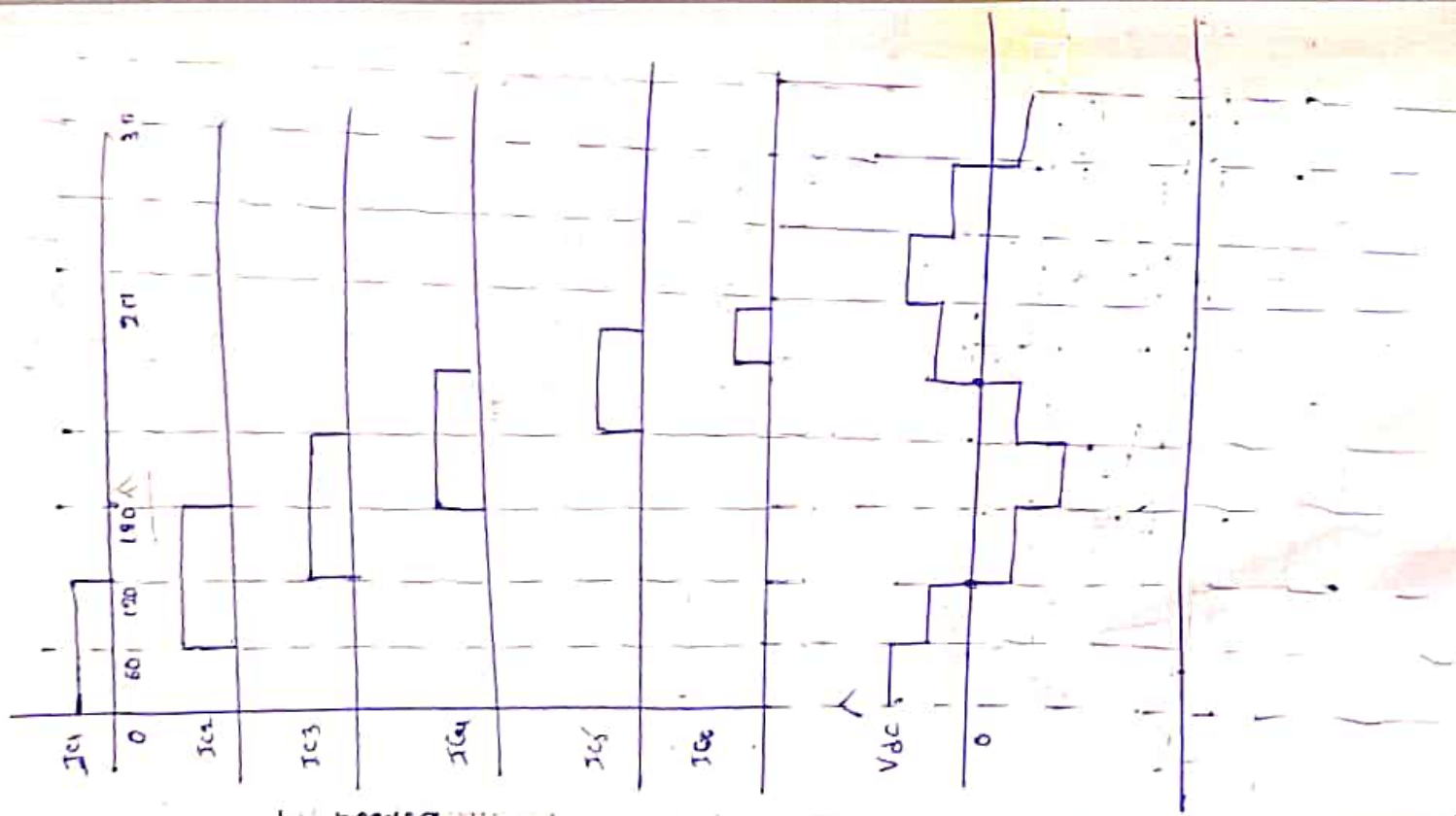- Thyristor T1 and T2 are on condition.
- Current passing through the supply to S1 to load to S2.
- Ve supply positive current increase cause.






Each thyristor  $T_1, T_2, T_3, T_4$

$$V_{o\text{rms}} = \frac{V_s}{2}$$

$$I_{o\text{rms}} = \frac{V_s}{2R}$$

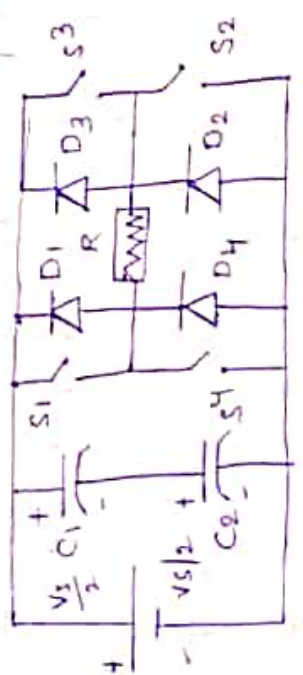single phase full bridge inverter with R load



It operates in 2 modes



$$1) S_1 \text{ close} \quad \left. \begin{array}{l} V_0 > 0 \\ -\frac{V_{dc}}{2} + V_0 = 0 \\ I_0 > 0 \end{array} \right\}$$

$$V_0 = \frac{V_{dc}}{2}$$

$$2) \text{ diode close (D}_1) \quad \left. \begin{array}{l} I_0 > 0 \\ V_0 > 0 \end{array} \right\}$$

$$-\frac{V_{dc}}{2} + V_0 = 0$$

$$3) S_2 \text{ close} \quad \left. \begin{array}{l} I_0 < 0 \\ V_0 < 0 \end{array} \right\}$$

$$V_0 = \frac{-V_{dc}}{2}$$

$$4) D_2 \text{ - ON}$$

$$\left. \begin{array}{l} I_0 > 0 \\ -\frac{V_{dc}}{2} - V_0 = 0 \\ V_0 < 0 \end{array} \right\}$$

Note: If an inductor is loading a pure inductive load the nature of current is  $\Delta^2$ 's wave.

$$\text{Peak value of current } (I_{\text{peak}}) = \frac{V_s}{L} \left( \frac{T}{4} \right)$$

$$\text{Peak to peak value of current} = \frac{V_s}{L} \left( \frac{T}{2} \right)$$

conduction angle of each diode is  $90^\circ$  (i.e.)

conduction time is  $T/4$

## Lecture 15: Three Phase DC-AC Inverters

### Three Phase DC-AC Inverters

#### Introduction

The topics covered in this chapter are as follows:

- Three phase DC-AC Converters
- 180-Degree Conduction with Star Connected Resistive Load
- 180-Degree Conduction with Star Connected  $R-L$  Load


#### Three Phase DC-AC Converters

Three phase inverters are normally used for high power applications. The advantages of a three phase inverter are:

- The frequency of the output voltage waveform depends on the switching rate of the switches and hence can be varied over a wide range.
- The direction of rotation of the motor can be reversed by changing the output phase sequence of the inverter.
- The ac output voltage can be controlled by varying the dc link voltage.

The general configuration of a three phase DC-AC inverter is shown in **Figure 1**. Two types of control signals can be applied to the switches:

- 180° conduction
- 120° conduction

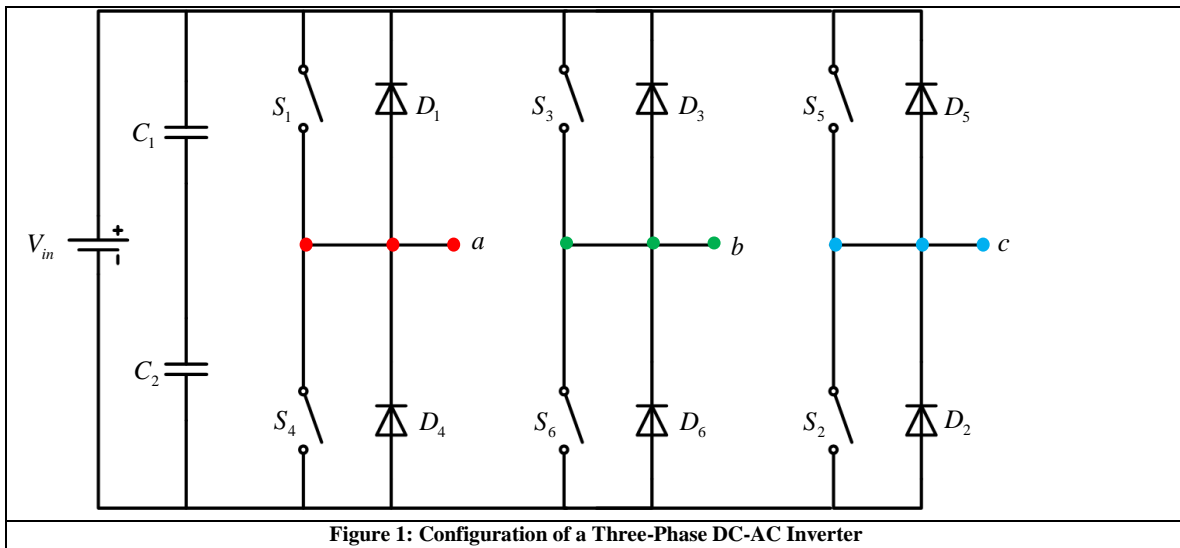

### 180-Degree Conduction with Star Connected Resistive Load

The configuration of the three phase inverter with star connected resistive load is shown in **Figure 2**. The following convention is followed:

- A current leaving a node point **a**, **b** or **c** and entering the neutral point **n** is assumed to be positive.
- All the three resistances are equal,  $R_a = R_b = R_c = R$ .

In this mode of operation each switch conducts for  $180^\circ$ . Hence, at any instant of time **three switches** remain **on**. When  $S_1$  is **on**, the terminal **a** gets connected to the positive terminal of input DC source. Similarly, when  $S_4$  is **on**, terminal **a** gets connected to the negative terminal of input DC source. There are six possible modes of operation in a cycle and each mode is of  $60^\circ$  duration and the explanation of each mode is as follows:

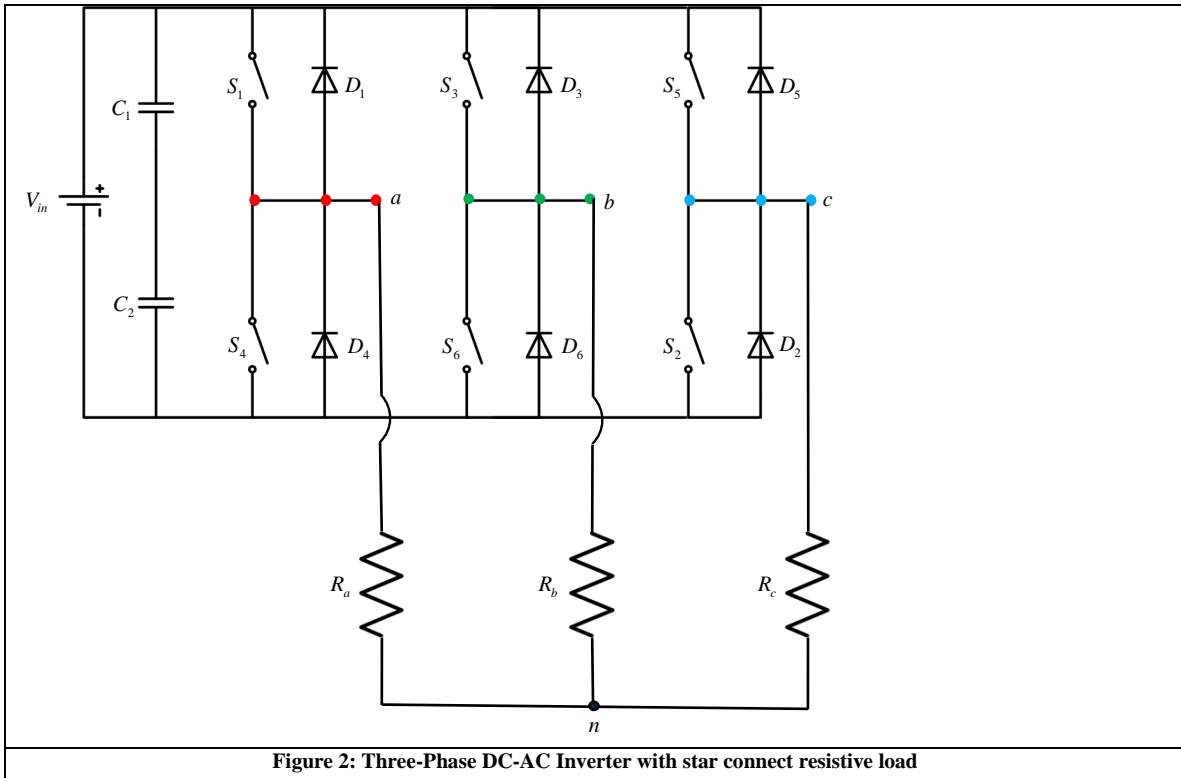


Figure 2: Three-Phase DC-AC Inverter with star connect resistive load

**Mode 1:** In this mode the switches  $S_5$ ,  $S_6$  and  $S_1$  are turned **on** for time interval  $0 \leq \omega t \leq \frac{\pi}{3}$ .

As a result of this the terminals **a** and **c** are connected to the positive terminal of the input DC source and the terminal **b** is connected to the negative terminal of the DC source. The current flow through  $R_a$ ,  $R_b$  and  $R_c$  is shown in **Figure 3a** and the equivalent circuit is shown in **Figure 3b**. The equivalent resistance of the circuit shown in **Figure 3b** is

$$R_{eq} = R + \frac{R}{2} = \frac{3R}{2} \quad (1)$$

The current  $i$  delivered by the DC input source is

$$i = \frac{V_{in}}{R_{eq}} = \frac{2}{3} \frac{V_{in}}{R} \quad (2)$$

The currents  $i_a$  and  $i_b$  are



$$i_a = i_c = \frac{1}{3} \frac{V_{in}}{R} \quad (3)$$

Keeping the current convention in mind, the current  $i_b$  is

$$i_b = -i = -\frac{2}{3} \frac{V_{in}}{R} \quad (4)$$

Having determined the currents through each branch, the voltage across each branch is

$$v_{an} = v_{cn} = i_a R = \frac{V_{in}}{3}; \quad v_{bn} = i_b R = -\frac{2V_{in}}{3} \quad (5)$$

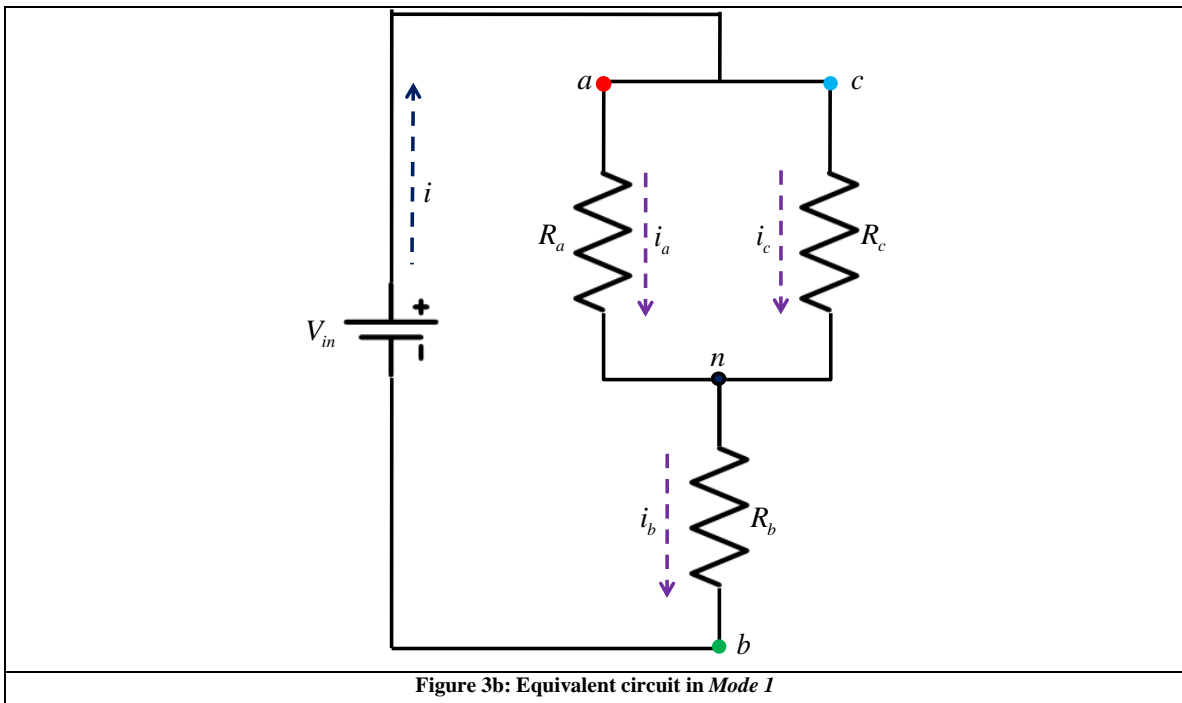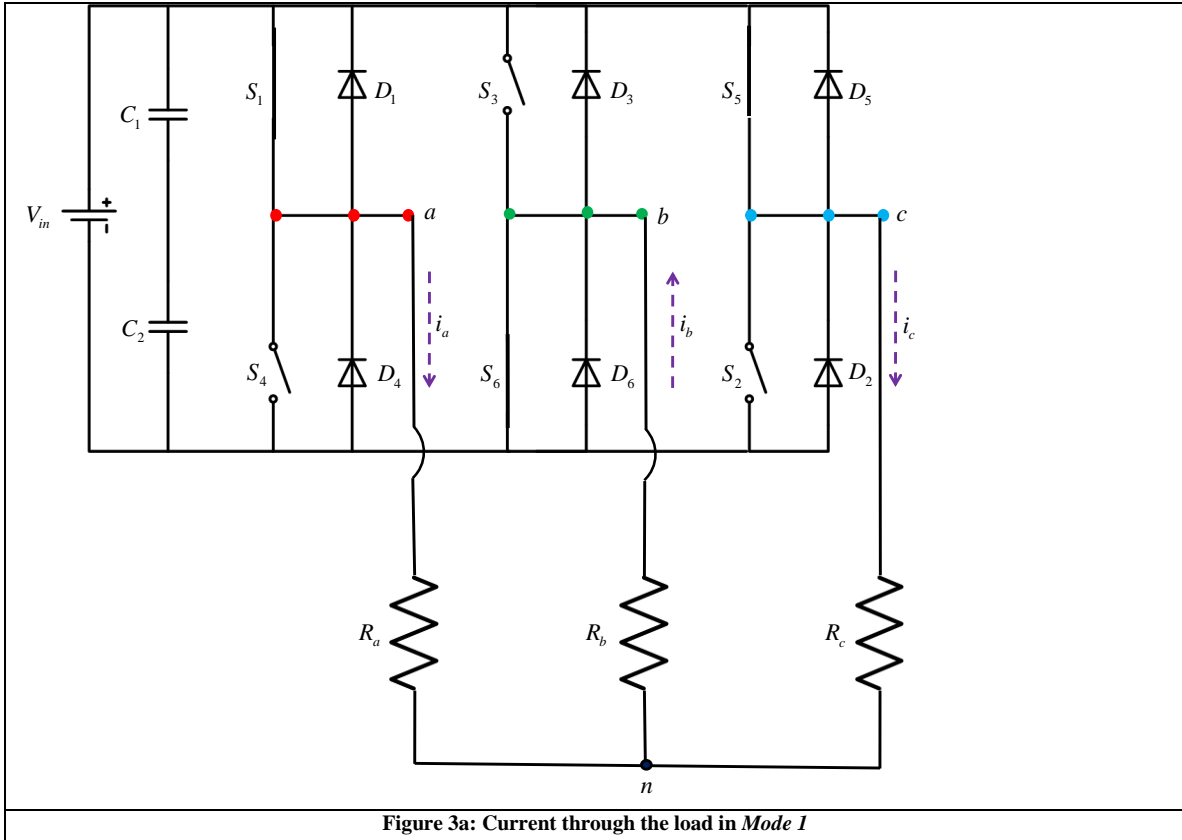


**Mode 2:** In this mode the switches  $S_6, S_1$  and  $S_2$  are turned **on** for time interval  $\frac{\pi}{3} \leq \omega t \leq \frac{2\pi}{3}$ .

The current flow and the equivalent circuits are shown in **Figure 4a** and **Figure 4b** respectively. Following the reasoning given for **mode 1**, the currents through each branch and the voltage drops are given by

$$i_b = i_c = \frac{1}{3} \frac{V_{in}}{R}; \quad i_a = -\frac{2}{3} \frac{V_{in}}{R} \quad (6)$$

$$v_{bn} = v_{cn} = \frac{V_{in}}{3}; \quad v_{an} = -\frac{2V_{in}}{3} \quad (7)$$

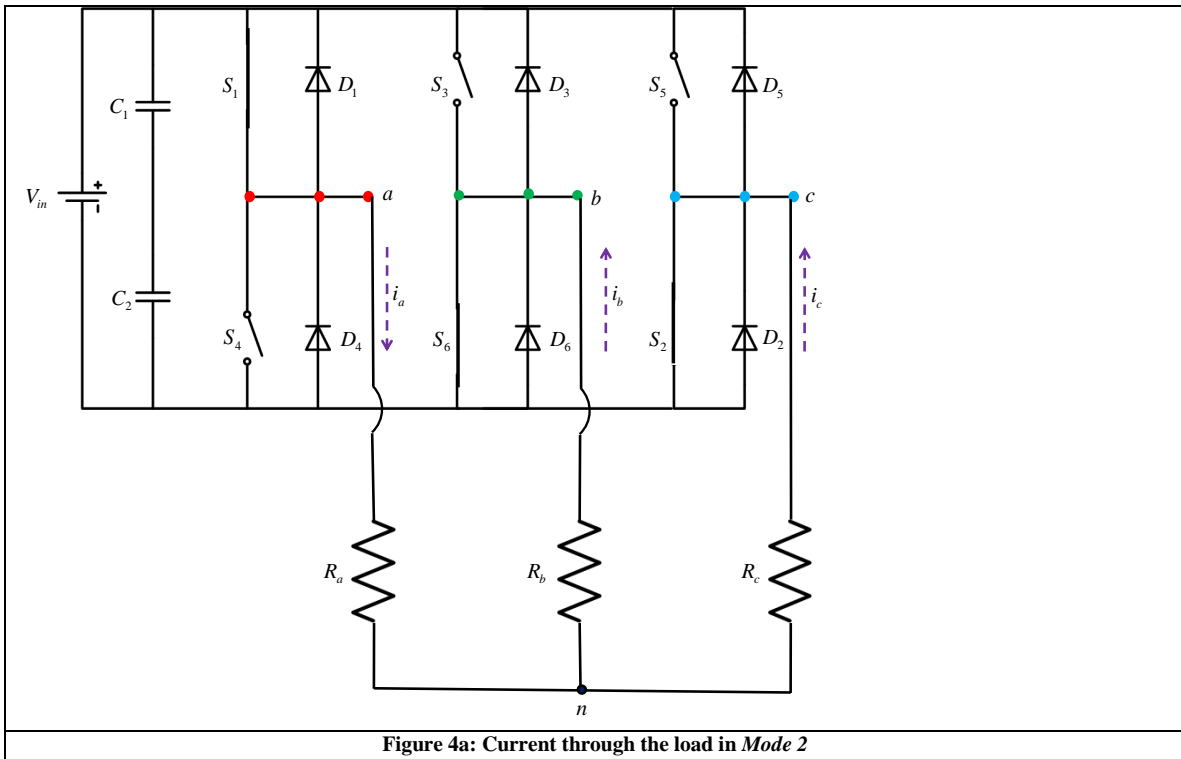



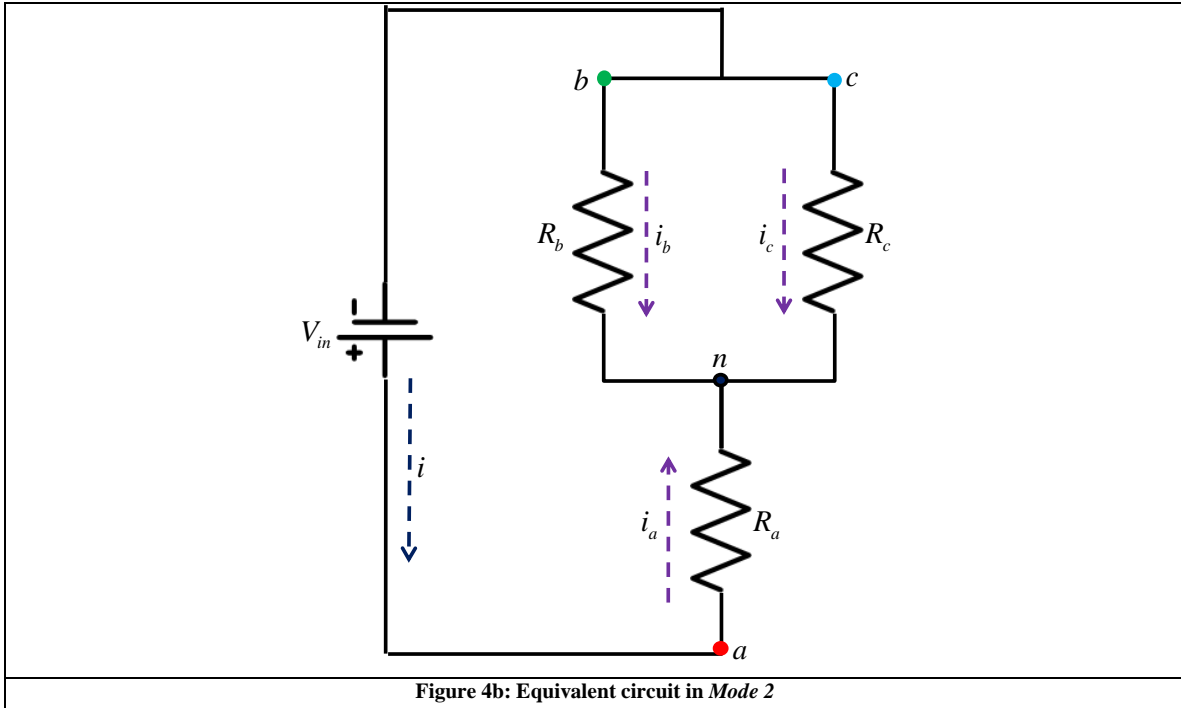


Figure 4b: Equivalent circuit in Mode 2

**Mode 3:** In this mode the switches  $S_1$ ,  $S_2$  and  $S_3$  are **on** for  $\frac{2\pi}{3} \leq \omega t \leq \pi$ . The current flow and the equivalent circuits are shown in **Figure 5a** and **figure 5b** respectively. The magnitudes of currents and voltages are:

$$i_a = i_b = \frac{1}{3} \frac{V_{in}}{R}; i_c = -\frac{2}{3} \frac{V_{in}}{R} \quad (8)$$

$$v_{an} = v_{bn} = \frac{V_{in}}{3}; v_{cn} = -\frac{2V_{in}}{3} \quad (9)$$

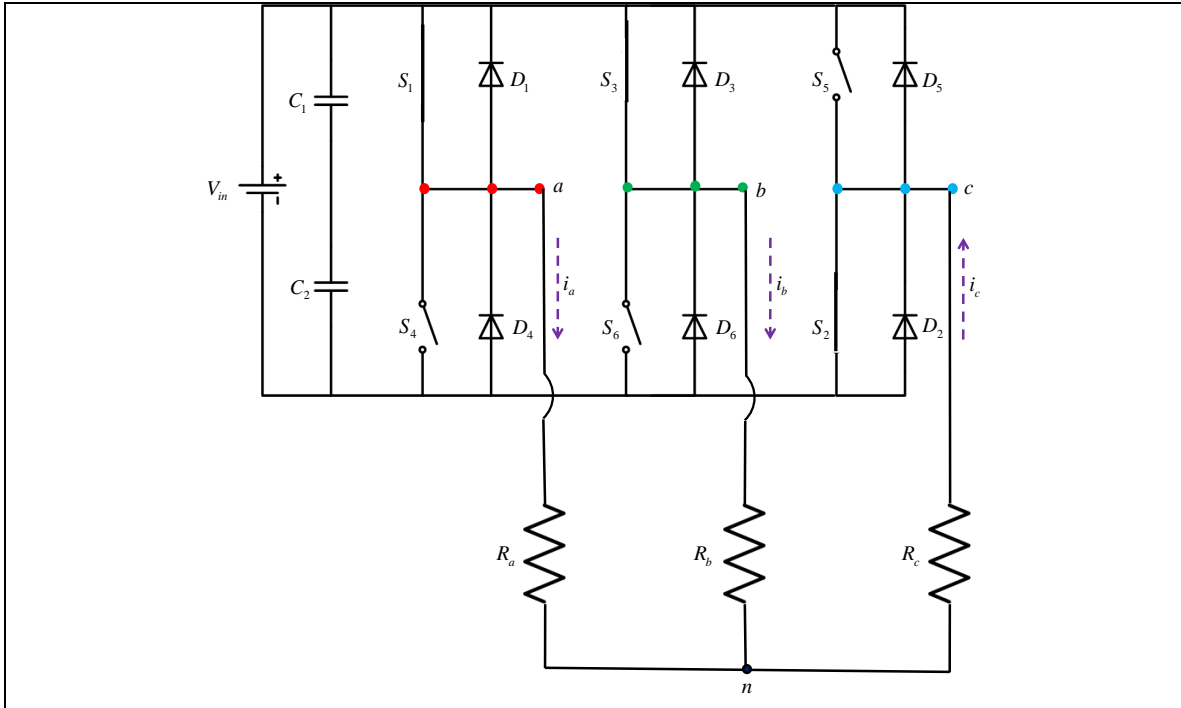


Figure 5a: Current through the load in Mode 32

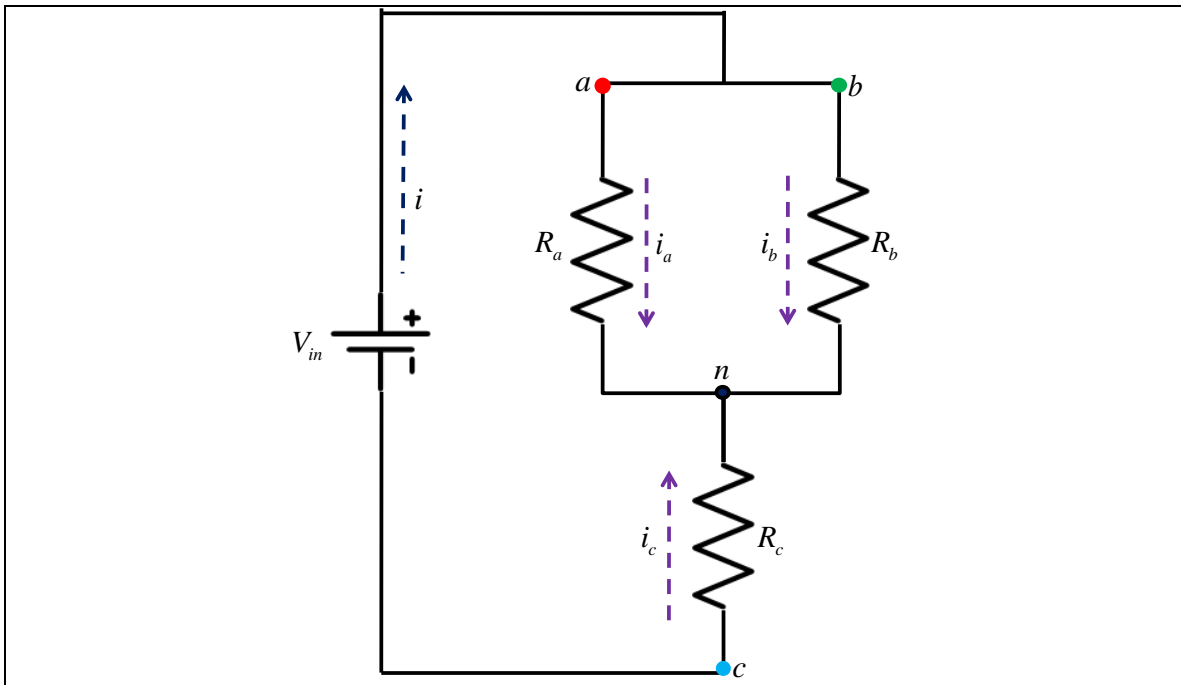


Figure 5b: Equivalent circuit in Mode 3

For **modes 4, 5** and **6** the equivalent circuits will be same as **modes 1, 2** and **3** respectively. The voltages and currents for each mode are:

$$\left. \begin{aligned} i_a = i_c = -\frac{1}{3} \frac{V_{in}}{R}; i_b = \frac{2}{3} \frac{V_{in}}{R} \\ v_{an} = v_{cn} = -\frac{V_{in}}{3}; v_{bn} = \frac{2V_{in}}{3} \end{aligned} \right\} \text{for mode 4} \quad (10)$$

$$\left. \begin{aligned} i_b = i_c = -\frac{1}{3} \frac{V_{in}}{R}; i_a = \frac{2}{3} \frac{V_{in}}{R} \\ v_{bn} = v_{cn} = -\frac{V_{in}}{3}; v_{an} = \frac{2V_{in}}{3} \end{aligned} \right\} \text{for mode 5} \quad (11)$$

$$\left. \begin{aligned} i_a = i_b = -\frac{1}{3} \frac{V_{in}}{R}; i_c = \frac{2}{3} \frac{V_{in}}{R} \\ v_{an} = v_{bn} = -\frac{V_{in}}{3}; v_{cn} = \frac{2V_{in}}{3} \end{aligned} \right\} \text{for mode 6} \quad (12)$$

The plots of the phase voltages ( $v_{an}$ ,  $v_{bn}$  and  $v_{cn}$ ) and the currents ( $i_a$ ,  $i_b$  and  $i_c$ ) are shown in **Figure 6**. Having known the phase voltages, the line voltages can also be determined as:

$$\begin{aligned} v_{ab} &= v_{an} - v_{bn} \\ v_{bc} &= v_{bn} - v_{cn} \\ v_{ca} &= v_{cn} - v_{an} \end{aligned} \quad (13)$$

The plots of line voltages are also shown in **Figure 6** and the phase and line voltages can be expressed in terms of Fourier series as:

$$\begin{aligned} v_{an} &= \sum_{n=1,3,5,\dots}^{\infty} \frac{4V_{in}}{3n\pi} \left[ 1 + \sin \frac{n\pi}{2} \sin \frac{n\pi}{6} \right] \sin(n\omega t) \\ v_{bn} &= \sum_{n=1,3,5,\dots}^{\infty} \frac{4V_{in}}{3n\pi} \left[ 1 + \sin \frac{n\pi}{2} \sin \frac{n\pi}{6} \right] \sin\left(n\omega t - \frac{2n\pi}{3}\right) \\ v_{cn} &= \sum_{n=1,3,5,\dots}^{\infty} \frac{4V_{in}}{3n\pi} \left[ 1 + \sin \frac{n\pi}{2} \sin \frac{n\pi}{6} \right] \sin\left(n\omega t - \frac{4n\pi}{3}\right) \end{aligned} \quad (14)$$

$$\begin{aligned} v_{ab} &= v_{an} - v_{bn} = \sum_{n=1,3,5,\dots}^{\infty} \frac{4V_{in}}{n\pi} \sin \frac{n\pi}{2} \sin \frac{n\pi}{3} \sin\left(n\omega t + \frac{n\pi}{6}\right) \\ v_{bc} &= v_{bn} - v_{cn} = \sum_{n=1,3,5,\dots}^{\infty} \frac{4V_{in}}{n\pi} \sin \frac{n\pi}{2} \sin \frac{n\pi}{3} \sin\left(n\omega t - \frac{n\pi}{2}\right) \\ v_{ca} &= v_{cn} - v_{an} = \sum_{n=1,3,5,\dots}^{\infty} \frac{4V_{in}}{n\pi} \sin \frac{n\pi}{2} \sin \frac{n\pi}{3} \sin\left(n\omega t - \frac{7n\pi}{6}\right) \end{aligned} \quad (15)$$


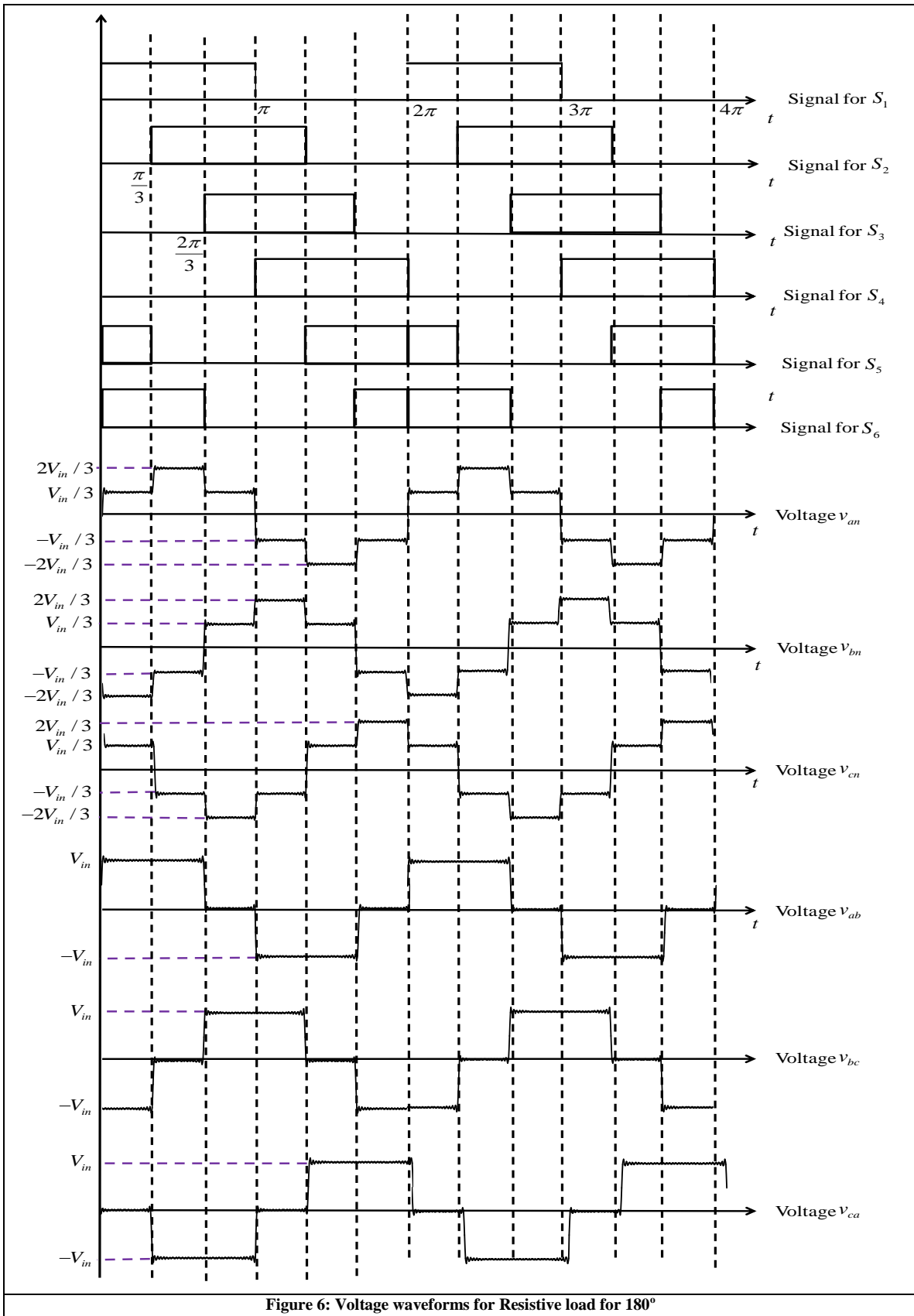


Figure 6: Voltage waveforms for Resistive load for 180°
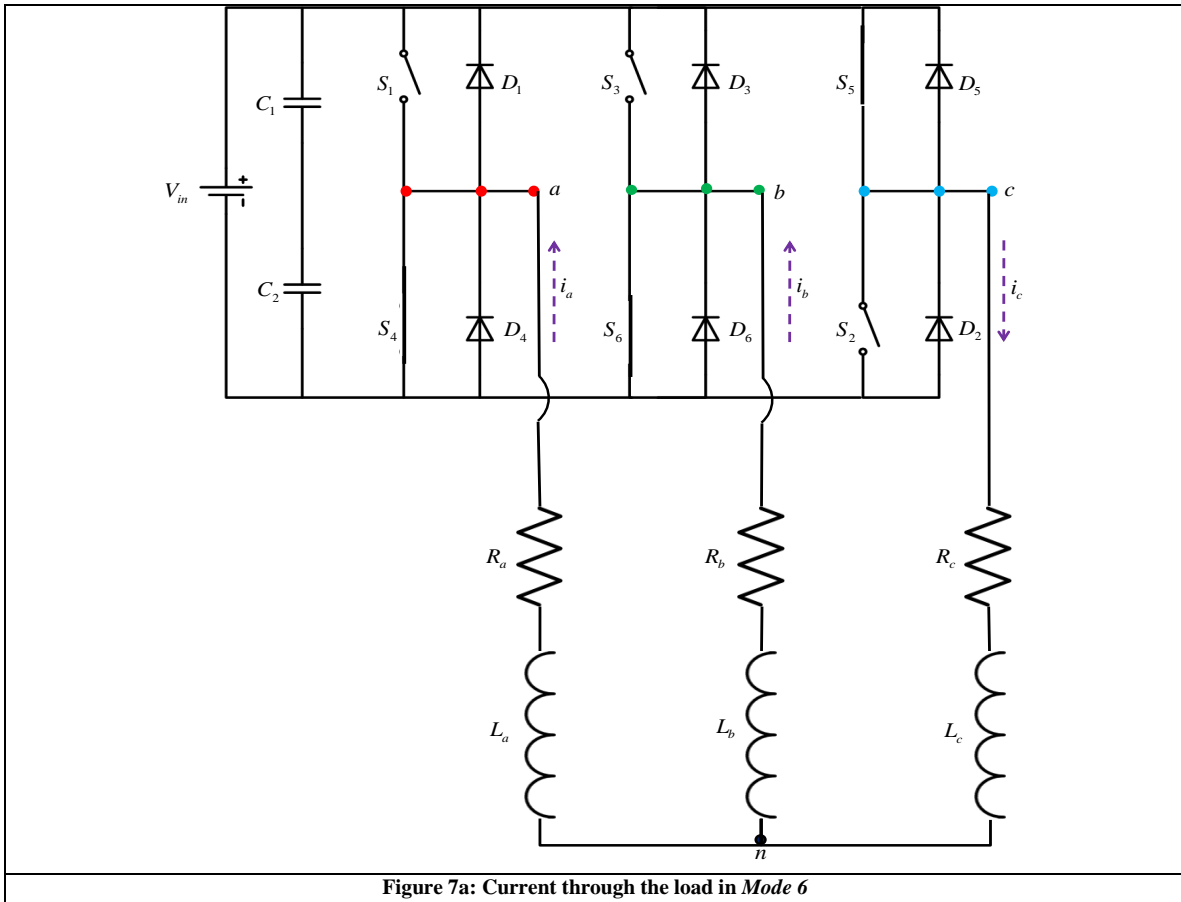
### 180-Degree Conduction with Star Connected $R-L$ Load

In *mode 1* the switches  $S_5, S_6$  and  $S_1$  are turned *on*. The mode previous to *mode 1* was *mode 6* and in *mode 6* the switches  $S_4, S_5$  and  $S_6$  were *on*. In the transition from *mode 6* to *mode 1* the switch  $S_4$  is turned *off* and  $S_1$  turned *on* and the current  $i_a$  changes its direction (*outgoing phase*). When the switch  $S_4$  was *on*, the direction of current was from point  $n$  to point  $a$ , the circuit configuration is shown in **Figure 7a** and the equivalent circuit is shown in **Figure 7b**. When  $S_1$  is turned *on* the direction of current should be from point  $a$  to point  $n$ . However, due to the presence of inductance, the current cannot change its direction instantaneously and continues to flow in the previous direction through diode  $D_1$  (**Figure 7c**) and the equivalent circuit of the configuration is shown in **Figure 7d**. Once  $i_a = 0$ , the diode  $D_1$  ceases to conduct and the current starts flowing through  $S_1$  as shown already in **Figure 3a** and **Figure 3b**. When ever one mode gets over and the next mode starts, the current of the outgoing phase cannot change its direction immediately due to presence of the inductance and hence completes its path through the freewheeling diode.





The phase currents are determined as follows:

$$\begin{aligned}
 i_a &= \sum_{n=1,3,5,\dots}^{\infty} \frac{1}{\sqrt{R^2 + (n\omega L)^2}} \frac{4V_{in}}{3n\pi} \left[ 1 + \sin \frac{n\pi}{2} \sin \frac{n\pi}{6} \right] \sin(n\omega t - \theta_n) \\
 i_b &= \sum_{n=1,3,5,\dots}^{\infty} \frac{1}{\sqrt{R^2 + (n\omega L)^2}} \frac{4V_{in}}{3n\pi} \left[ 1 + \sin \frac{n\pi}{2} \sin \frac{n\pi}{6} \right] \sin\left(n\omega t - \frac{2n\pi}{3} - \theta_n\right) \\
 i_c &= \sum_{n=1,3,5,\dots}^{\infty} \frac{1}{\sqrt{R^2 + (n\omega L)^2}} \frac{4V_{in}}{3n\pi} \left[ 1 + \sin \frac{n\pi}{2} \sin \frac{n\pi}{6} \right] \sin\left(n\omega t - \frac{4n\pi}{3} - \theta_n\right)
 \end{aligned} \tag{16}$$

where

$$\theta_n = \tan^{-1}\left(\frac{n\omega L}{R}\right)$$

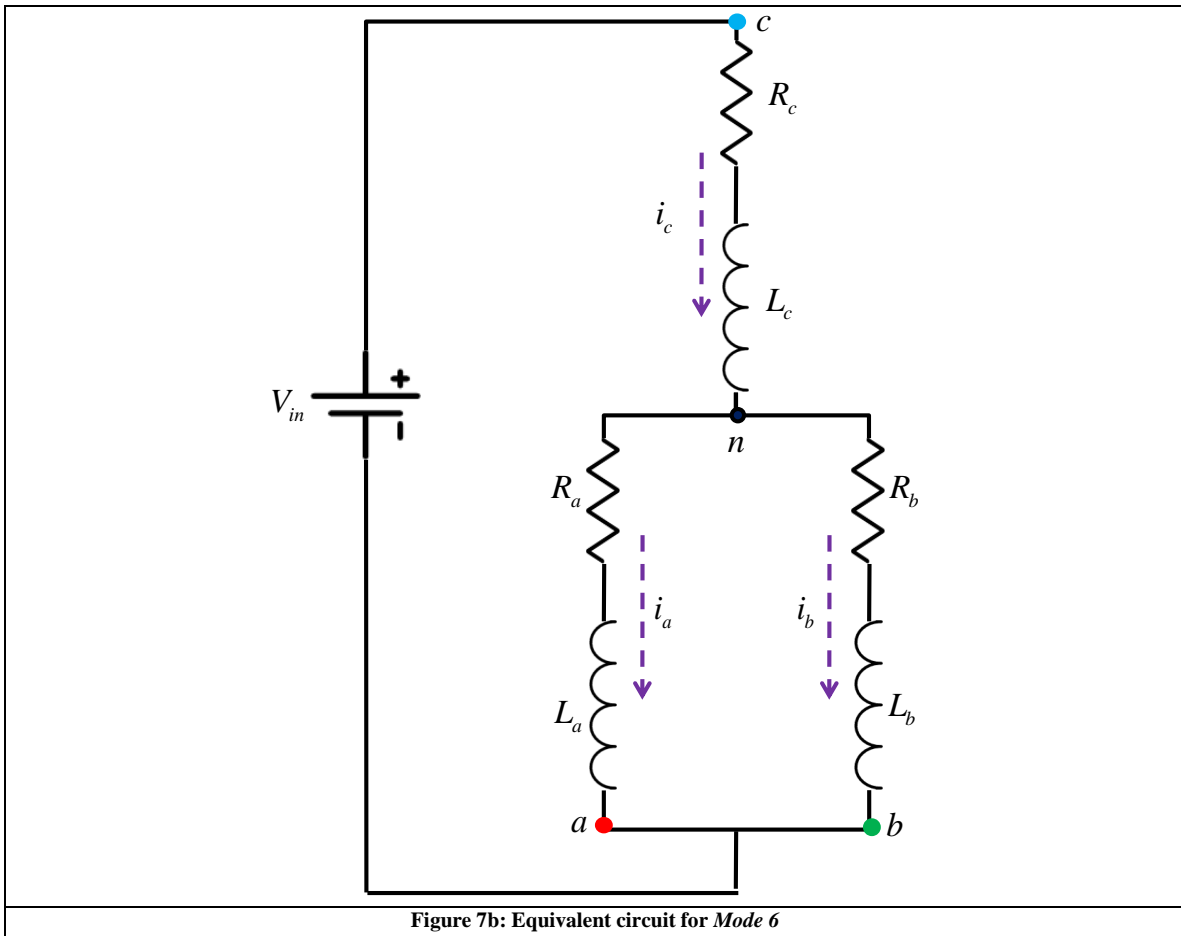

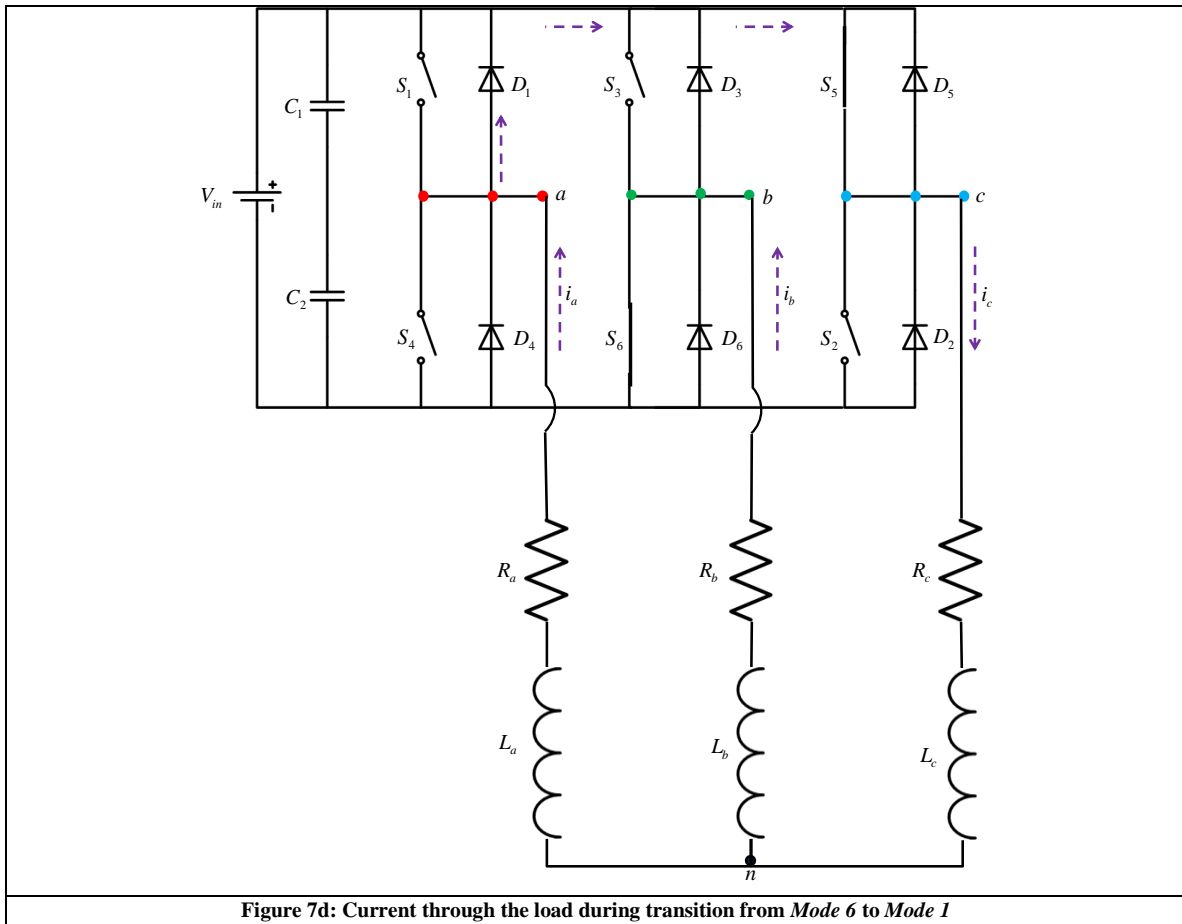

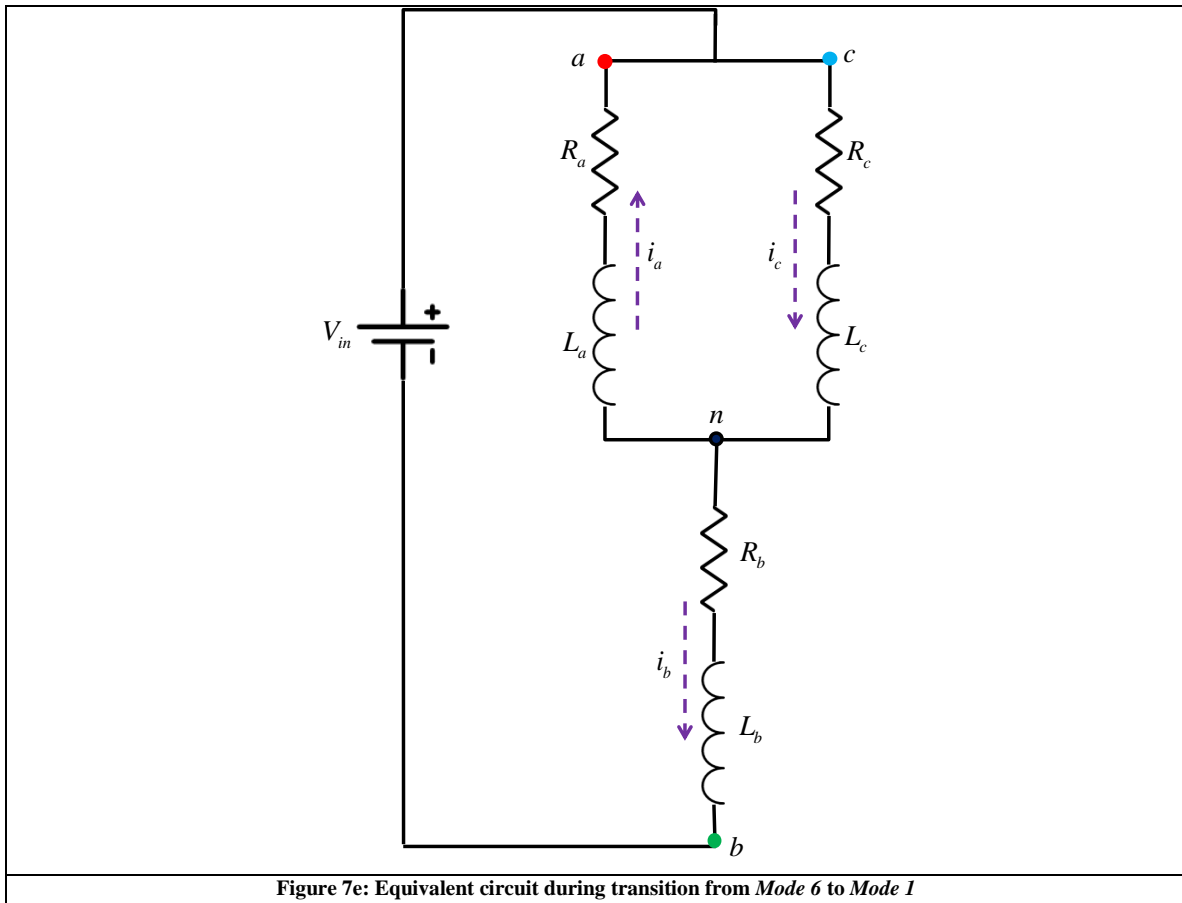


Figure 7e: Equivalent circuit during transition from Mode 6 to Mode 1

**Suggested Reading:**

- [1] M. H. Rashid, *Power Electronics: Circuits, Devices and Applications*, 3<sup>rd</sup> edition, Pearson, 2004
- [2] V. R. Moorthi, *Power Electronics: Devices, Circuits and Industrial Applications*, Oxford University Press, 2007



## Lecture 16: Voltage Control of DC-AC Inverters Using PWM

### Voltage Control of DC-AC Inverters Using PWM

#### Introduction

The topics covered in this chapter are as follows:

- Need for PWM
- Single Pulse Width Modulation
- Sinusoidal Pulse Width Modulation
- Three Phase Sinusoidal Pulse Width Modulation

#### Need for PWM in Voltage Source Inverters

The electric motors used in EV applications are required to have large speed ranges as shown in **Figure 1**. Large speed ranges can be achieved by feeding the motor with voltages of different frequencies and also different voltage magnitudes. One of the most convenient voltage control technique to generate variable frequency and magnitude voltages is **Pulse Width Modulation (PWM)**.

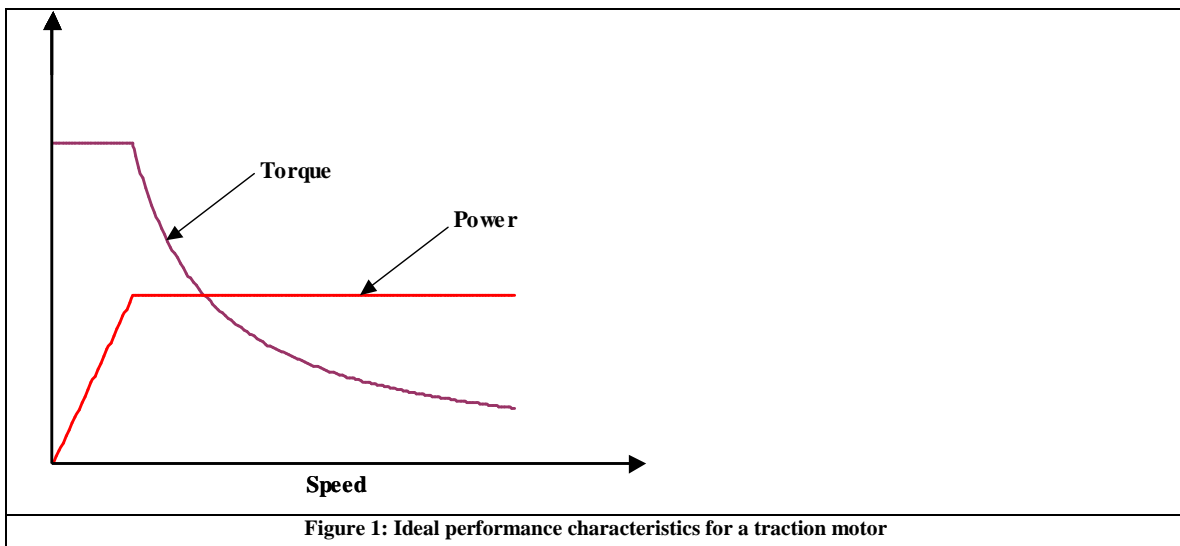


Figure 1: Ideal performance characteristics for a traction motor

The voltage control techniques for single phase inverters are:

- **Single Pulse Width Modulation**
- **Multiple Pulse Width Modulation**
- **Sinusoidal Pulse Width Modulation**
- Modified Sinusoidal Pulse Width Modulation
- Phase Displacement Control

Some of the important voltage control techniques for three phase inverters are:

- **Sinusoidal PWM**
- Space vector modulation

In this lecture, the techniques marked bold are discussed.

## Voltage Control of Single Phase Inverter

The single phase DC-AC inverter considered in this section is shown in **Figure 2**.

### Single Pulse Width Modulation

In this modulation only one pulse per half cycle exists and the width of the pulse is varied to control the inverter output voltage. The generation of the gating signals and the output voltage of single phase full-bridge inverters are shown in **Figure 3**. The gating signals are generated by comparing a rectangular reference signal of amplitude  $A_r$  with a triangular carrier wave of amplitude  $A_c$ . *The frequency of the reference signal determines the fundamental frequency of the output voltage.* The ratio of  $A_r$  to  $A_c$  is the control variable and defined as the amplitude *modulation index* or *modulation index* and is given by

$$M = \frac{A_r}{A_c} \quad (1)$$

The output voltage shown in **Figure 3** can be expressed as

$$v_o = \sum_{n=1,3,5,\dots}^{\infty} \frac{4V_{in}}{n\pi} \sin \frac{n\pi}{2} \sin \frac{n\delta}{2} \sin n\omega t \quad (2)$$

And the rms value of the output voltage is

$$V_{o,rms} = \left[ \frac{2}{2\pi} \int_{\frac{\pi-\delta}{2}}^{\frac{\pi+\delta}{2}} V_{in}^2 d(\omega t) \right]^{1/2} = V_{in} \sqrt{\frac{\delta}{\pi}} \quad (3)$$

The relation between  $\delta$  and modulation index  $M$  is:

$$M = \frac{\delta}{\pi} = \frac{A_r}{A_c} \quad (4)$$

Using **equation 4**, the rms voltage can be expressed as

$$V_{o,rms} = V_{in} \sqrt{M} \quad (5)$$

The load current in case of resistive load is

$$i_L = \sum_{n=1,3,5,\dots}^{\infty} \frac{4V_{in}}{n\pi R} \sin \frac{n\pi}{2} \sin \frac{n\delta}{2} \sin n\omega t \quad (6)$$

For **R-L** load, the load current is given by


$$i_L = \sum_{n=1,3,5,\dots}^{\infty} \frac{4V_{in}}{n\pi \sqrt{R^2 + (n\omega L)^2}} \sin \frac{n\pi}{2} \sin \frac{n\delta}{2} \sin(n\omega t - \theta_n) \quad (7)$$



where

$$\theta_n = \tan^{-1} \left( \frac{\omega L}{R} \right)$$

The currents for both  $R$  and  $R-L$  loads are also shown in **Figure 3**.

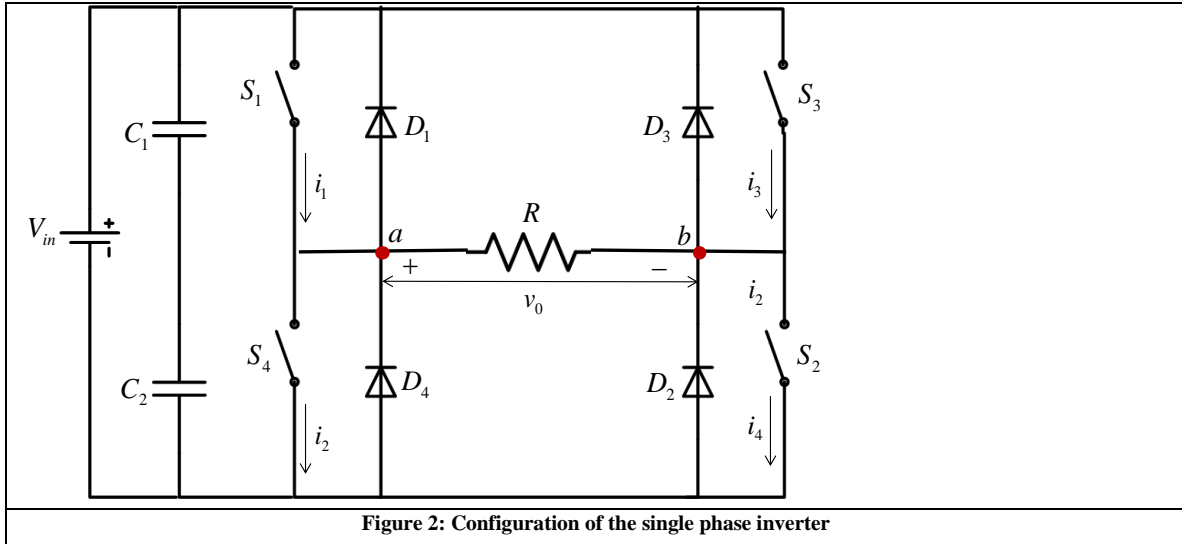By varying  $A_r$  from 0 to  $A_c$ , the pulse width  $\delta$  can be modified from  $0^\circ$  to  $180^\circ$  and the rms voltage  $V_{o,rms}$  from 0 to  $V_{in}$ . The harmonic content for different harmonics for different modulation indices is shown in **Figure 4**.



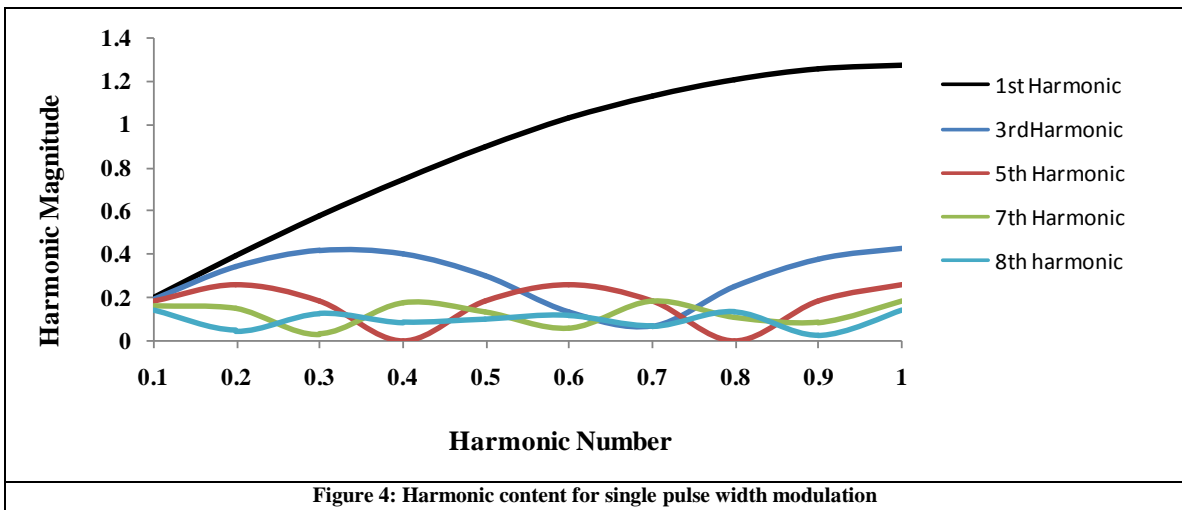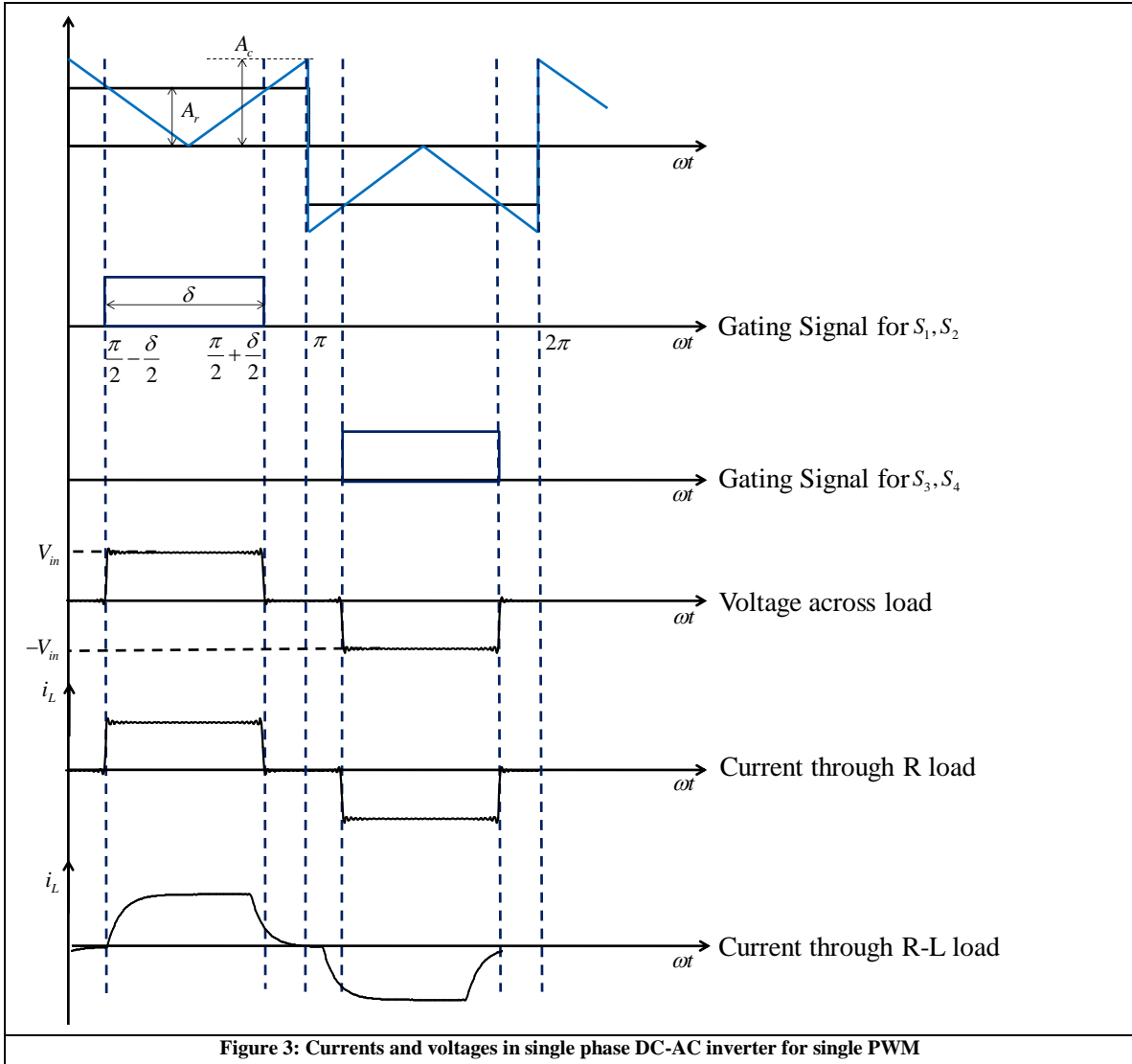

### Single Pulse Width Modulation

The harmonic content in the voltage  $v_o$  can be reduced by using several pulses in each half cycle. The generation of the gating signal is done by comparing a reference signal with a triangular carrier waveform (**Figure 5**). The generated gate signals are shown in **Figure 5**. The frequency of the reference signal  $f_r$  and the carrier signal  $f_c$  determine the number of pulses per half cycle ( $n_p$ ) as

$$n_p = \frac{f_c}{2f_r} = \frac{m_f}{2} \quad (8)$$

where

$$m_f = \frac{f_c}{f_r} \text{ is frequency modulation ration}$$

The instantaneous output voltage ( $v_o$ ) and the current for resistive and inductive loads are shown in **Figure 5**. The output voltage in terms of Fourier series is given by

$$v_o = \sum_{n=1,3,5,\dots}^{\infty} B_n \sin(n\omega t)$$

where

$$B_n = \sum_{m=1}^{2n_p} \frac{4V_{in}}{n\pi} \sin \frac{n\pi}{2} \sin \frac{n\delta}{2} \sin \left( n\omega t - n\alpha_m + \frac{(2n_p - 1)}{2} n\delta \right)$$

where

$n_p$  is number of pulses in the half cycle

$M$  is modulation index

$\delta$  is width of each pulse

$\alpha$  is the angle of left most pulse

$$\delta = \frac{M}{n_p} \times 180$$

$$\alpha = \frac{180(1-M)}{2n_p}$$

$$\alpha_m = (2m-1)\alpha + (m-1)\delta \quad (9)$$

The magnitude of the currents for **R-L** load are given by

$$i_L = \sum_{n=1,3,5,\dots}^{\infty} A_n \sin(n\omega t)$$

where

$$A_n = \sum_{m=1}^{2n_p} \frac{4V_{in}}{n\pi} \frac{1}{Z_n} \sin \frac{n\pi}{2} \sin \frac{n\delta}{2} \sin \left( n\omega t - n\alpha_m + \frac{(2n_p - 1)}{2} n\delta - \theta_n \right) \quad (10)$$


where

$$Z_n = \sqrt{R^2 + (n\omega L)^2}$$

$$\theta_n = \tan^{-1} \left( \frac{n\omega L}{R} \right)$$

The rms value of the output voltage is
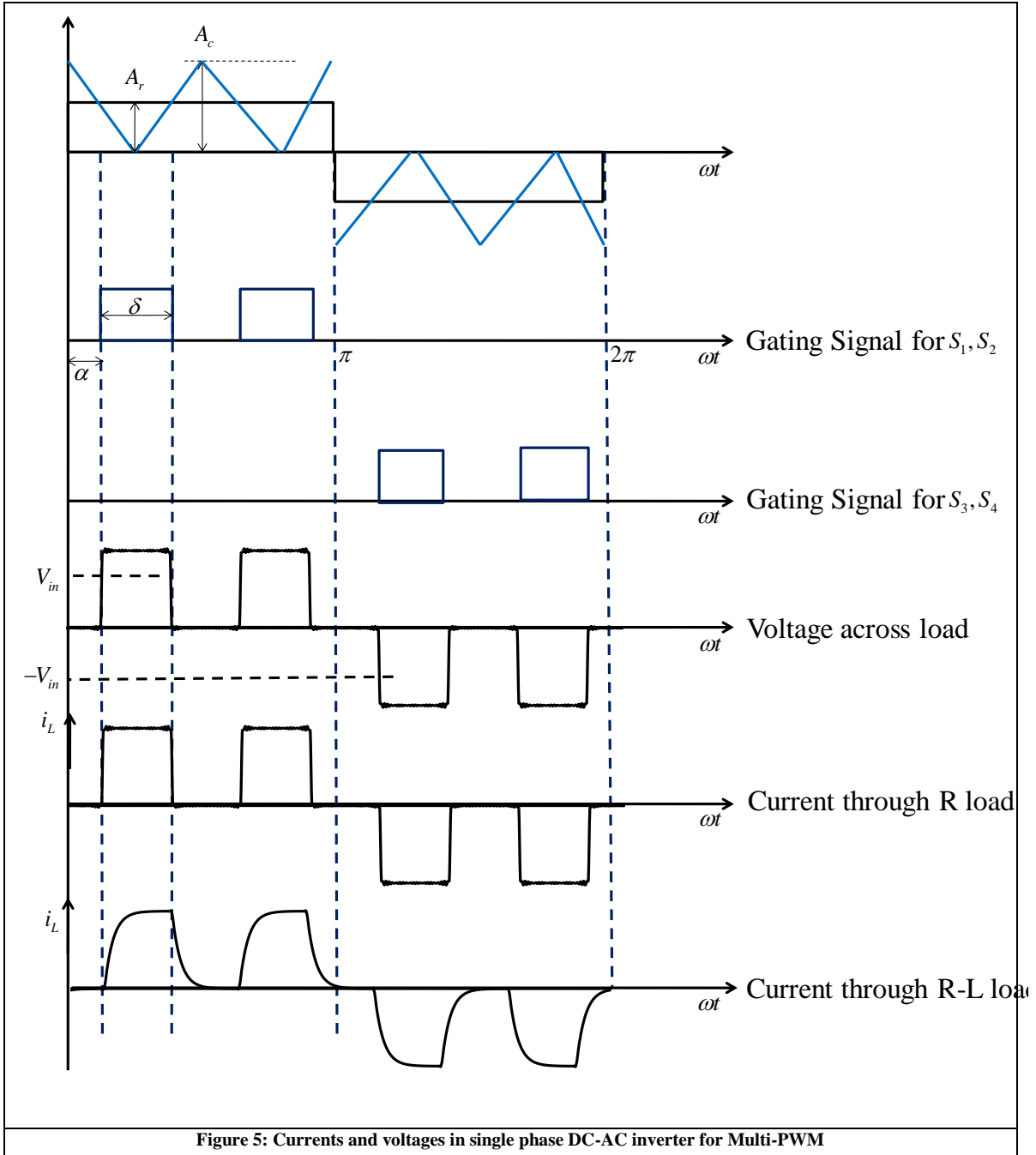
$$V_{o,rms} = \left[ \frac{2n_p}{2\pi} \int_{\left(\frac{\pi}{2}-\delta\right)/2}^{\left(\frac{\pi}{2}+\delta\right)/2} V_{in}^2 d(\omega t) \right]^{1/2} = V_{in} \sqrt{\frac{n_p \delta}{\pi}} \quad (11)$$



**Sinusoidal Pulse Width Modulation**

In sinusoidal PWM, also called *sine-PWM*, the resulting pulse widths are varied throughout the half cycle in such a way that they are proportional to the instantaneous value of the reference sine wave at the centre of the pulses. The distance between the centres of the pulses is kept constant as in multi-PWM. Voltage control is achieved by varying the widths of all pulses without disturbing the sinusoidal relationship. The generation of the gating signals for sinusoidal PWM and the output voltage and currents is shown in **Figure 6**.

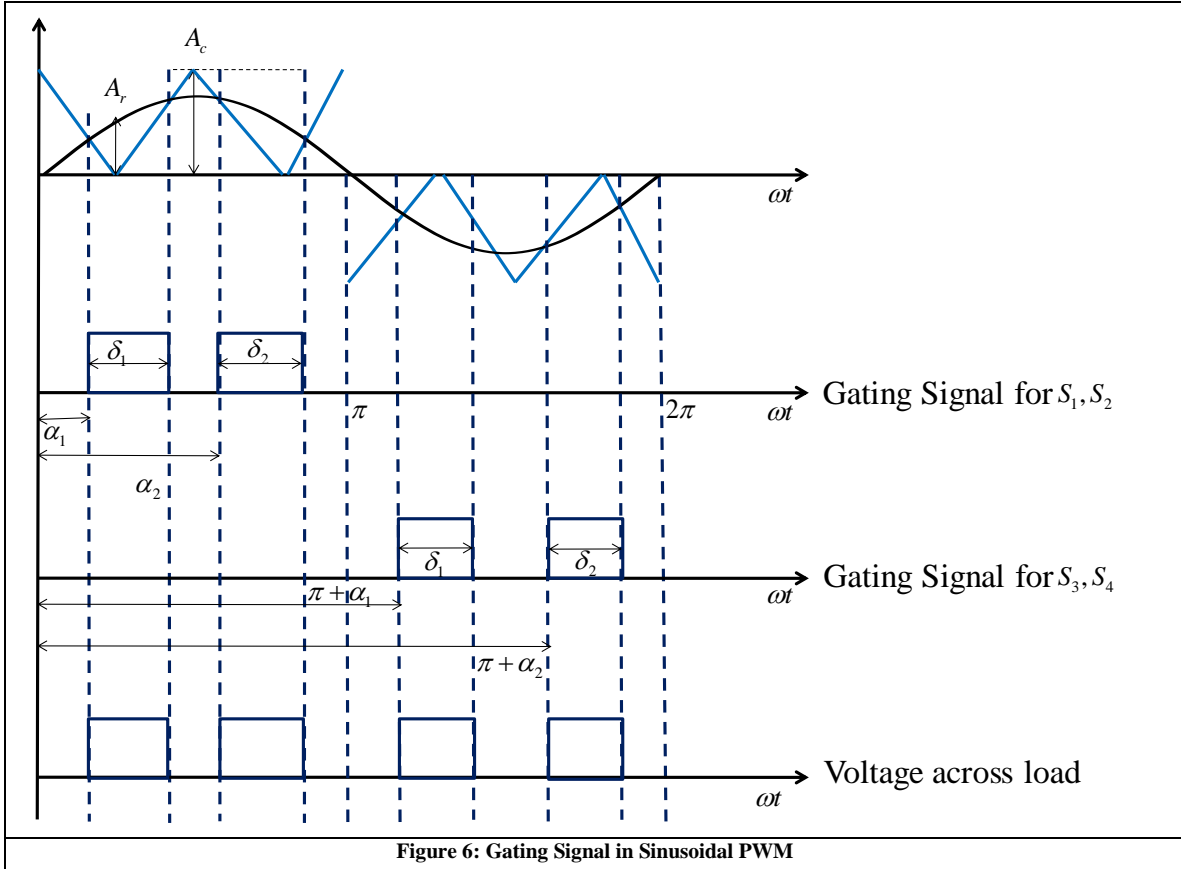


Figure 6: Gating Signal in Sinusoidal PWM

The output voltage in case of sinusoidal PWM can be expressed as

$$v_o = \sum_{n=1,3,5,\dots}^{\infty} \frac{4V_{in}}{n\pi} \sum_{k=1,2,\dots}^{n_p} \sin \frac{n\delta_k}{2} \left[ \cos \left( n\omega t - \frac{n\delta_k}{2} - n\alpha_k \right) \right] \tag{12}$$

where

- $n_p$  is the number of pulses in the half cycle
- $\delta_k$  is the width of the  $k$ th pulse
- $\alpha_k$  is the starting angle of the  $k$ th pulse



The width of the  $k^{\text{th}}$  pulse ( $\delta_k$ ) is approximately given by

$$\delta_k = \left( \frac{\pi}{n_p} \right) m_a \sin(\alpha_k) \quad (13)$$

where

$$m_a = \frac{A_r}{A_c} \text{ is the modulation index}$$

The value of the starting angle of the  $k^{\text{th}}$  pulse ( $\alpha_k$ ) is given by numerically solving the following equation

$$m_a \sin(\alpha_k) = -\frac{m_f}{\pi} \alpha_k + (2k - 1) \quad (14)$$

where

$$m_f = 2n_p$$

The angles  $\theta$  and  $\alpha$  for a sine PWM with 6 pulses per half cycle are calculated using **equations 13** and **14** and listed in **Table 1**. The waveforms of the voltage and current are shown in **Figure 7**.

The r.m.s value of the output voltage is

$$v_o = V_{in} \sqrt{\sum_{m=1}^{2n_p} \frac{\delta_m}{\pi}} \quad (15)$$

The load for an **R-L** load is given by

$$i_L = \sum_{n=1,3,5,\dots}^{\infty} \frac{4V_{in}}{n\pi Z_n} \sum_{k=1,2,\dots}^{n_p} \sin \frac{n\delta_k}{2} \left[ \cos \left( n\omega t - \frac{n\delta_k}{2} - n\alpha_k - \theta_n \right) \right] \quad (16)$$


where

$$Z_n = \sqrt{R^2 + (n\omega L)^2}$$

$$\theta_n = \tan^{-1} \left( \frac{\omega L}{R} \right)$$

**Table 1: The starting angle and pulse width for Sine PWM with 6 pulses per half cycle**

Pulse Number	Starting angle $\alpha$ [°]	Pulse Width $\delta$ [°]
1	12.98	4.04
2	39.30	11.40
3	66.73	16.54
4	96.05	17.90
5	127.90	14.20
6	162.26	5.49

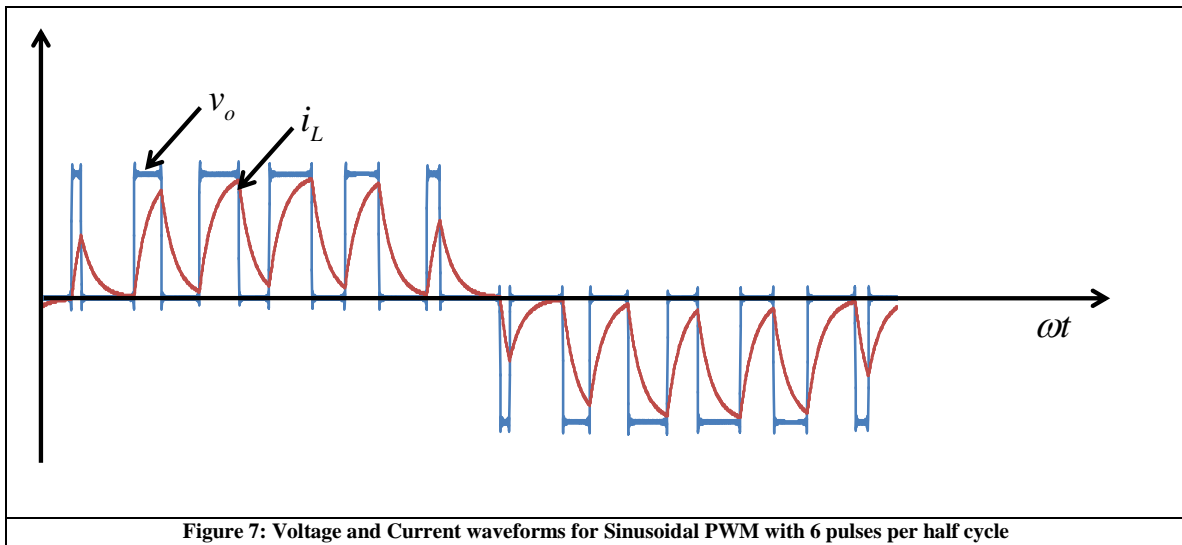

### Voltage Control of Three Phase DC-AC Inverter using Sinusoidal PWM

The generation of gating signals for a three phase DC-AC inverter with sine PWM are shown in **Figure 8**. There are three sinusoidal reference waves ( $v_{ra}, v_{rb}, v_{rc}$ ) each shifted by  $120^\circ$ . A triangular carrier wave is compared with the reference signals to produce the gating signals. Comparing the carrier signal  $v_{cr}$  with the reference phases  $v_{ra}, v_{rb}, v_{rc}$  produces the signals for gates 1, 2 and 3 ( $g_1, g_2, g_3$ ). The instantaneous line-to-line output voltage is

$$v_{ab} = V_{in} (g_1 - g_3) \quad (12)$$

The output voltage is generated by eliminating the condition that two switching devices in the same arm cannot conduct at the same time.

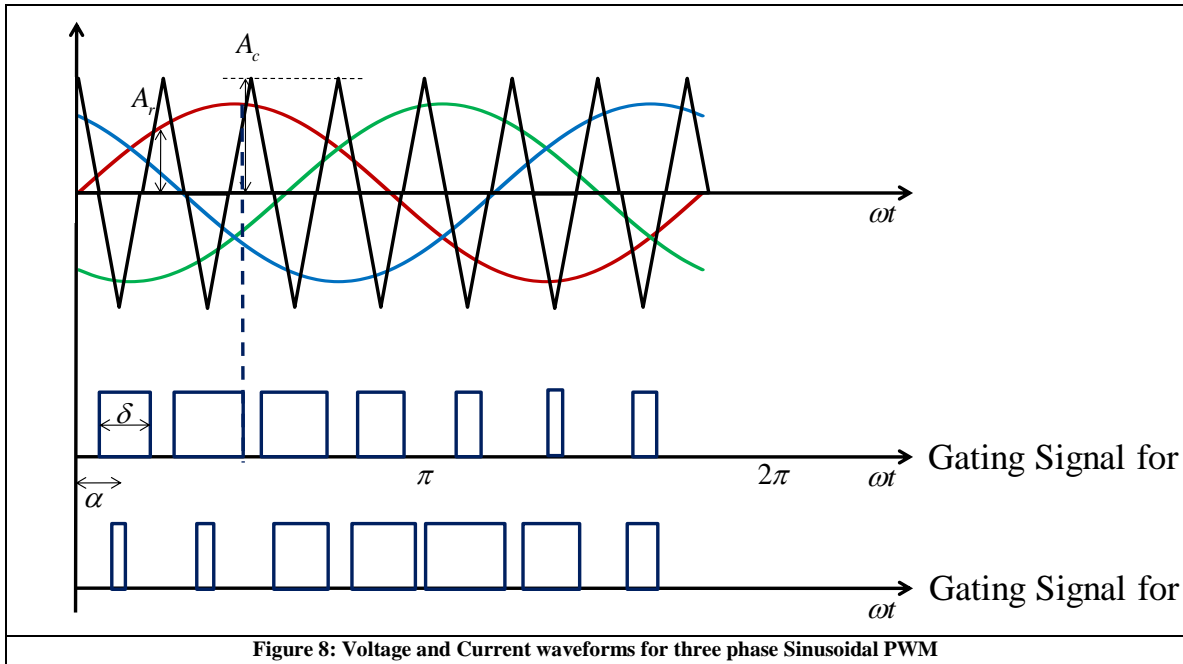


Figure 8: Voltage and Current waveforms for three phase Sinusoidal PWM

**Suggested Reading:**

- [1] M. H. Rashid, *Power Electronics: Circuits, Devices and Applications*, 3<sup>rd</sup> edition, Pearson, 2004
- [2] V. R. Moorthi, *Power Electronics: Devices, Circuits and Industrial Applications*, Oxford University Press, 2007

# **PREVIOUS YEAR QUESTION PAPERS**

**III B. Tech I Semester Regular/Supplementary Examinations, October/November - 2019**

**POWER ELECTRONICS**

(Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 70

Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)

2. Answer **ALL** the question in **Part-A**

3. Answer any **FOUR** Questions from **Part-B**

**PART -A**

(14 Marks)

1. a) What are the necessary conditions for turning ON a SCR? [2M]
- b) What is reactive power input of single phase full converter at  $\alpha = 30^\circ$ ? [2M]
- c) Give the list of applications of three phase controlled converters. [2M]
- d) What is the principle of operation of fly-back converter in CCM? [3M]
- e) What are the difference between VSI and CSI? [3M]
- f) Draw the waveforms of single phase ac voltage controller with R load with  $\alpha = 60^\circ$ . [2M]

**PART -B**

(56 Marks)

2. a) What are the types of switching characteristics of SCR? How do you known turn ON and turn OFF times from the switching characteristics? Explain. [7M]
- b) What are the requirements of good gate driver circuits of IGBT and MOSFET? Explain. [7M]
3. a) Explain the operation of single phase full-wave controlled rectifier using center tapped transformer with R-L load under continuous mode of operation. Draw the waveforms of output voltage, voltage across SCR and average load current for  $\alpha = 45^\circ$ . [7M]
- b) A single phase fully controlled bridge converter is connected to R-L load with  $R = 10 \Omega$  and  $L = 6 \text{ mH}$ . The converter is supplied from 230 V, 50 Hz ac supply. (i) Determine average and rms load current; (ii) if one SCR of the bridge configuration is open circuited due to fault, what will be the average and rms load current at this condition? [7M]
4. a) Draw the output voltage waveforms and derive the average and rms voltage expressions of three phase semi converter on discontinuous conduction mode. [7M]
- b) A three phase full converter is connected to a resistive load of  $10 \Omega$ . If the firing angle of SCR is  $\alpha = 45^\circ$  and it feeds 4 kW power to a resistive load determine the amplitude of maximum line input voltage. [7M]
5. a) Explain the operation of boost converter in the CCM mode and obtain the expression for amplitude of ripple current. [7M]
- b) A buck-boost converter has the input voltage of 12 V and it operates at 20 kHz, when the average output voltage is 24 V, the average load current is 1.2 A, it is having  $L = 300 \mu\text{H}$ ,  $C = 150 \mu\text{F}$ . Find duty cycle, ripple current through the inductor, ripple voltage and critical values of L and C. [7M]

6. a) Discuss various PWM techniques used in inverters. How sinusoidal PWM is useful in the harmonic elimination? [7M]
- b) A 50 Hz single – phase full bridge produces a square wave voltage across load when operating from a 300 V DC supply, the AC load consists of a resistance of  $30 \Omega$  in series with inductance 15 mH. Determine the frequencies and r.m.s values of the lowest order harmonics in the AC load current. [7M]
7. Explain the operation of a three – phase bidirectional AC voltage controlled feeding star connected with resistive load. Draw the output voltage waveform with  $\alpha = 60^\circ$  and  $\alpha = 120^\circ$ . [14M]

\*\*\*\*\*

**III B. Tech I Semester Regular/Supplementary Examinations, October/November - 2019**  
**POWER ELECTRONICS**  
 (Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 70

- Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)  
 2. Answer **ALL** the question in **Part-A**  
 3. Answer any **FOUR** Questions from **Part-B**

**PART -A****(14 Marks)**

1. a) Define holding current. [2M]
- b) What are the drawbacks of source inductance on the performance of phase controlled rectifiers? [2M]
- c) Compare continuous and discontinuous modes of operation of converters. [2M]
- d) List any two applications of choppers. [3M]
- e) List differences between CSI and VSI. [3M]
- f) Explain the principle of Integral Cycle control. [2M]

**PART -B****(56 Marks)**

2. a) Explain the various turn-on methods of SCRs. [7M]
- b) Following are the specifications of a thyristor operating from a peak supply voltage of 500 V. [7M]
 

Repetitive peak current,  $I_p = 250 \text{ A}$ ;

$$\left(\frac{di}{dt}\right)_{\max} = 60 \text{ A} / \mu\text{s}, \left(\frac{dv_a}{dt}\right)_{\max} = 200 \text{ V} / \mu\text{s}$$

Take a factor of safety as 2 for the specifications mentioned above. Design a suitable snubber circuit, if the minimum load resistance is  $20 \Omega$ . Take  $\xi=0.65$ .
3. a) Explain the effect of source inductance on the performance of a single-phase full converter with the help of voltage waveforms. Derive an expression for its output voltage in terms of supply voltage, source inductance and load current. [7M]
- b) A single phase semi converter is supplied from 230 V, 50 Hz source. The load consists of  $R= 10 \Omega$  and  $E = 100 \text{ V}$  and a large inductor so as to maintain the load current constant. For a firing angle of  $45^\circ$ , find i) average output voltage ii) average output current iii) average and rms values of thyristor currents iv) input power factor. [7M]
4. a) Explain the working of three phase semi converter with relevant wave forms with highly inductive load for firing angle of  $30^\circ$ . [7M]
- b) A three-phase, half-wave converter is supplying a load with a continuous constant current of 40A over a firing angle range from 0 to  $75^\circ$ . What will be the power dissipated by the load at these limiting values of firing angle? The supply voltage is 415 V (line). [7M]

5. a) Explain the working of boost converter with relevant waveforms in CCM mode and also derive the expressions for critical values of L and C. [10M]
- b) The buck regulator has an input voltage of  $V_s = 15$  V. The required average output voltage is  $V_a = 5$  V at  $R = 400 \Omega$  and the peak-to-peak output ripple voltage is 10 mV. The switching frequency is 20 kHz. If the peak-to-peak ripple current of inductor is limited to 0.6 A, determine: i) the duty cycle ii) the filter inductance L, iii) the filter capacitor C. [4M]
6. a) With necessary waveforms explain the working of single phase full bridge inverter with RL load and also derive the expression for RMS value of output voltage. [7M]
- b) Single phase half bridge inverter has a resistive load of  $R = 3 \Omega$  and DC input voltage of 50 V. Calculate: i) RMS output voltage at fundamental frequency, ii) output power, iii) Average and peak current of each thyristors. [7M]
7. a) Describe the principle of phase control in single phase half wave ac voltage regulator. Derive the expressions for average and rms value of output voltage for this control. [7M]
- b) A single phase full wave ac voltage controller has a load of  $R = 5 \Omega$  and input voltage is 230 V, 50 Hz. If the load power is 5 kW, find firing angle delay of SCR and input power factor. [7M]

\*\*\*\*\*



**III B. Tech I Semester Regular/Supplementary Examinations, October/November - 2019**  
**POWER ELECTRONICS**  
 (Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 70

- Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)  
 2. Answer **ALL** the question in **Part-A**  
 3. Answer any **FOUR** Questions from **Part-B**

**PART -A****(14 Marks)**

1. a) Why protection is required during the operation of SCR? [2M]
- b) Calculate power delivered to a 1 kW heater which is connected to a single phase half wave controlled rectifier when  $\alpha = 30^\circ$ , Supply voltage = 220V. [2M]
- c) Give the conduction periods of lower group thyristors in 6 pulse converters for 60 Hz frequency with  $\alpha = 60^\circ$ . [2M]
- d) Write the advantages of buck-boost converter. [3M]
- e) Mention the advantages of pulse width modulation control strategy. [3M]
- f) Draw the waveforms of single phase unidirectional ac voltage controller with RL load with  $\alpha = 30^\circ$ . [2M]

**PART -B****(56 Marks)**

2. a) Describe the switching characteristics of power MOSFET and what are the requirements of gate drive to get less turn OFF and turn ON times? [7M]
- b) Explain the design of snubber circuit used for a SCR, how it provides different voltage protections? [7M]
3. a) Explain the operation of single phase full-wave controlled rectifier using center tapped transformer having R-L load and freewheeling diode under discontinuous and continuous conduction modes with the help of wave forms. [7M]
- b) A single phase fully controlled bridge converter is supplied from 230 V, 50 Hz ac supply and it is fed to load consisting of  $R = 10 \Omega$  and large inductance such that load current is constant. When the firing angle is  $45^\circ$ , i) calculate average and rms current ii) if the source inductance of 1.5 mH is connected find the average voltage and overlap angle at the same firing angle. [7M]
4. a) Derive the average and rms voltage expressions of three phase half-wave controlled rectifier having R load operated on discontinuous conduction mode. [7M]
- b) A three phase full converter is fed by 230 V, 50 Hz, three phase supply, the average load current is 25A and the load is highly inductive. For firing angle of  $60^\circ$  find average, rms and peak current through the SCR's. [7M]
5. a) Explain the operation of buck converter in the DCM mode and obtain the expression for amplitude of ripple current. [7M]
- b) A buck-boost converter has the input voltage of 24 V and it operates at 30 kHz, when the duty cycle is 0.25,  $L = 300 \mu\text{H}$ ,  $C = 150 \mu\text{F}$  and the average load current is 1.5 A. Determine average output voltage, peak to peak ripple current through the inductor, peak to peak ripple voltage and critical values of L and C. [7M]

6. a) Draw a neat circuit diagram for single phase full bridge inverter feeding inductive load. [7M]  
What is the function of feedback diodes?
- b) Explain the working of a current source inverter with a neat circuit diagram and waveforms. [7M]
7. a) A single phase voltage controller has input voltage of 230 V, 50 Hz; the load consists of a resistance  $30 \Omega$  in series with inductance 15 mH, for 6 cycles off and 4 cycles on. Determine the output voltage and input power factor. [7M]
- b) Explain the synchronous connection charge control of a Single-phase transformer connection charger. [7M]

\*\*\*\*\*

**III B. Tech I Semester Regular/Supplementary Examinations, October/November - 2019**  
**POWER ELECTRONICS**  
 (Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 70

- Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)  
 2. Answer **ALL** the question in **Part-A**  
 3. Answer any **FOUR** Questions from **Part-B**

**PART - A****(14 Marks)**

1. a) What is meant by reverse recovery time of a SCR? [2M]
- b) Calculate power delivered to a 1 kW heater which is connected to a single phase full wave controlled bridge rectifier, when  $\alpha = 90^\circ$ , Supply voltage = 220V? [2M]
- c) Give the conduction periods of upper group thyristors in 6 pulse converters for 60 Hz frequency with  $\alpha = 30^\circ$ . [2M]
- d) What is meant by fly back mode of operation of buck-boost converter? [3M]
- e) Mention the advantages of sinusoidal pulse width modulation control. [3M]
- f) Draw the static V – I characteristics of a TRIAC. [2M]

**PART - B****(56 Marks)**

2. a) Describe the switching characteristics of power IGBT and what are the requirements of gate drive to get less turn OFF and turn ON times? [7M]
- b) Discuss about the different turn ON methods of a SCR. [7M]
3. a) Explain the operation of single phase half-wave controlled rectifier having R-L load and freewheeling diode under discontinuous and continuous conduction modes with the help of wave forms. [7M]
- b) A single phase full converter is used to deliver a constant load current, it is operated such that overlap angle is  $15^\circ$  for a firing angle,  $\alpha = 0^\circ$ . Determine the overlap angles for firing angles  $\alpha = 30^\circ$ ,  $\alpha = 45^\circ$  and  $\alpha = 60^\circ$ . [7M]
4. a) Describe the operation of three phase full converter feeding an R load and draw the wave forms for any firing angle which is more than the  $90^\circ$ . [7M]
- b) A three-phase three pulse controlled rectifier with freewheeling diode  $D_F$  is fed from three phase, 400 V, 50 Hz ac supply and it is connected with a constant current load of 90 A at firing angle of  $\alpha = 45^\circ$ . Calculate dc output voltage, rms output voltage, average and rms current of free-wheeling diode. [7M]
5. a) Explain the working of buck converter in continuous conduction mode. Derive the expression for output voltage. [7M]
- b) A boost converter has the input voltage of 24 V and it operates at 20 kHz, when the average output voltage is 12 V, the average load current is 1.2 A, it is having  $L = 300 \mu\text{H}$ ,  $C = 150 \mu\text{F}$ . Find duty cycle, ripple current through the inductor, ripple voltage and critical values of L and C ? [7M]

6. a) Explain the working of a three phase inverter with  $120^\circ$  mode of conduction with three phase delta connected resistive load. [7M]
- b) A 50 Hz PWM inverter employs sinusoidal pulse width modulation based on sine-triangle comparison. If the triangular carrier frequency is 15 kHz, what will be the number of pulses per half period in the output waveform and with 80% modulation index what will be the width of the longest pulse? [7M]
7. a) Describe the operation of single phase full wave ac regulator feeding resistive load. Derive the expression for output voltage. [7M]
- b) A single phase ac voltage controller is employed for controlling the power flow from 230 V, 50 Hz source in to a load circuit consisting of  $R = 4 \Omega$  and  $\omega L = 3 \Omega$ . Calculate: i) the control range of Firing angle; ii) the maximum power delivered to load and power factor; iii) the maximum values of average and rms SCR currents. [7M]

\*\*\*\*\*

**III B. Tech I Semester Supplementary Examinations, October/November - 2020****POWER ELECTRONICS**

(Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 70

Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)2. Answer **ALL** the question in **Part-A**3. Answer any **FOUR** Questions from **Part-B****PART -A****(14 Marks)**

1. a) Define Latching Current. [2M]
- b) Why power factor of semi converter is better than full converter? [2M]
- c) Draw the circuit diagram of three phase M-3 controlled converter. [2M]
- d) List the applications of step up choppers. [3M]
- e) What is shoot through fault? Explain. [3M]
- f) A 1-phase voltage controller has input voltage of 230 V, 50 Hz for 6 cycles on and 4 cycles off. Determine RMS output voltage. [2M]

**PART -B****(56 Marks)**

2. a) Explain the operation of snubber circuit and also design the parameters of snubber circuit. [7M]
- b) Draw the two-transistor analogy of a SCR? Explain SCR operation with this analogy. [7M]
3. a) Explain the operation of single phase two pulse midpoint converter with relevant voltage and current waveforms and also derive the expression for average output voltage. [7M]
- b) A single phase semi converter is delivering power to RLE load with  $R = 5\Omega$ ,  $L = 10\text{ mH}$  and  $E = 80\text{ V}$ . The ac source voltage is 230 V, 50 Hz. For continuous conduction, find the average value of output current for a firing angle of  $50^\circ$ . If one of the SCR is damaged and open circuited find the new value of average output current on the assumption to continuous conduction. Also sketch the output voltage and current waveforms? [7M]
4. a) Explain the working of three-phase half wave uncontrolled rectifier with relevant wave forms for 'R' load. [7M]
- b) A Three phase fully controlled bridge converter is connected to a supply voltage of 230 V per phase and frequency of 50 Hz. The source inductance is 3 mH. The load current on dc side is constant at 15 A. If load consists of a dc source voltage of 400 V having an internal resistance of  $1\Omega$ . Find the firing angle and overlap angle. [7M]
5. a) Explain the principle of operation and working of buck converter with relevant waveforms in CCM mode. [10M]
- b) A boost regulator has an input voltage of  $V_s = 5\text{ V}$ . The average output voltage  $V_a = 15\text{ V}$  and the average load current  $I_a = 0.5\text{ A}$ . The switching frequency is 25 kHz. If  $L = 150\text{ }\mu\text{H}$  and  $C = 220\text{ }\mu\text{F}$ , determine (i) the duty cycle, (ii) the ripple current of inductor  $\Delta I$ , (iii) the critical values of L and C. [4M]

6. a) With necessary waveforms explain the working of single phase half bridge inverter with RL load and also derive the expression for RMS value of output voltage. [7M]
- b) Single phase full bridge inverter has a resistive load of  $R = 2.4$  ohms and DC input voltage of 48 volts. Calculate: i) RMS output voltage at fundamental frequency, ii) output power, iii) Average and peak current of each thyristors. [7M]
7. a) Explain the operation of a single phase AC voltage controller with a neat circuit diagram and output wave forms with respect to source voltage waveforms at  $\alpha = 60$  degrees for R-load. [7M]
- b) Explain the principle of integral cycle control with relevant waveforms and also derive the expression for rms value of output voltage, power delivered to load and input power factor. [7M]

\*\*\*\*\*